
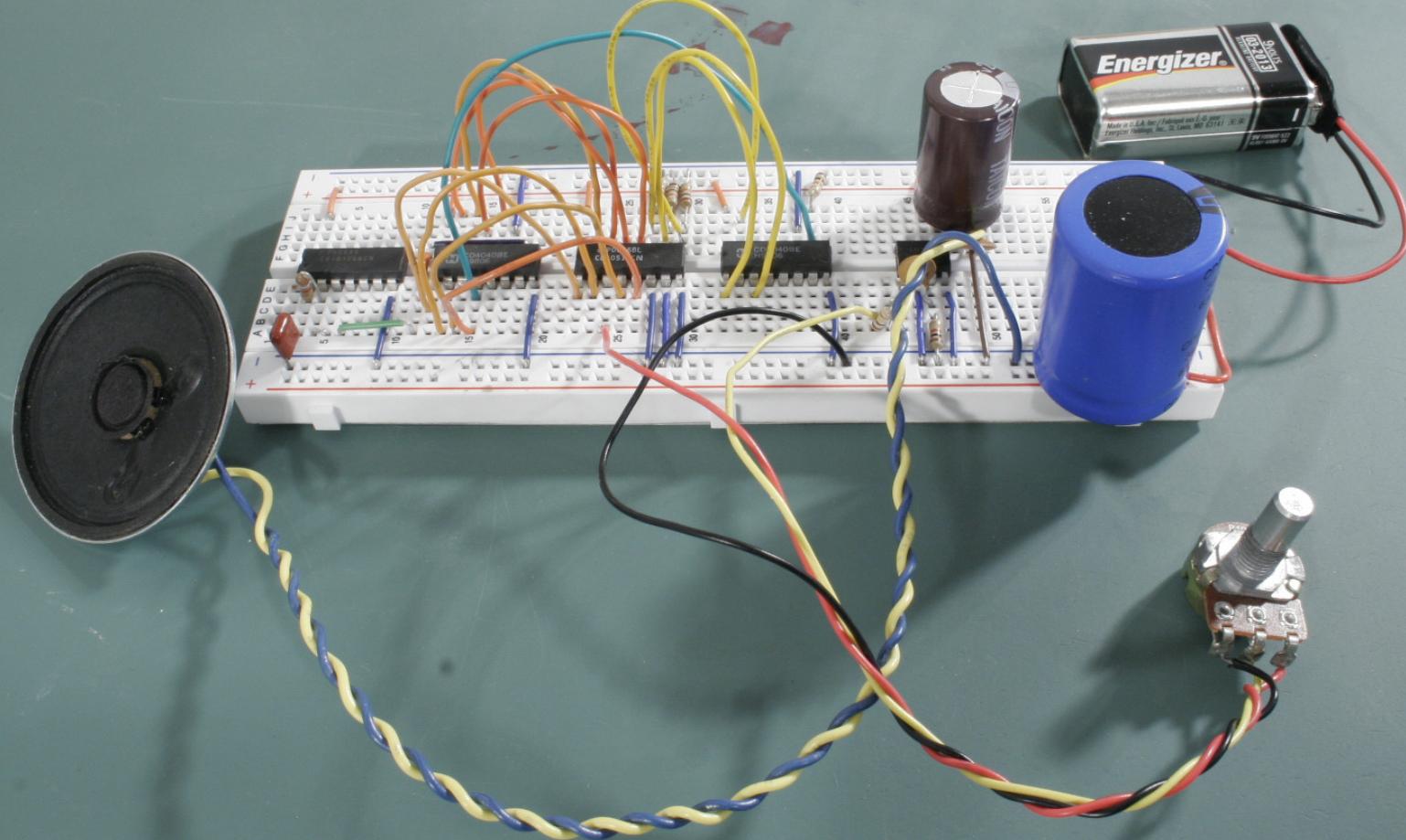


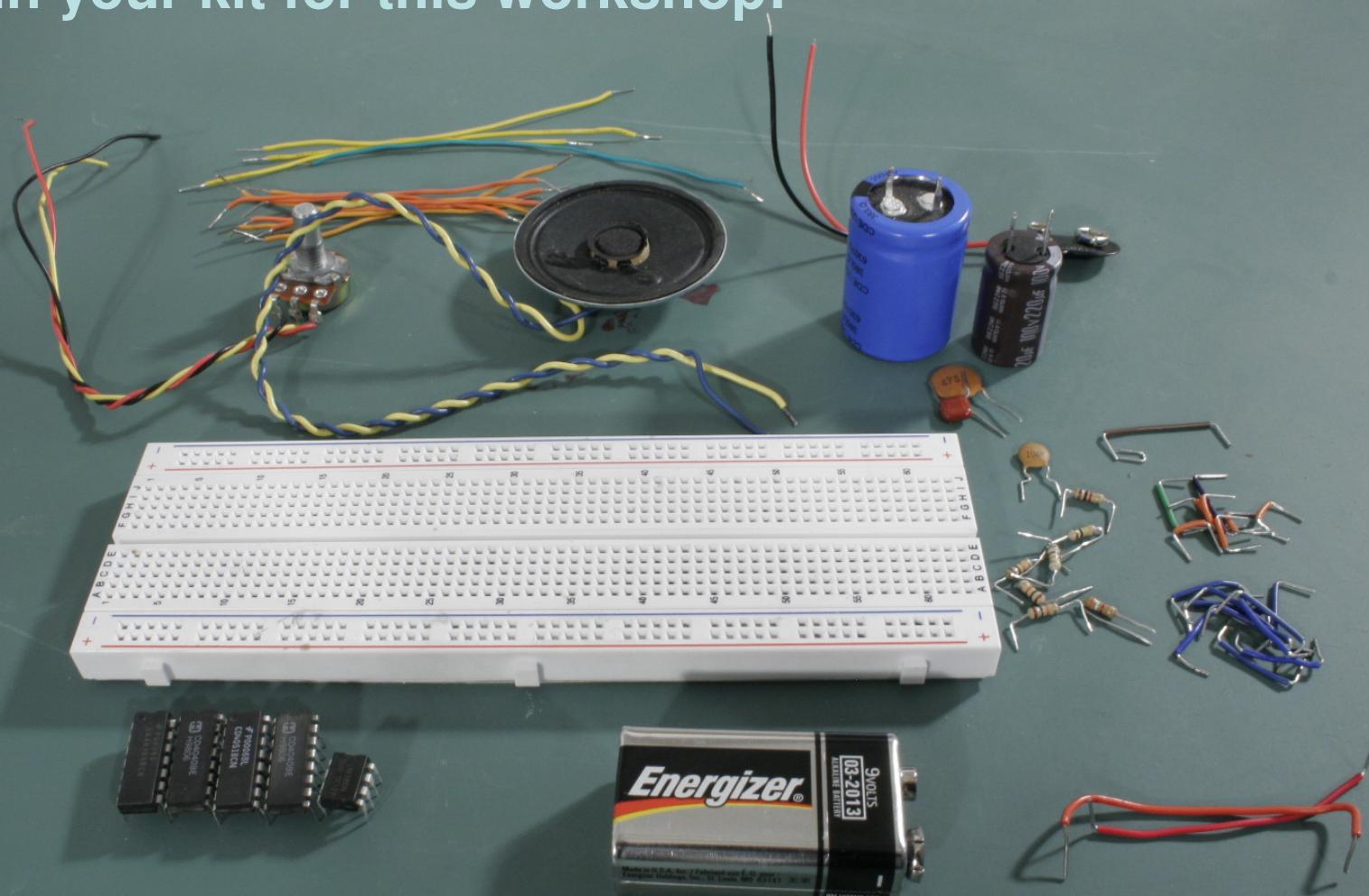
Welcome to the CMOS Music I – 1 bit synthesizer workshop!




Parts in your kit for this workshop:




Breadboard

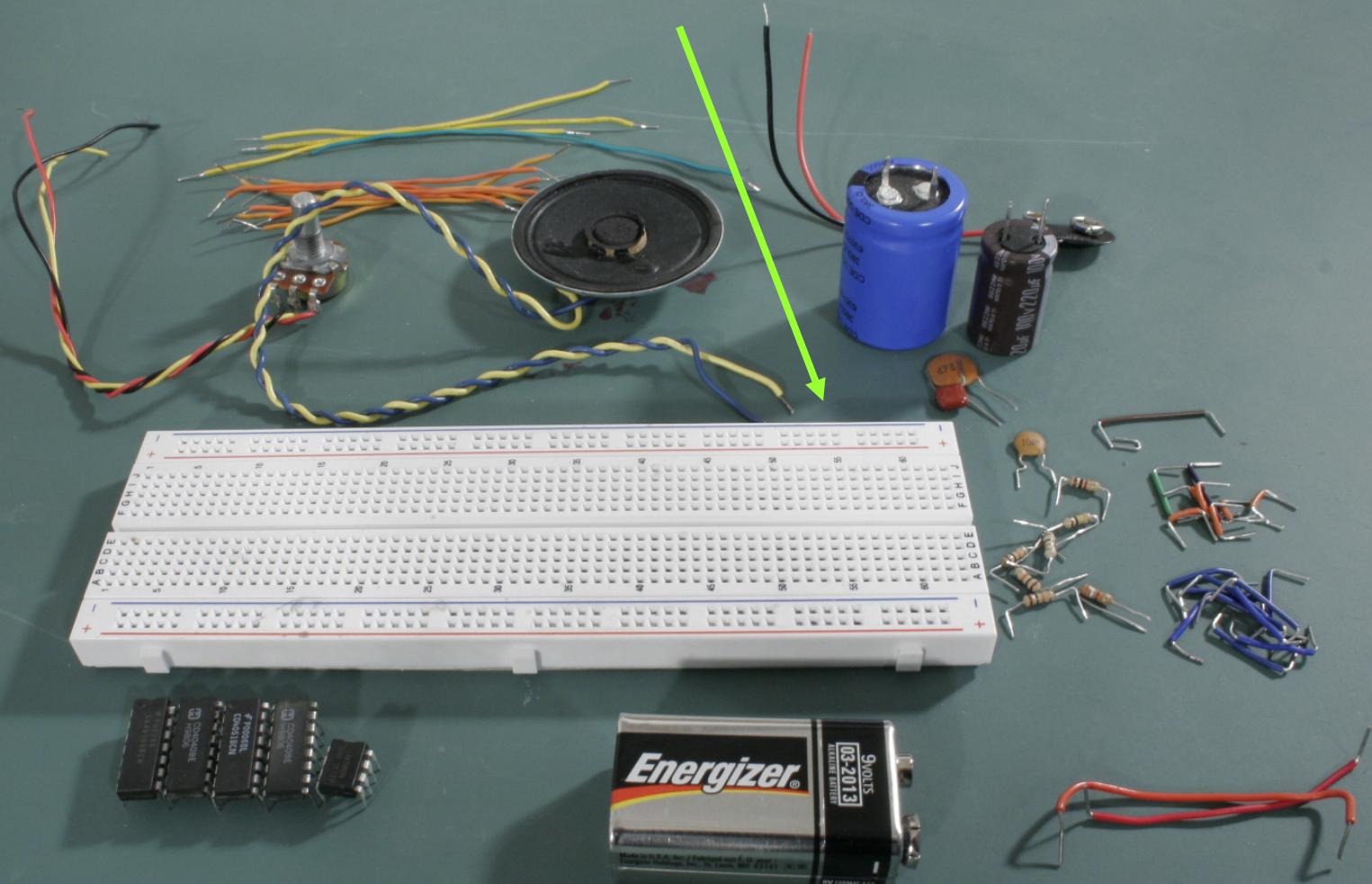


Jumpers

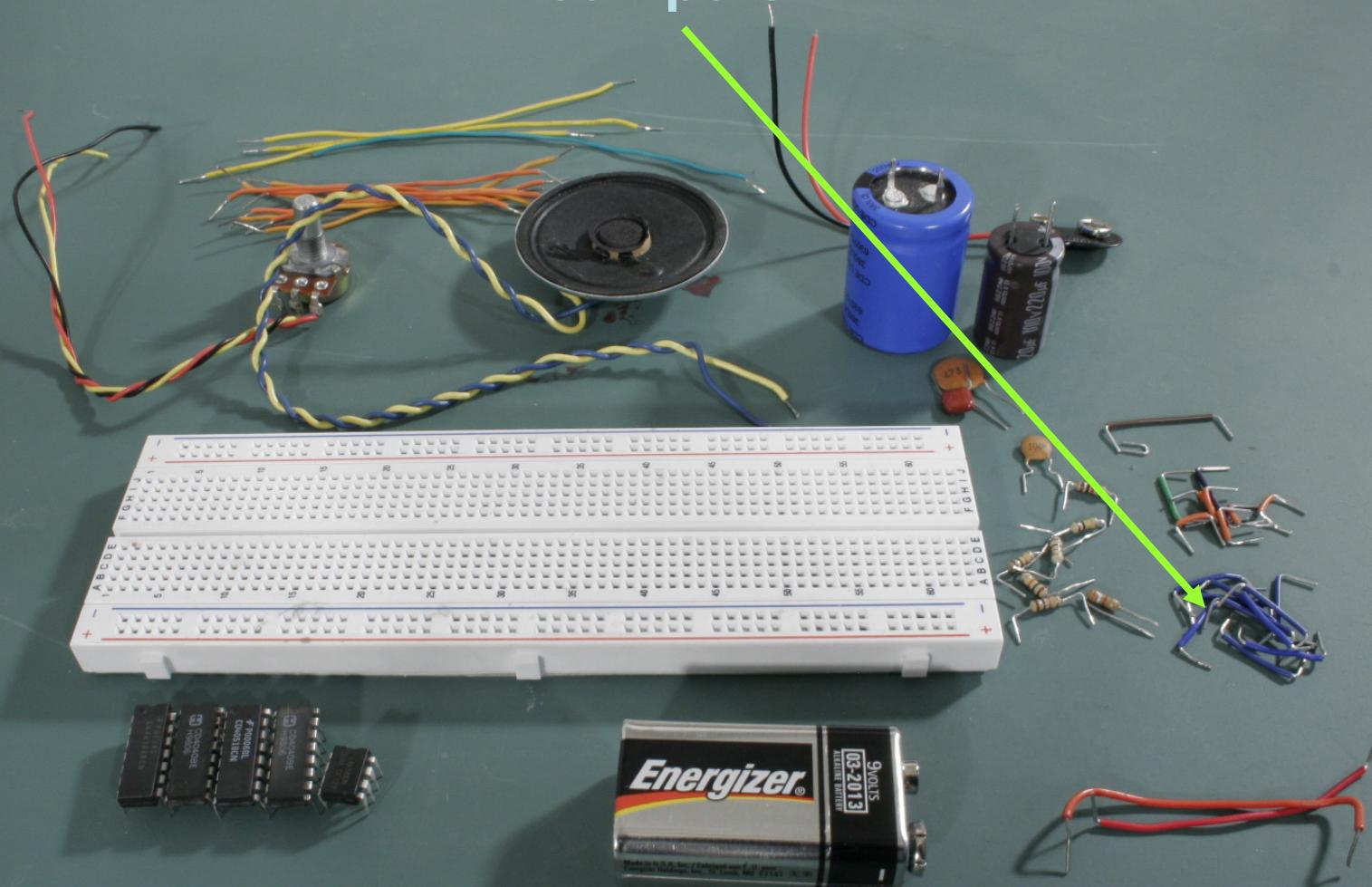


Jumpers

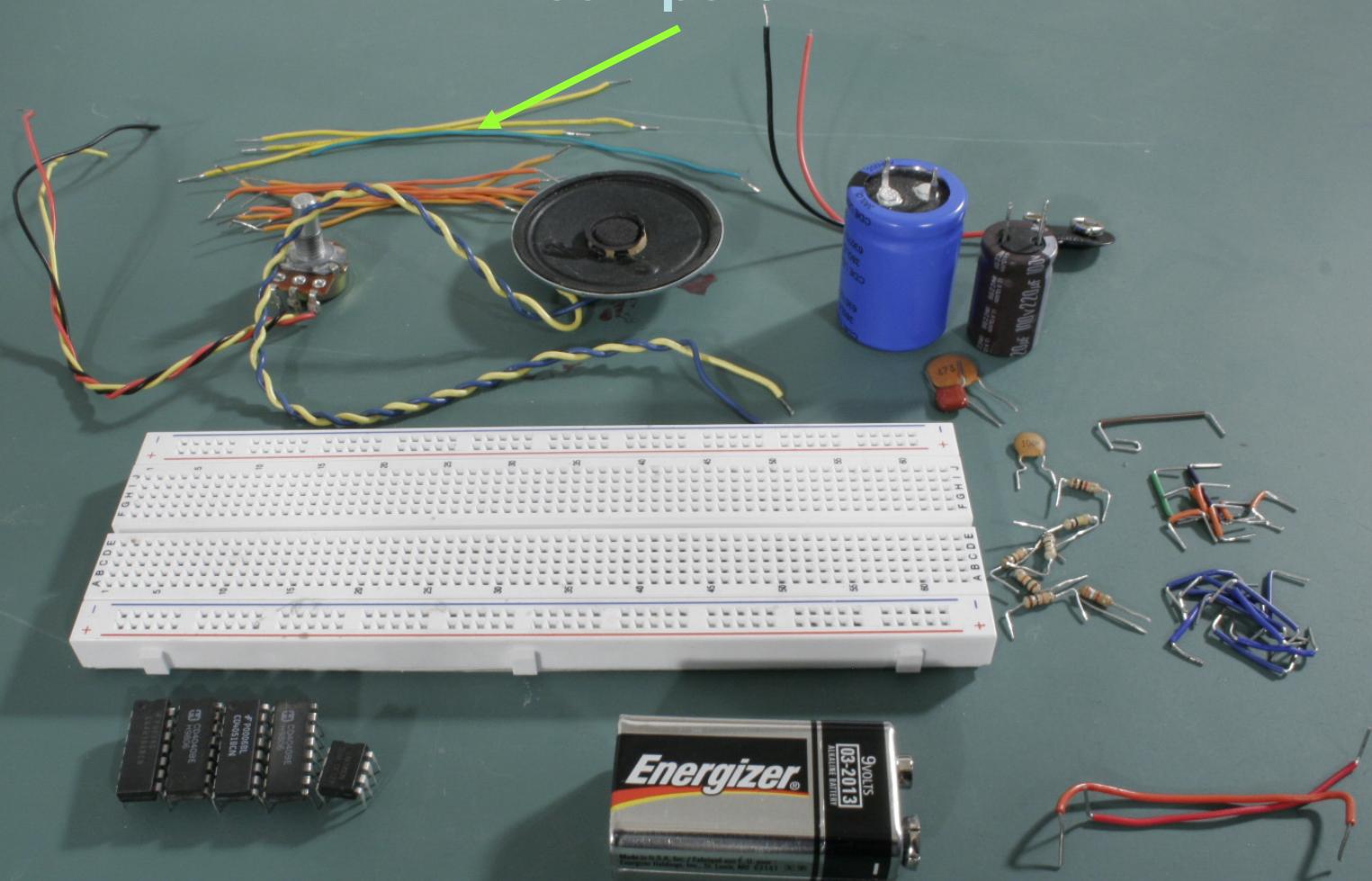


Capacitors

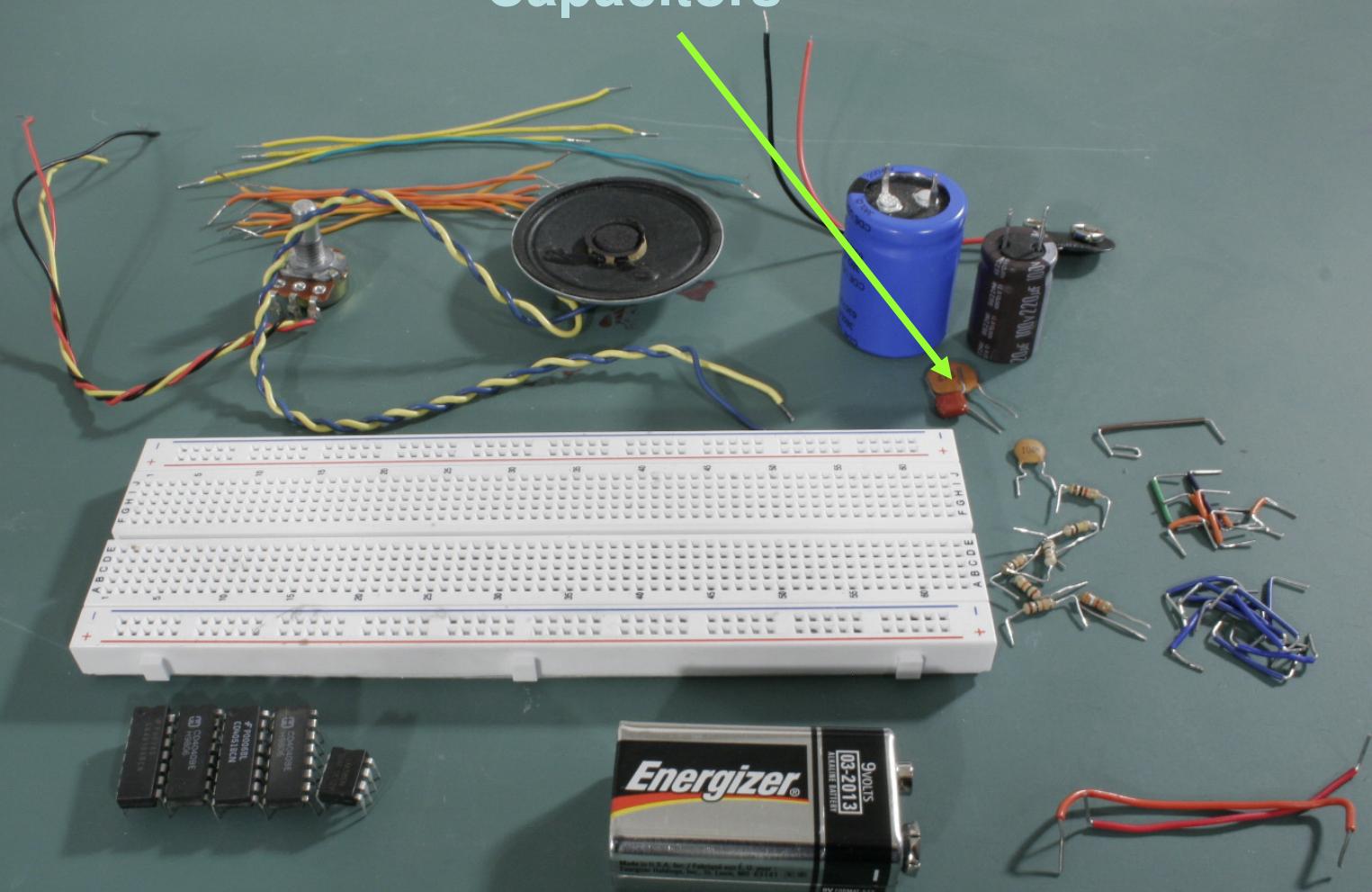


Resistors

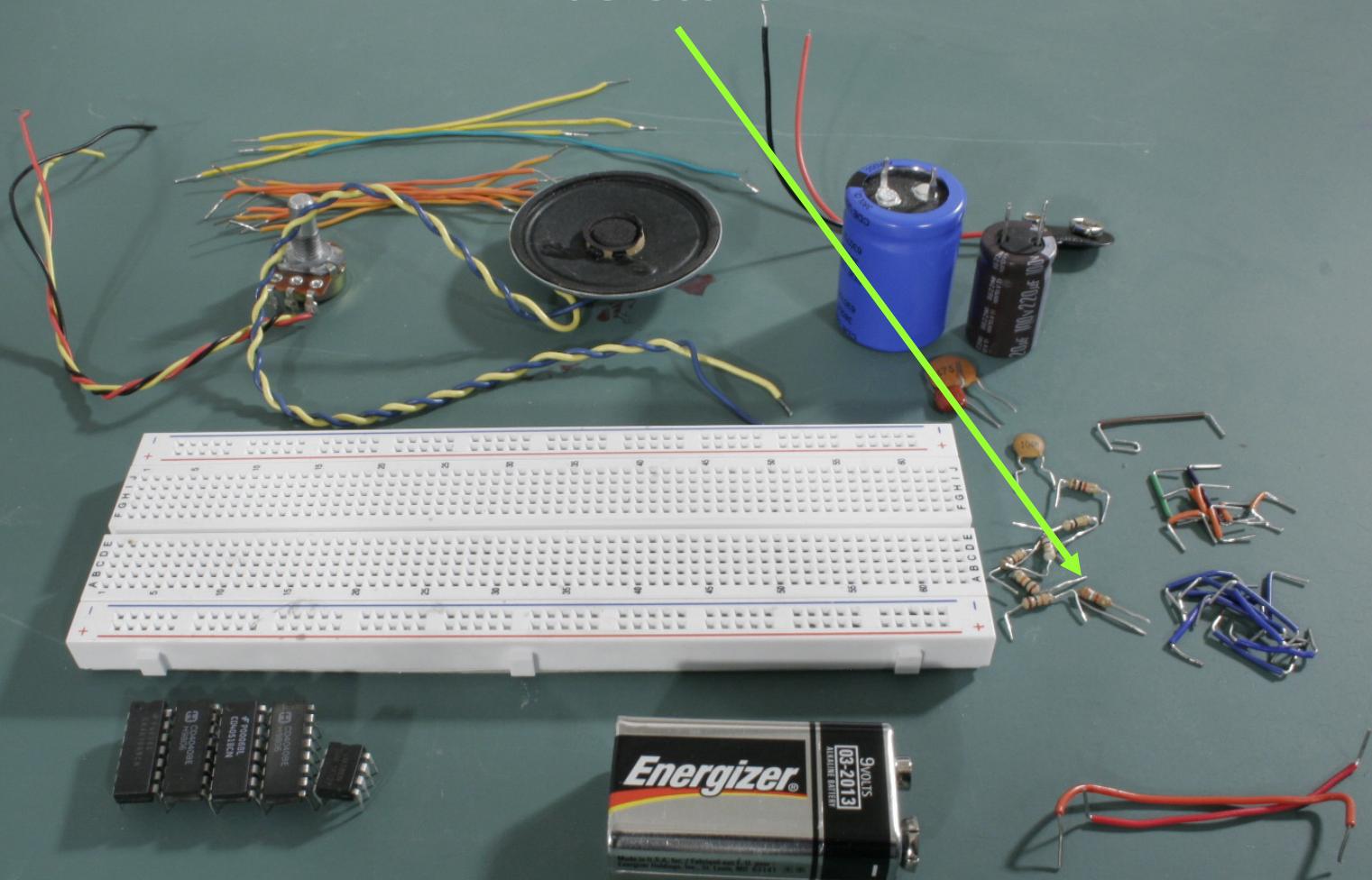


Integrated Circuits

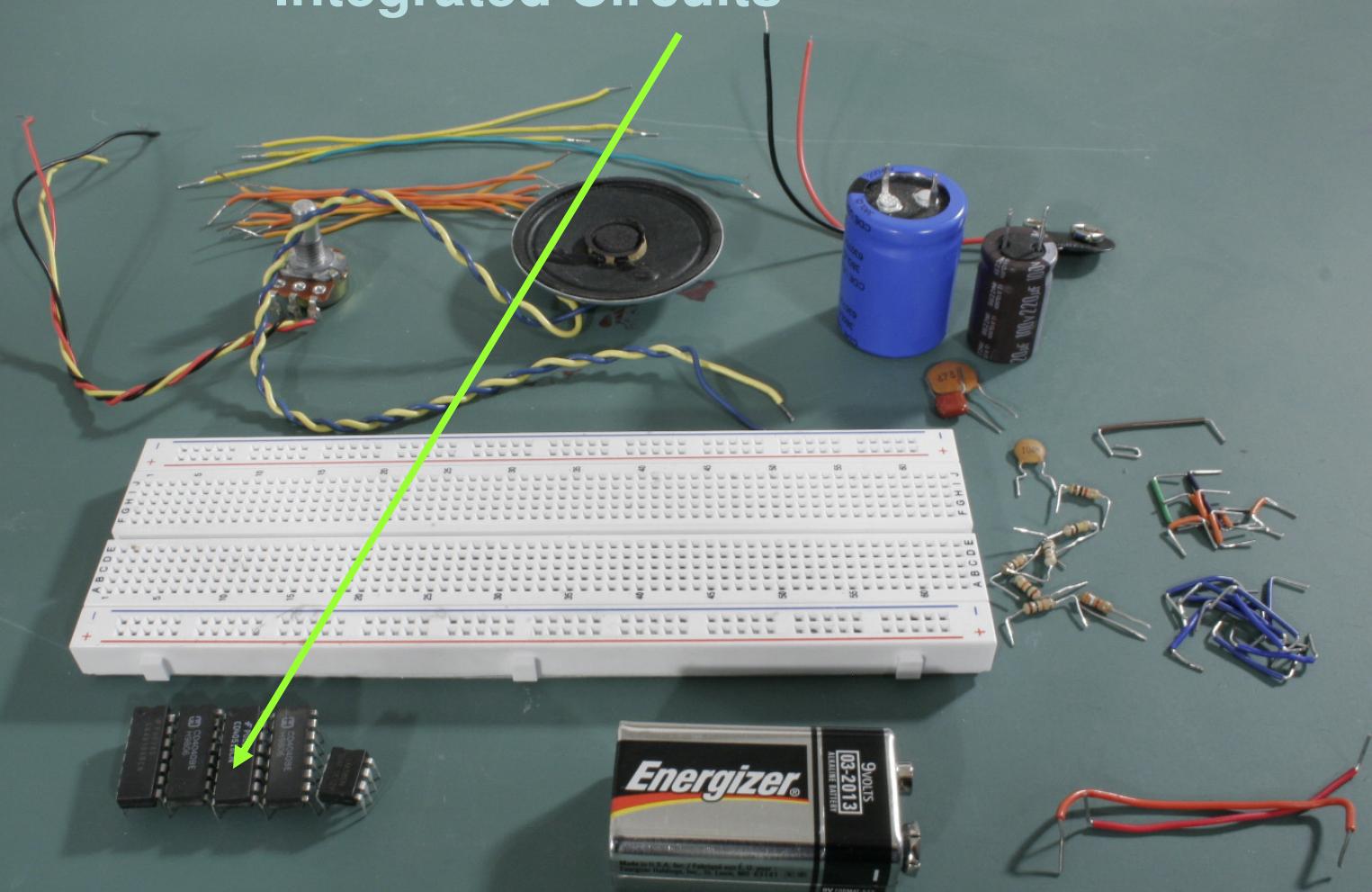


Potentiometer

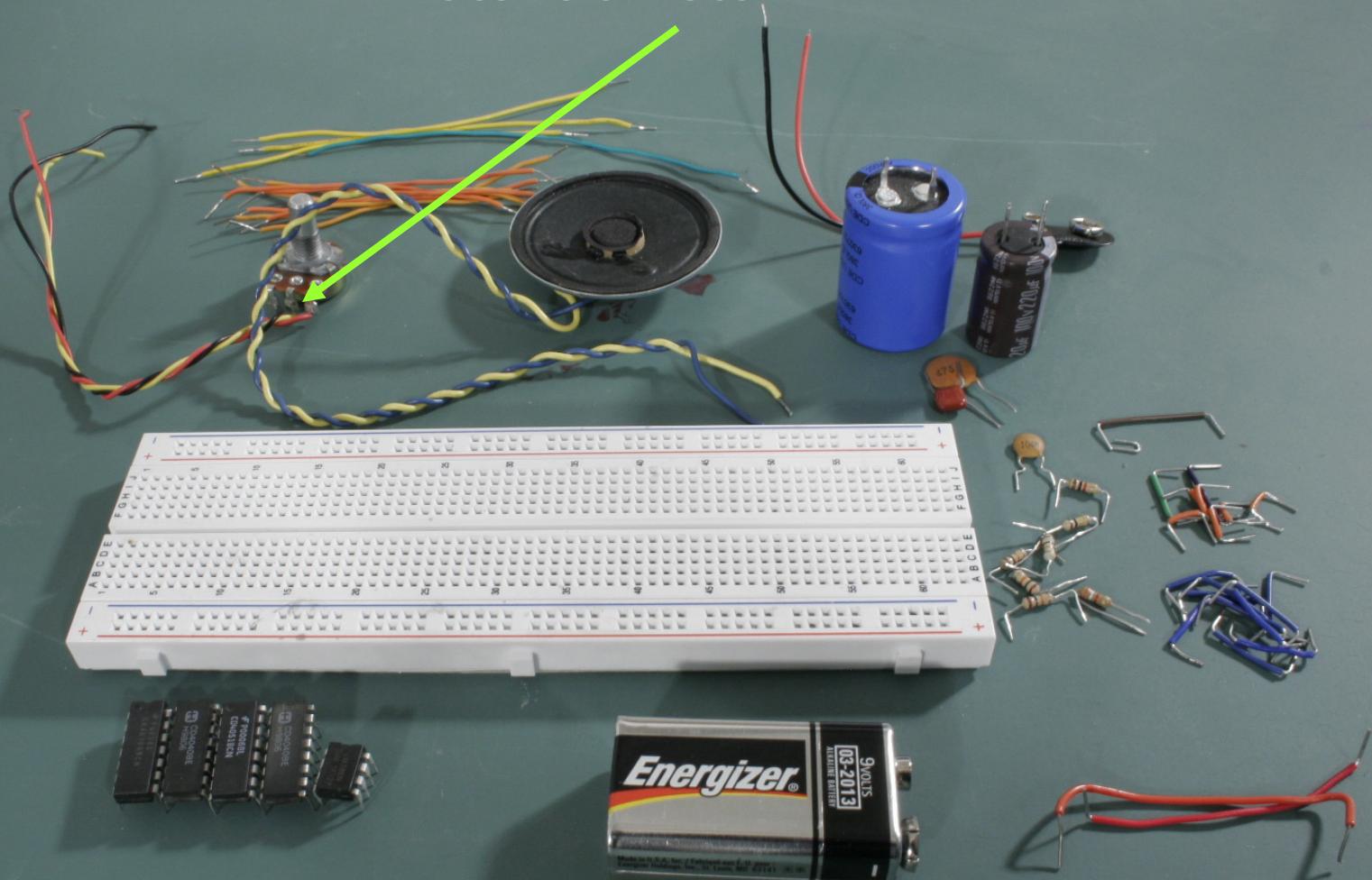


Speaker

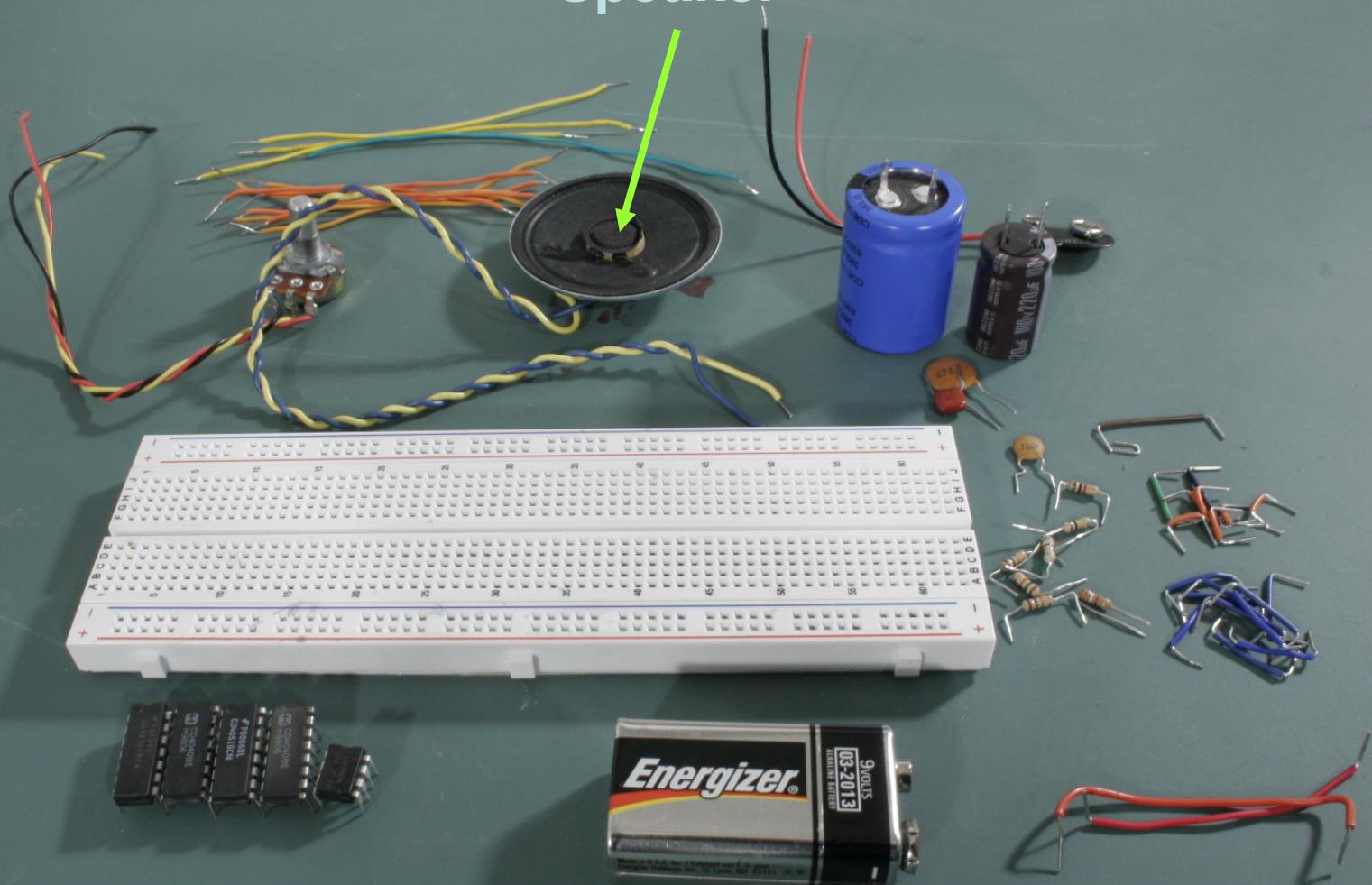


Battery Clip

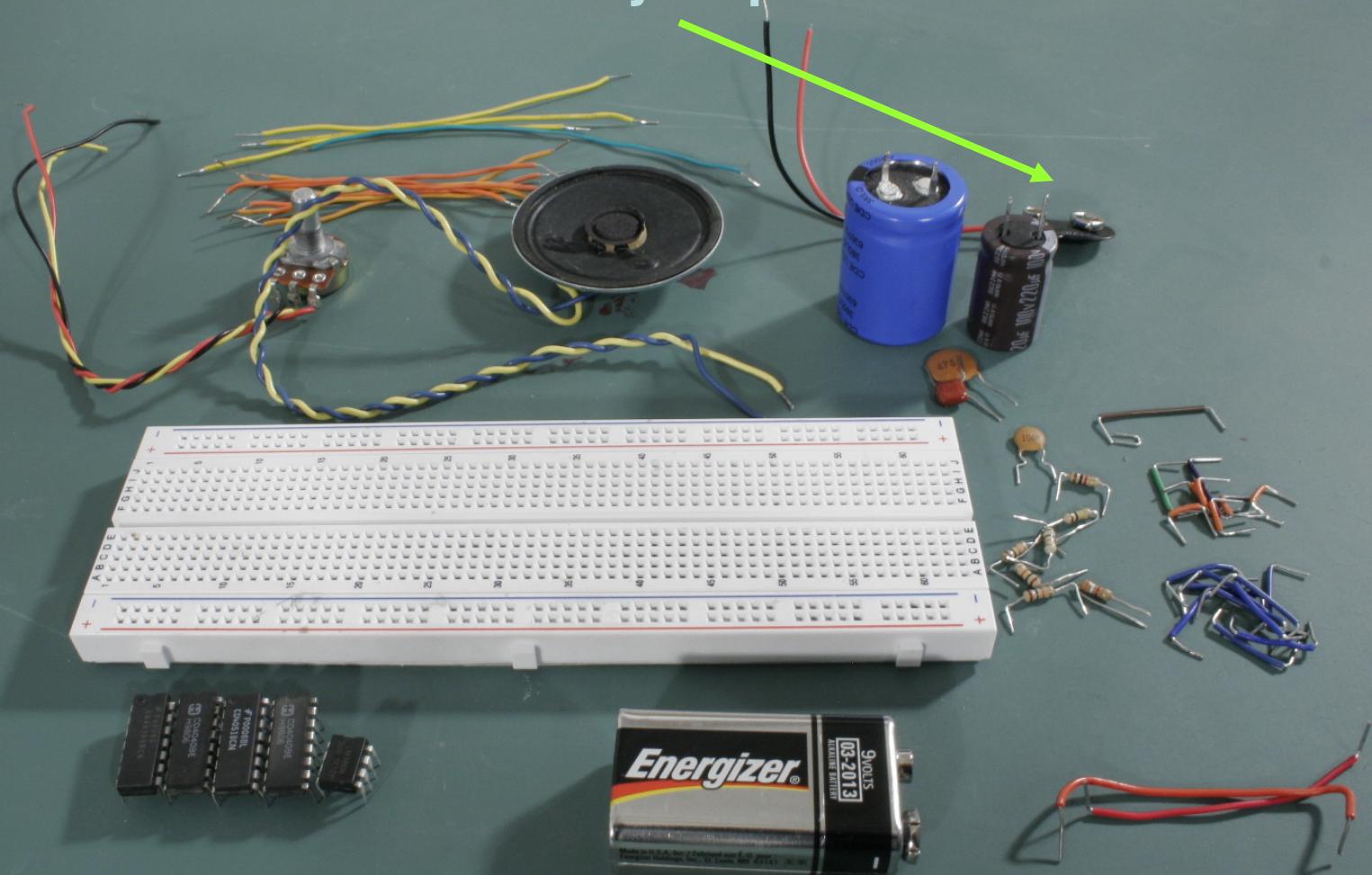


Battery

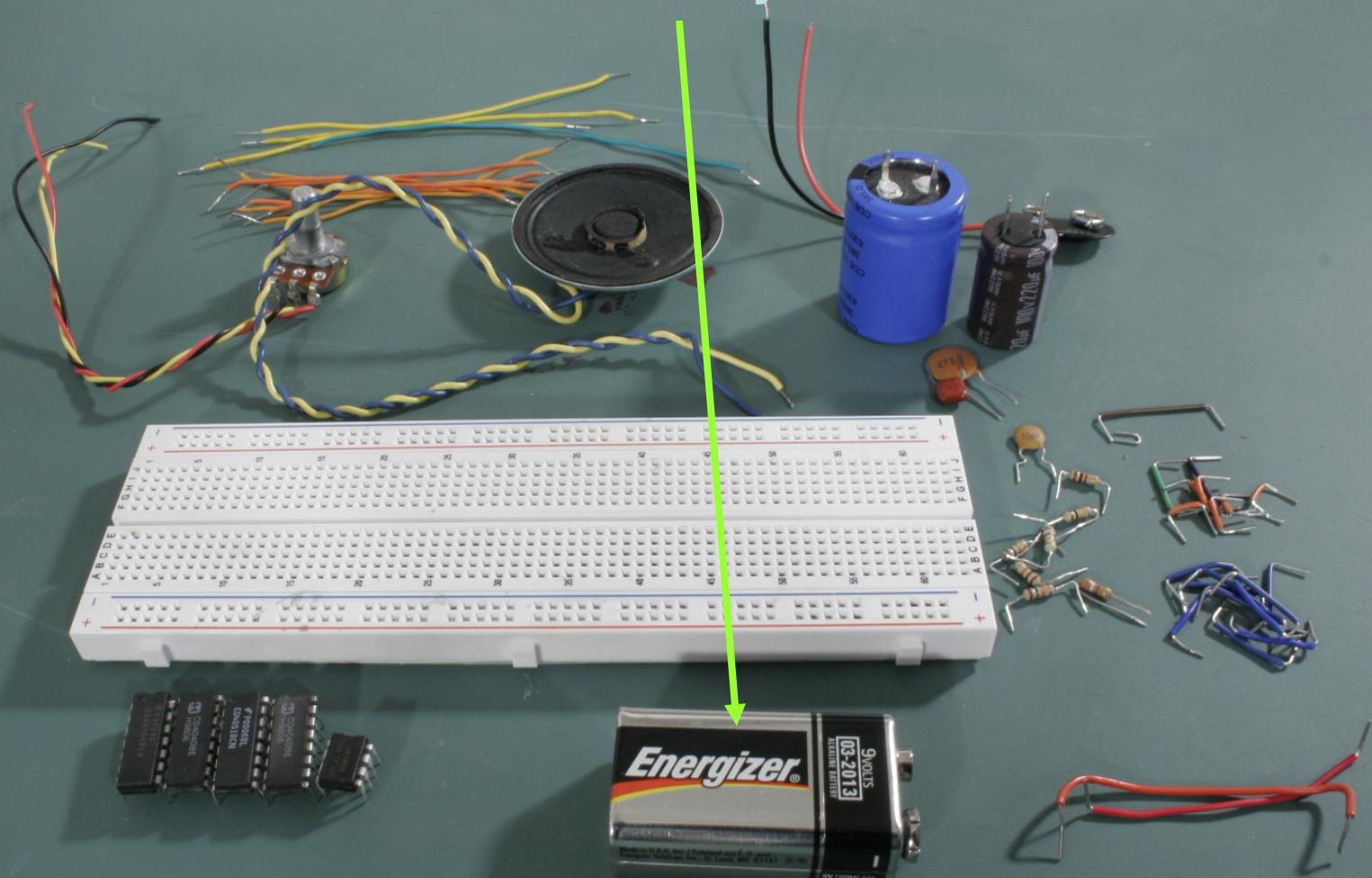

Parts	Quantity
Breadboard + Jumpers	1 (800+contacts) + 1 kit
Wire (24 AWG stranded)	3 different colors 16" each
9 volt Battery	1
Battery Clip	1
Speaker (8 ohm)	1
1k ohm resistor	1
10k ohm resistor	4
100k ohm resistor	1
100k ohm potentiometer	1
3.9k ohm resistor	1
CD40106 (IC)	1
CD4051 (IC)	1
CD4040 (IC)	2
LM386 (IC)	1
1500pF or .0015 uF Capacitor	1
.047 uF Capacitor	1
.1 uF Capacitor	1
220 uF Capacitor	1

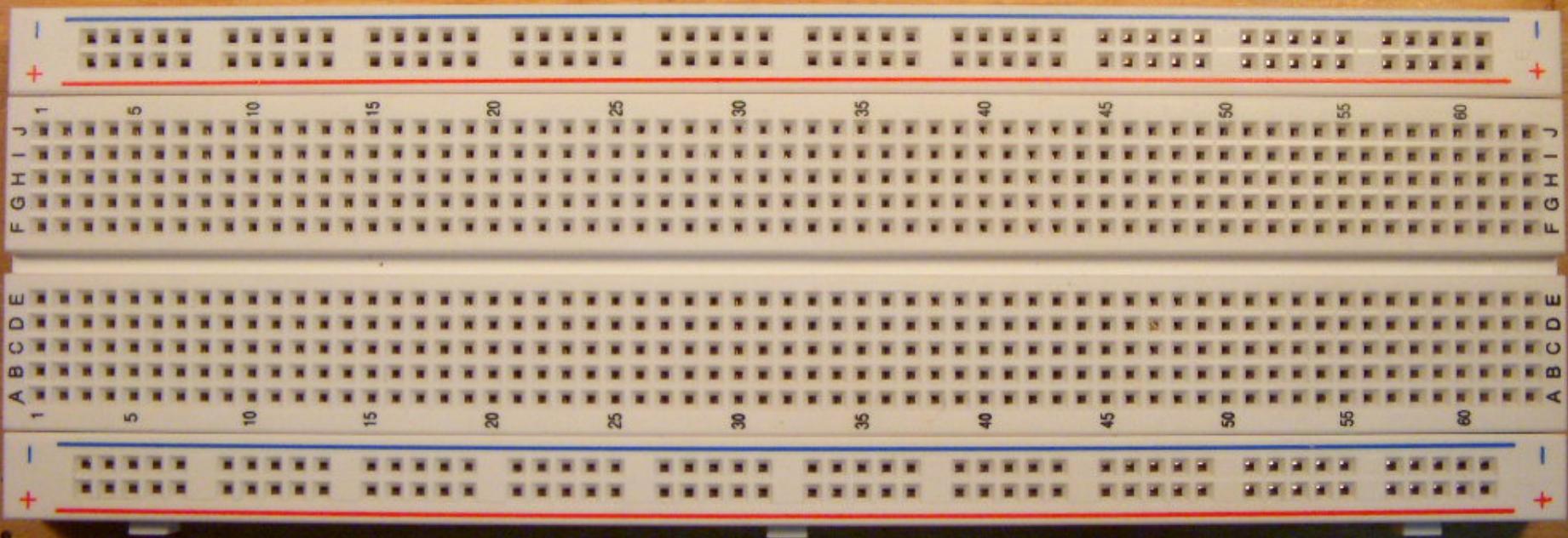


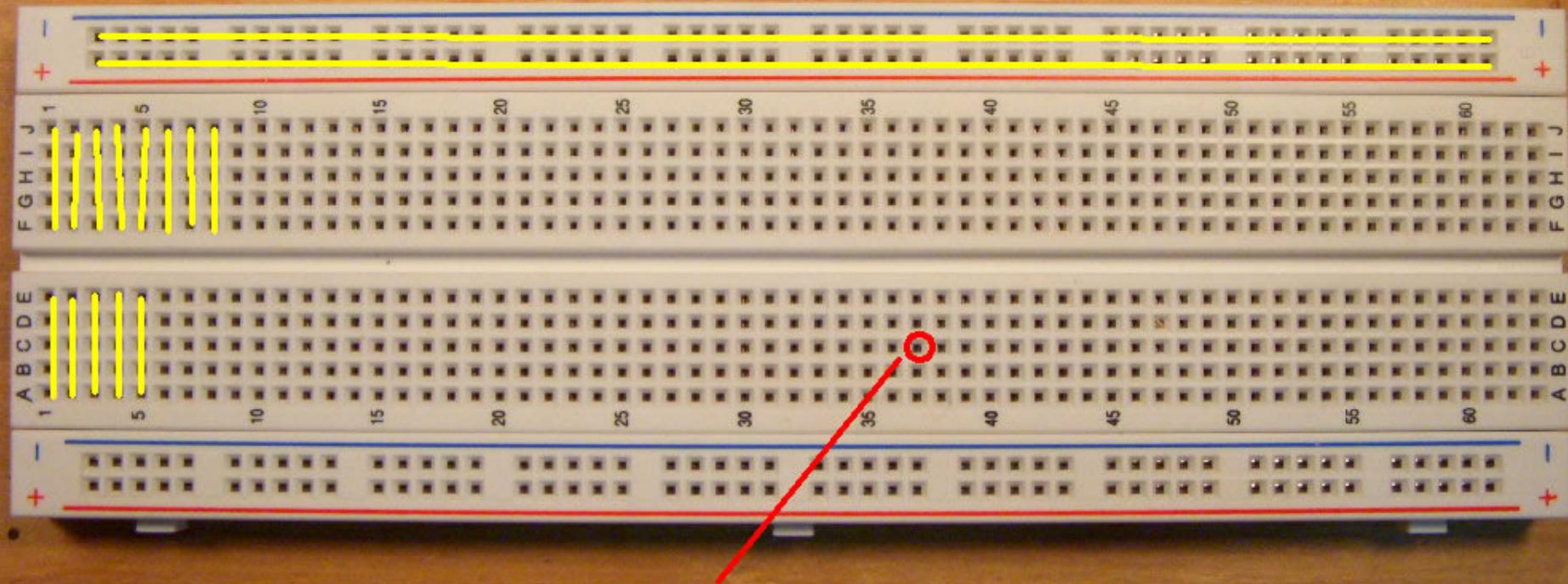Bread boards contain hundreds of contact points. Each point is connected to other points in rows and columns via strips of metal indicated by the yellow lines below.




Each point has an alpha numeric coordinate.
This point is C-37 -- column C, row 37.

Place the 40106 on the breadboard

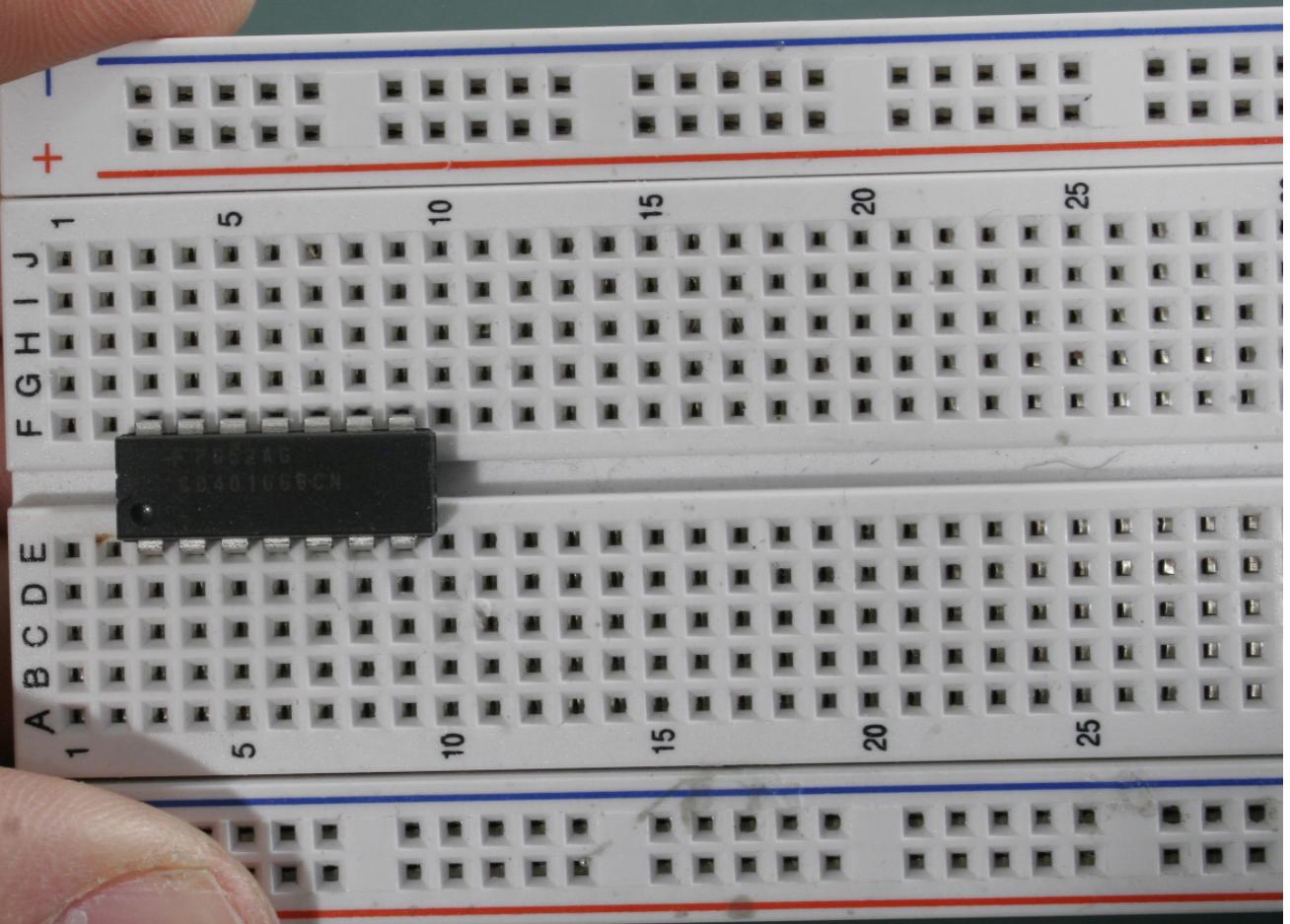

Notch to the left side

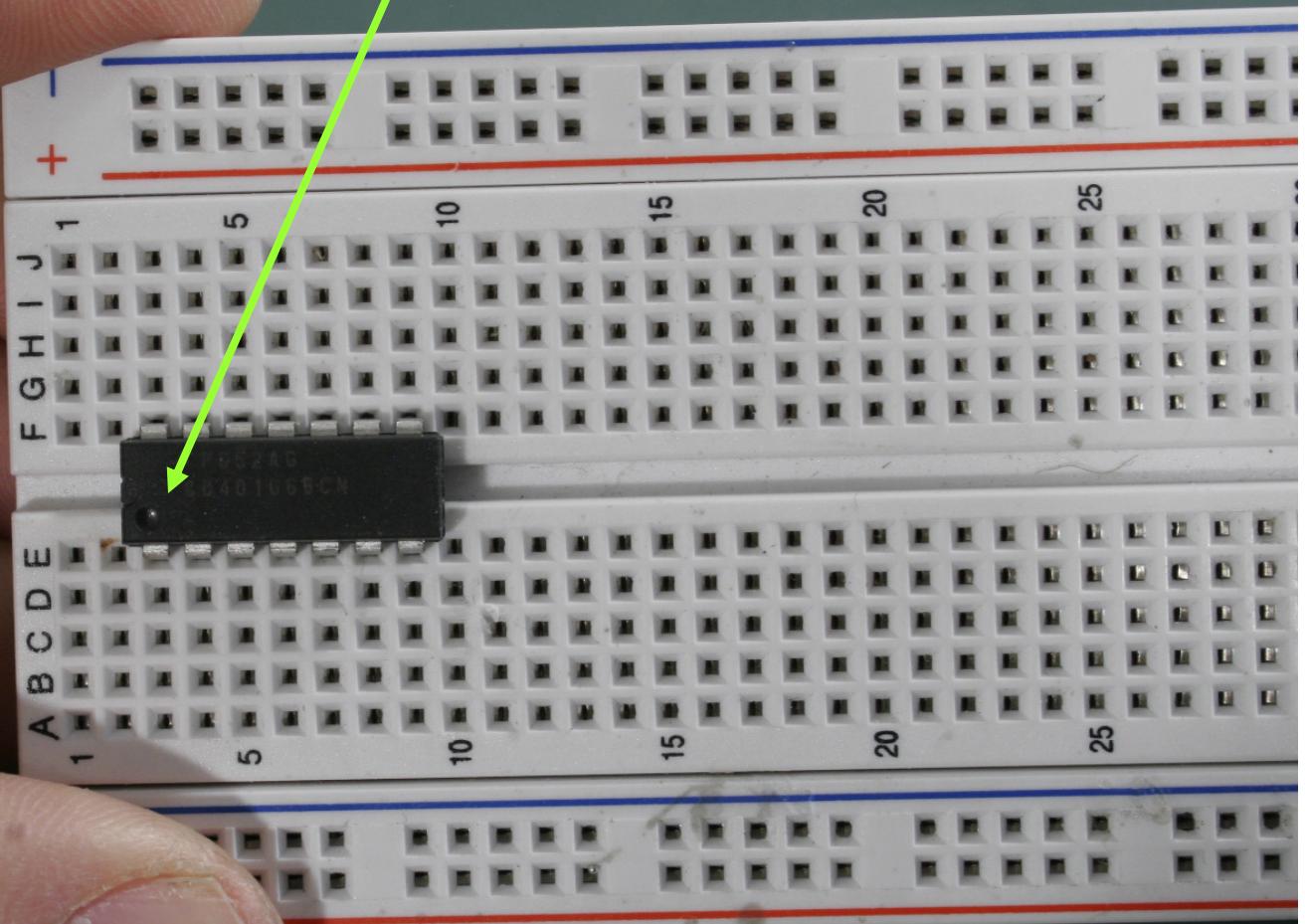


Notch to the left side

Pin 1 to row 3, column E

Notch to the left side

Pin 7

Pin 1

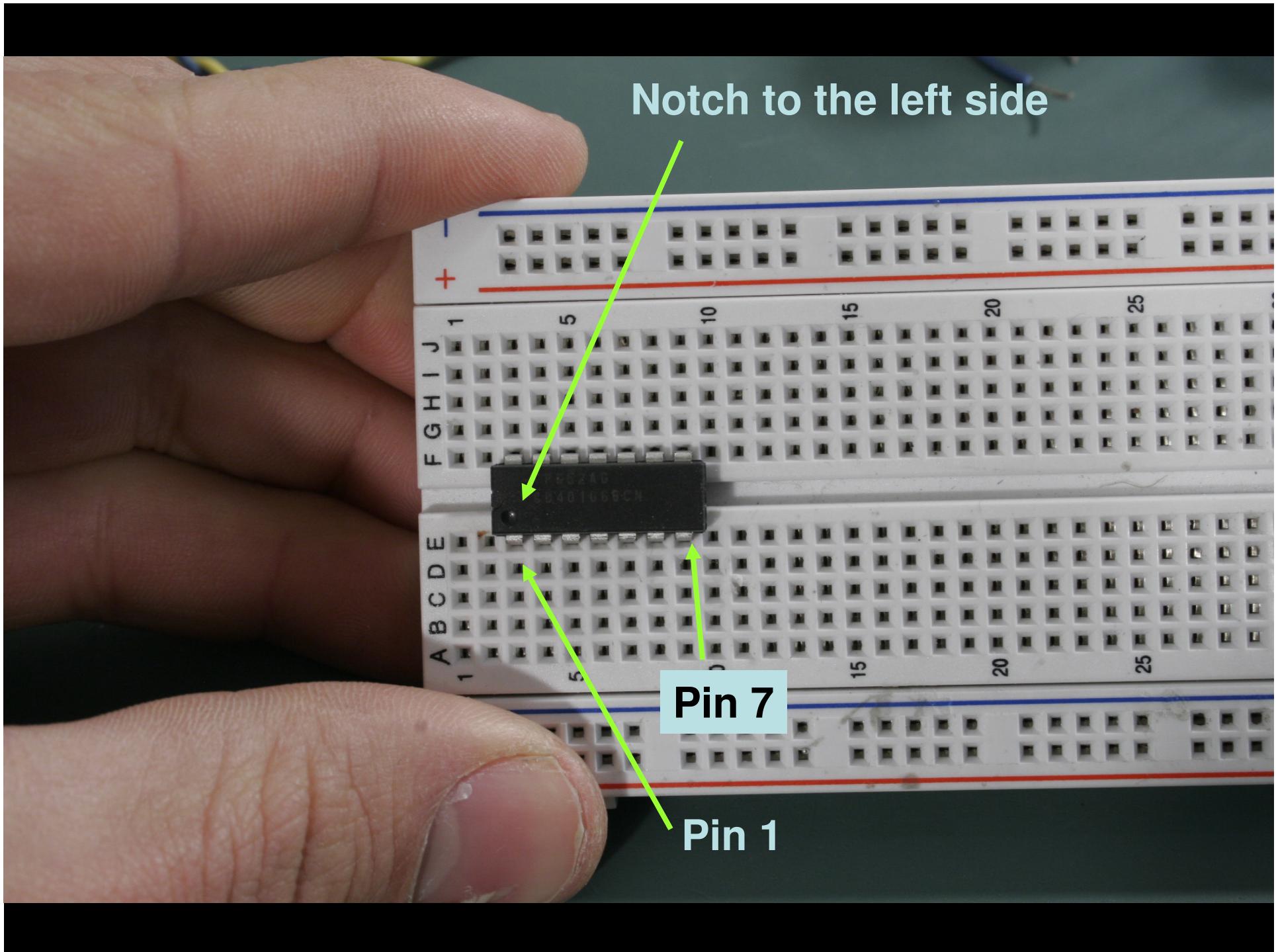


Notch to the left side

Pin 8

Pin 7

Pin 1

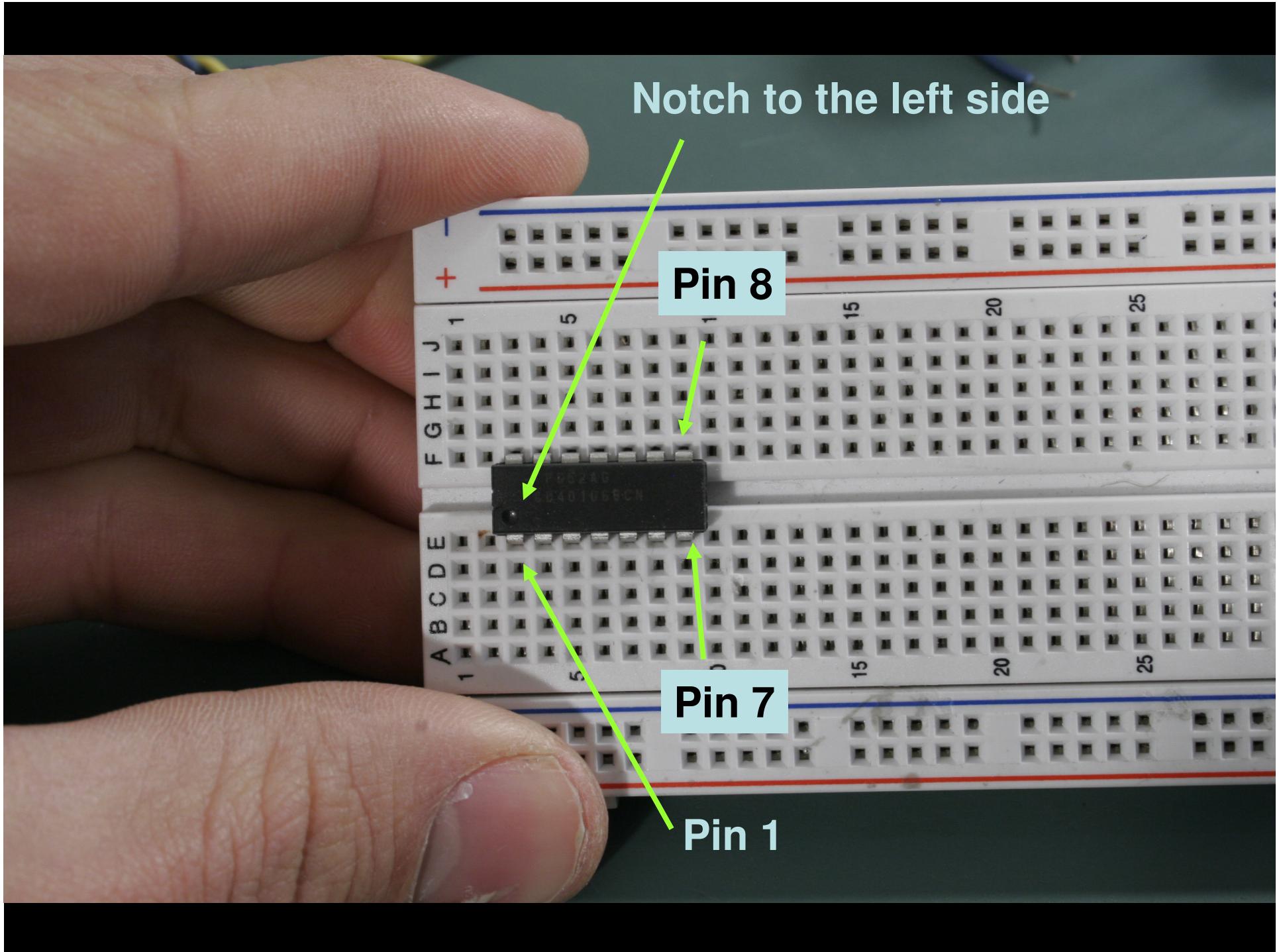


Notch to the left side

Pin 14


Pin 8

Pin 7


Pin 1

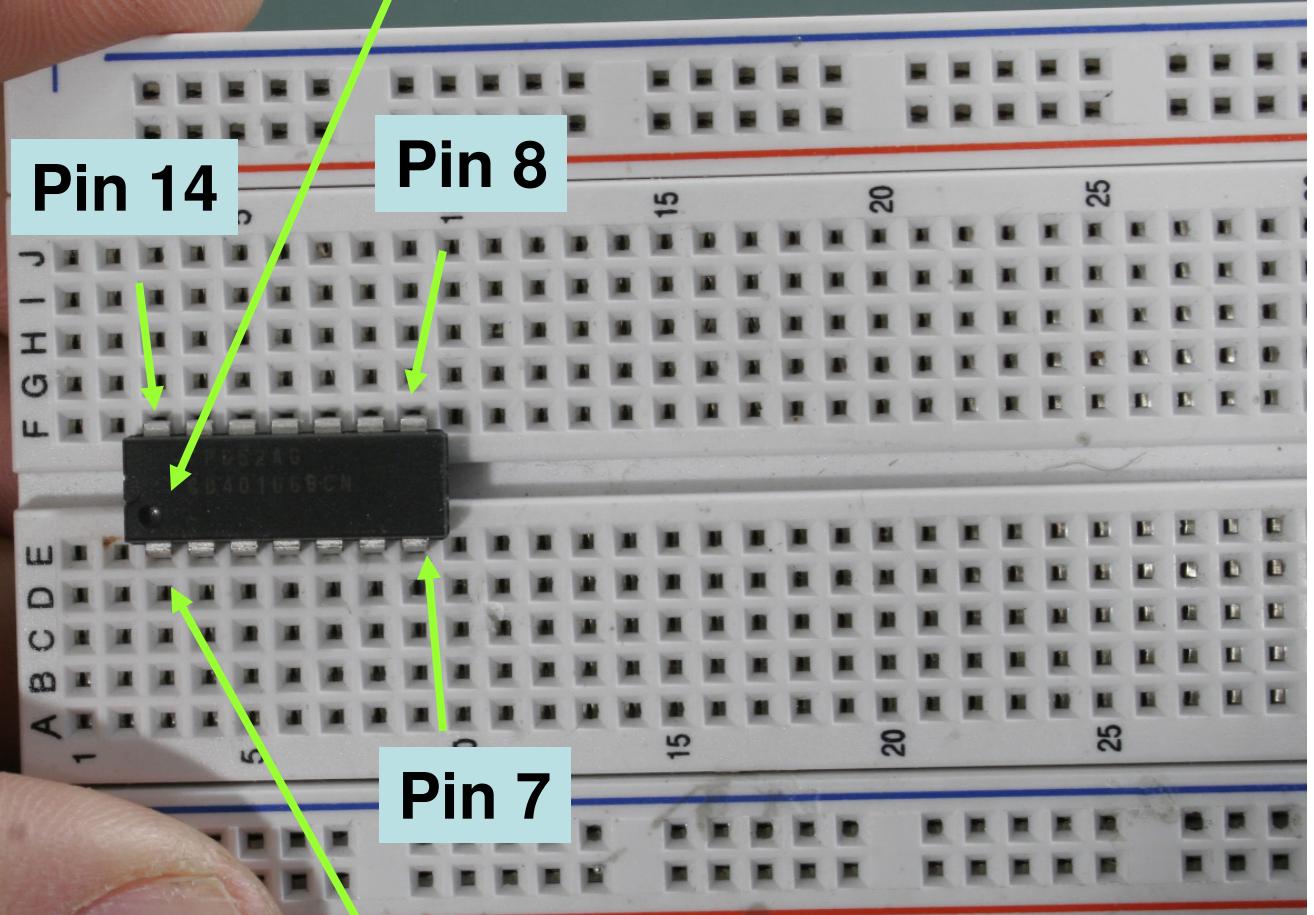

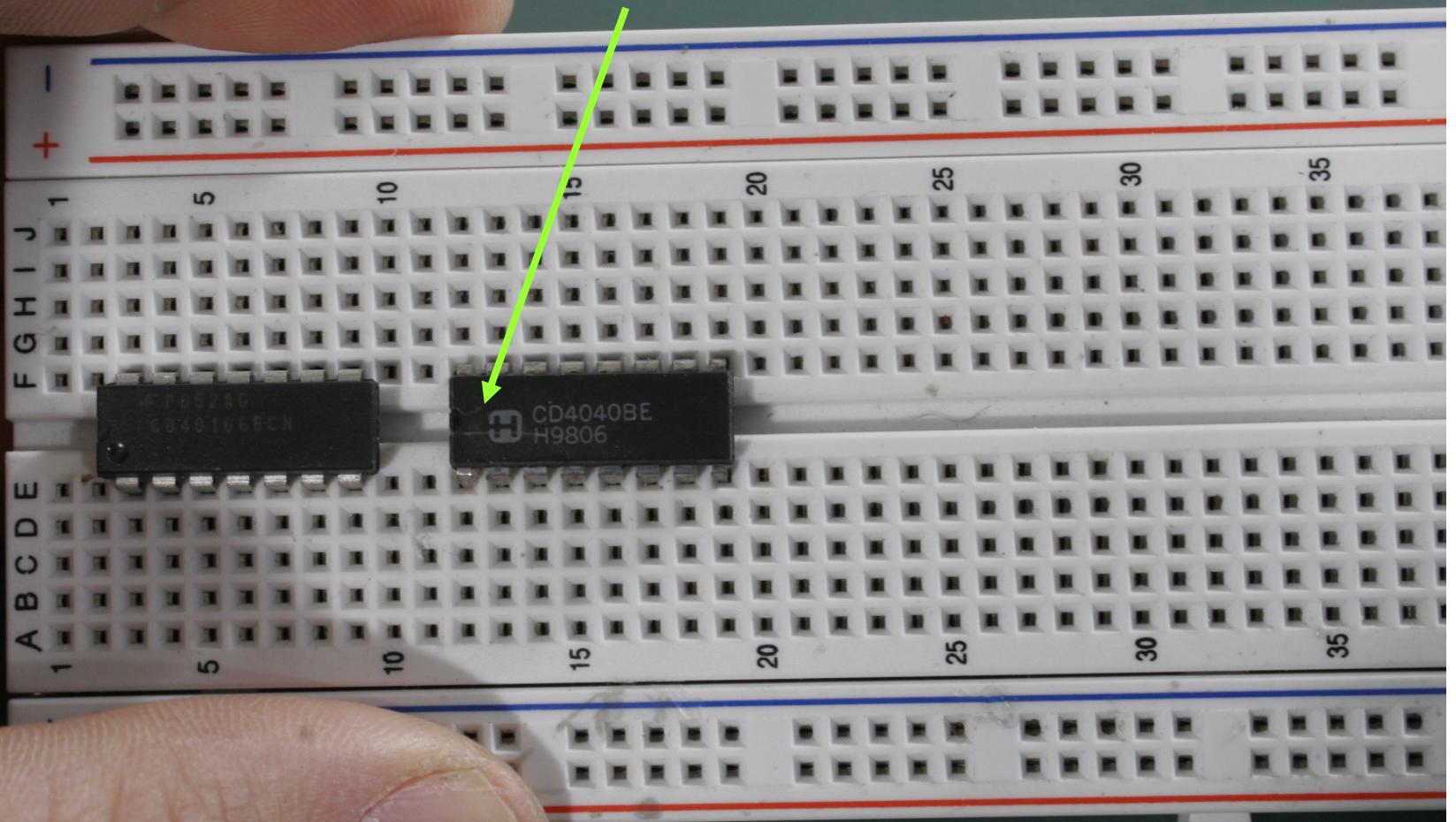
Place one 4040 on the breadboard with the notch to the left.



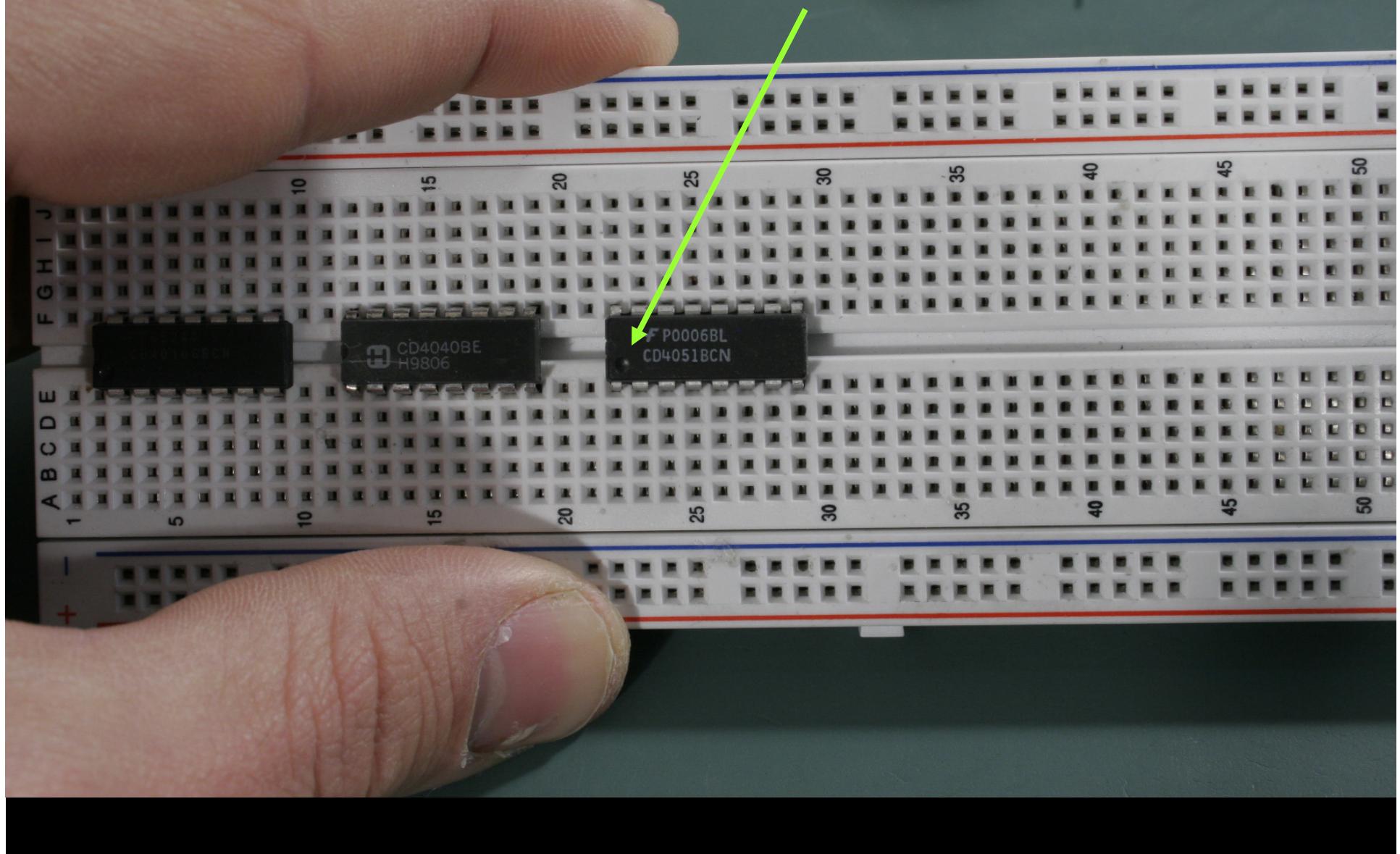
Place the 4051 on the breadboard
with the notch on the left side




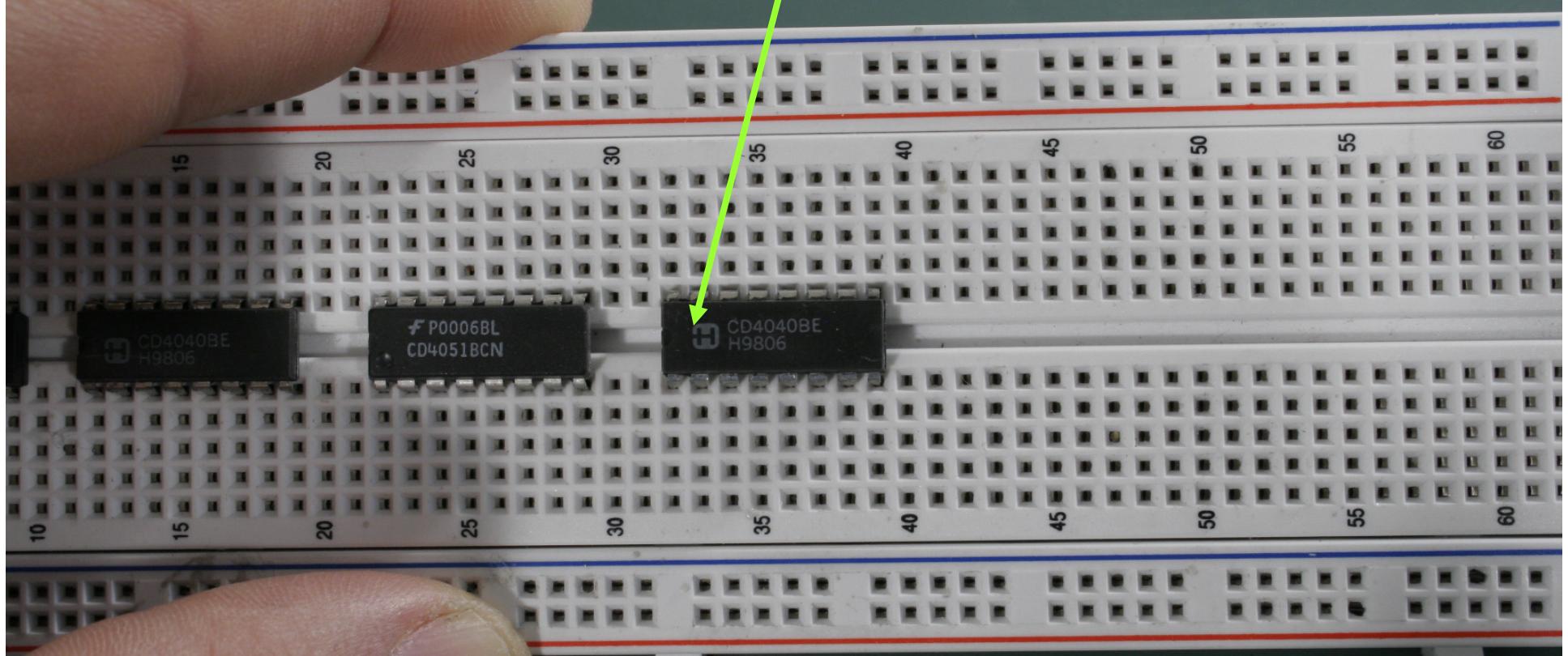
Place one 4040 on the breadboard
with the notch to the left.




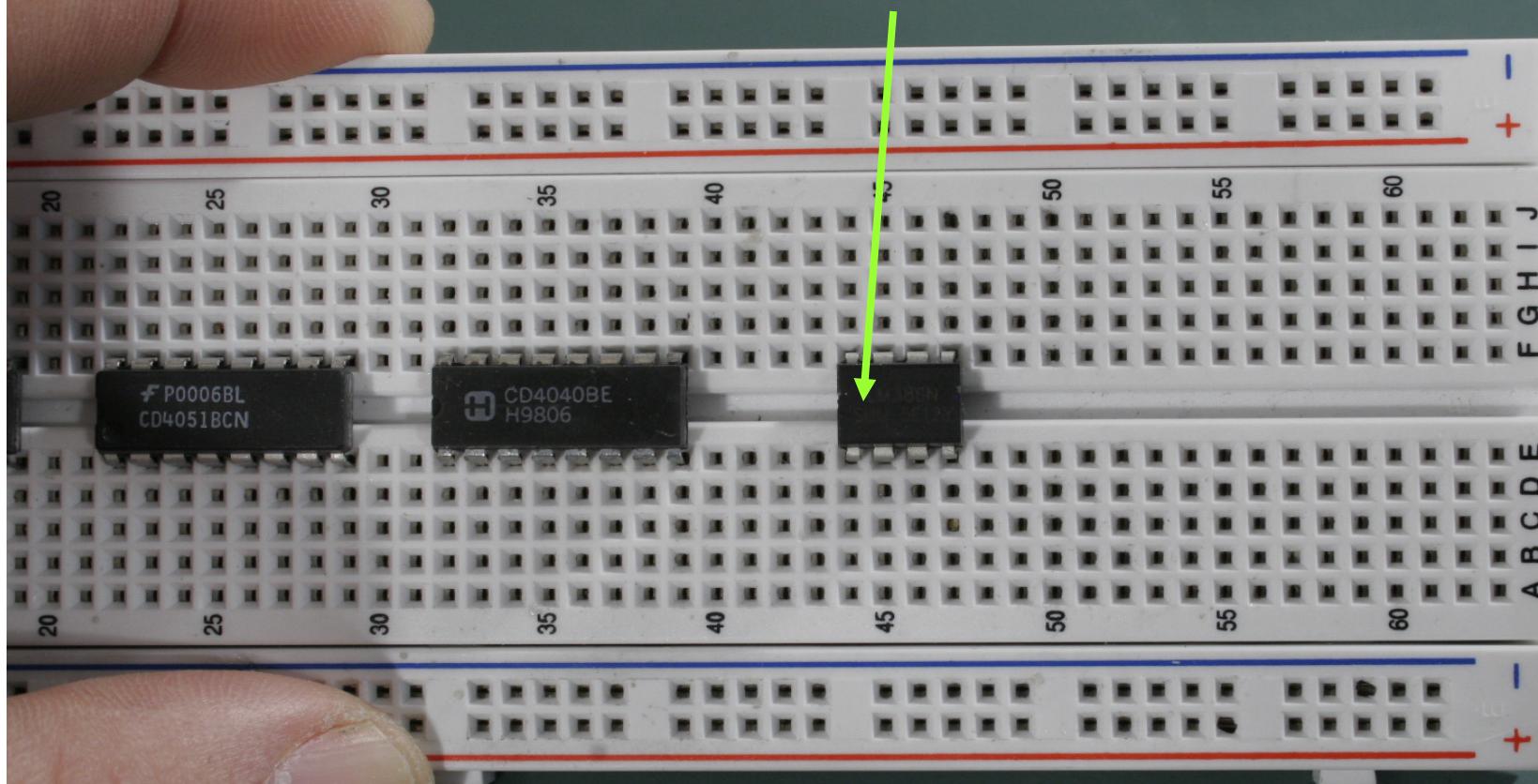Place one LM396 on the breadboard
with the notch to the left.




Connect the top and bottom power strips

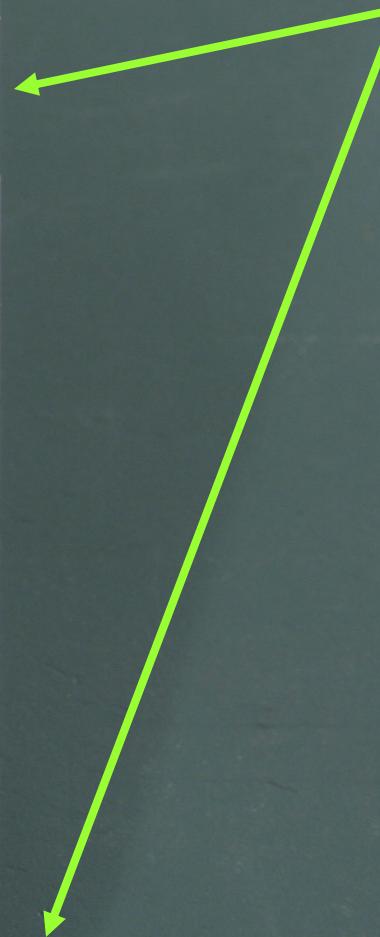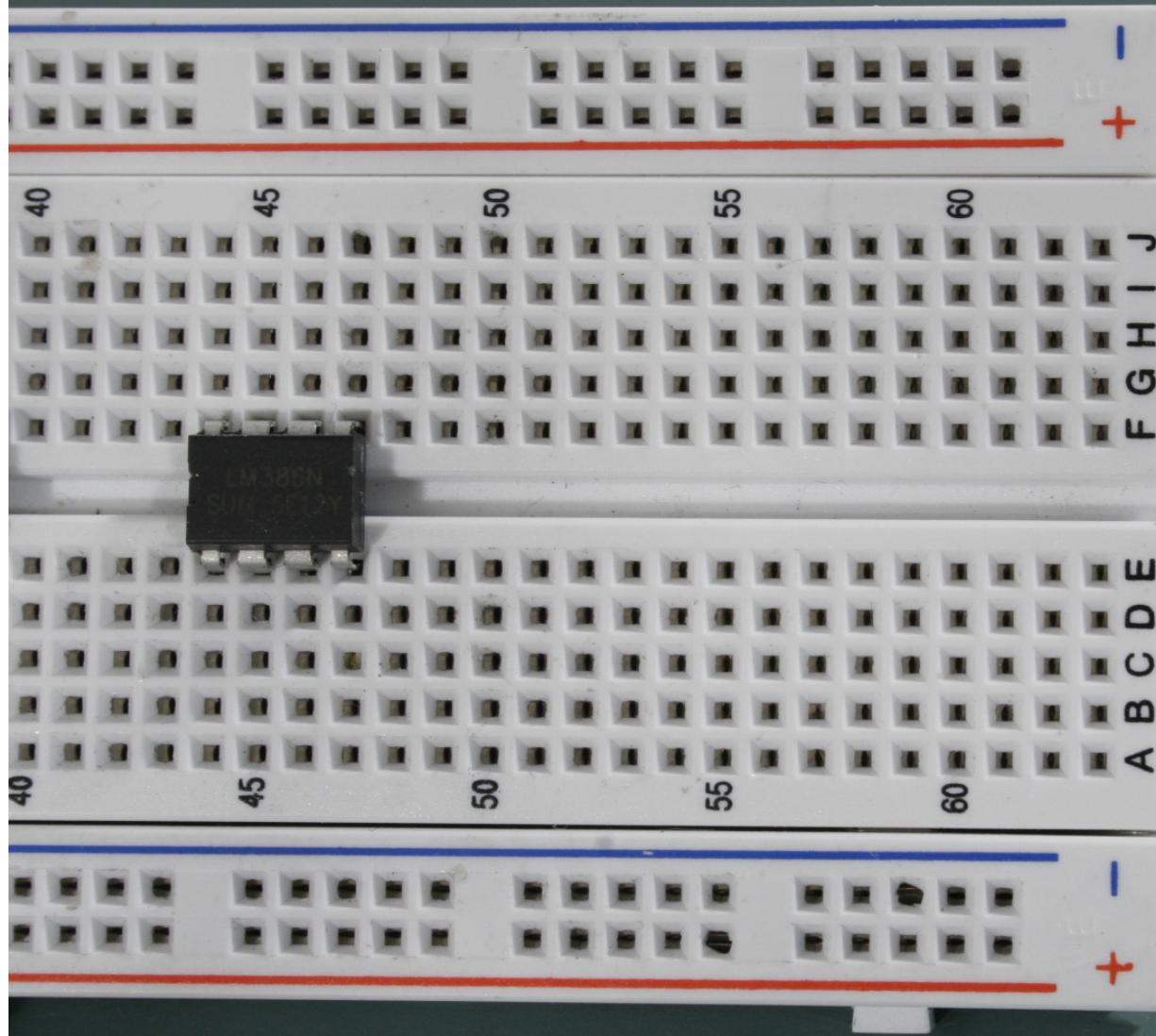


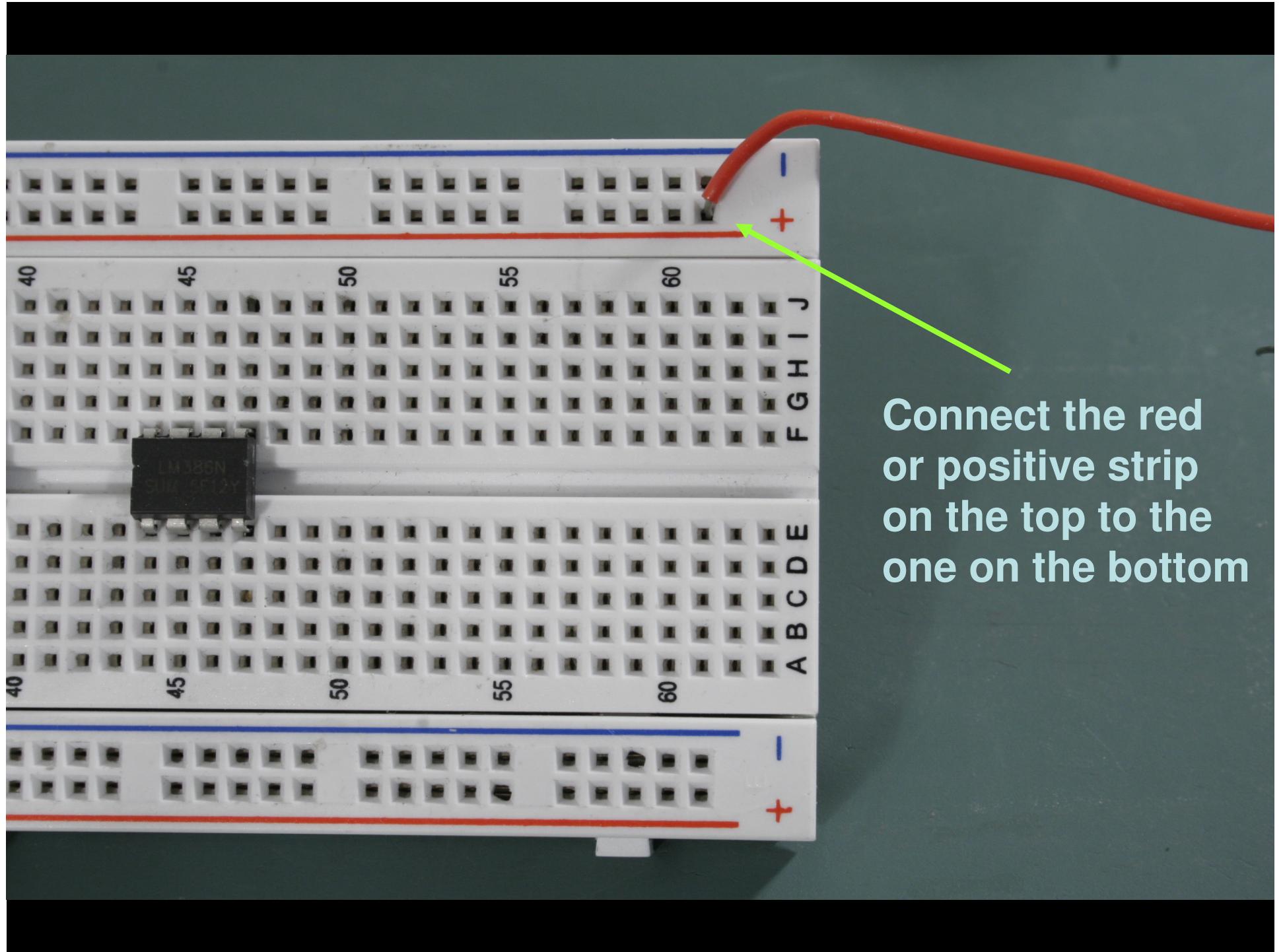


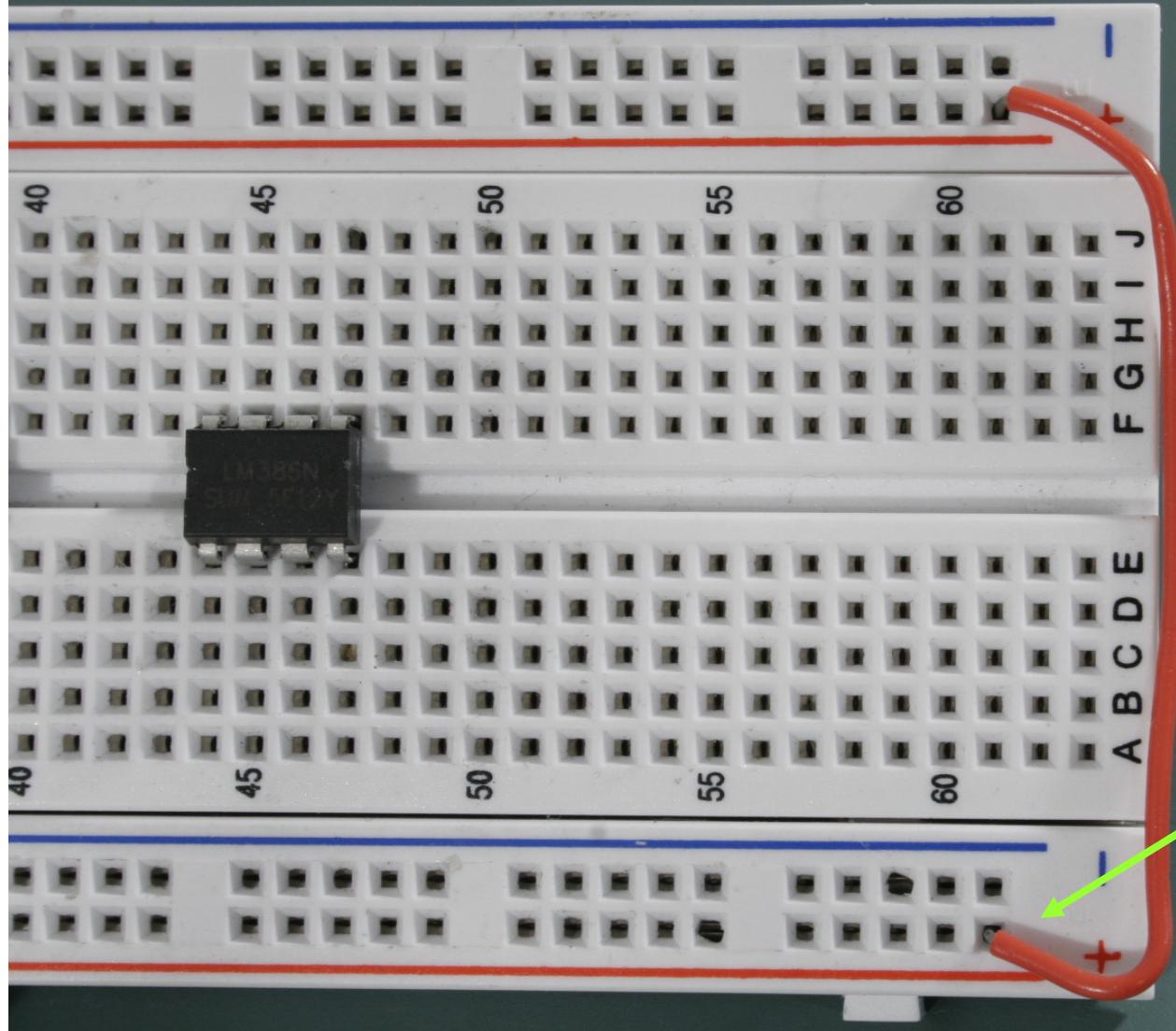Connect the red
or positive strip
on the top to the
one on the bottom




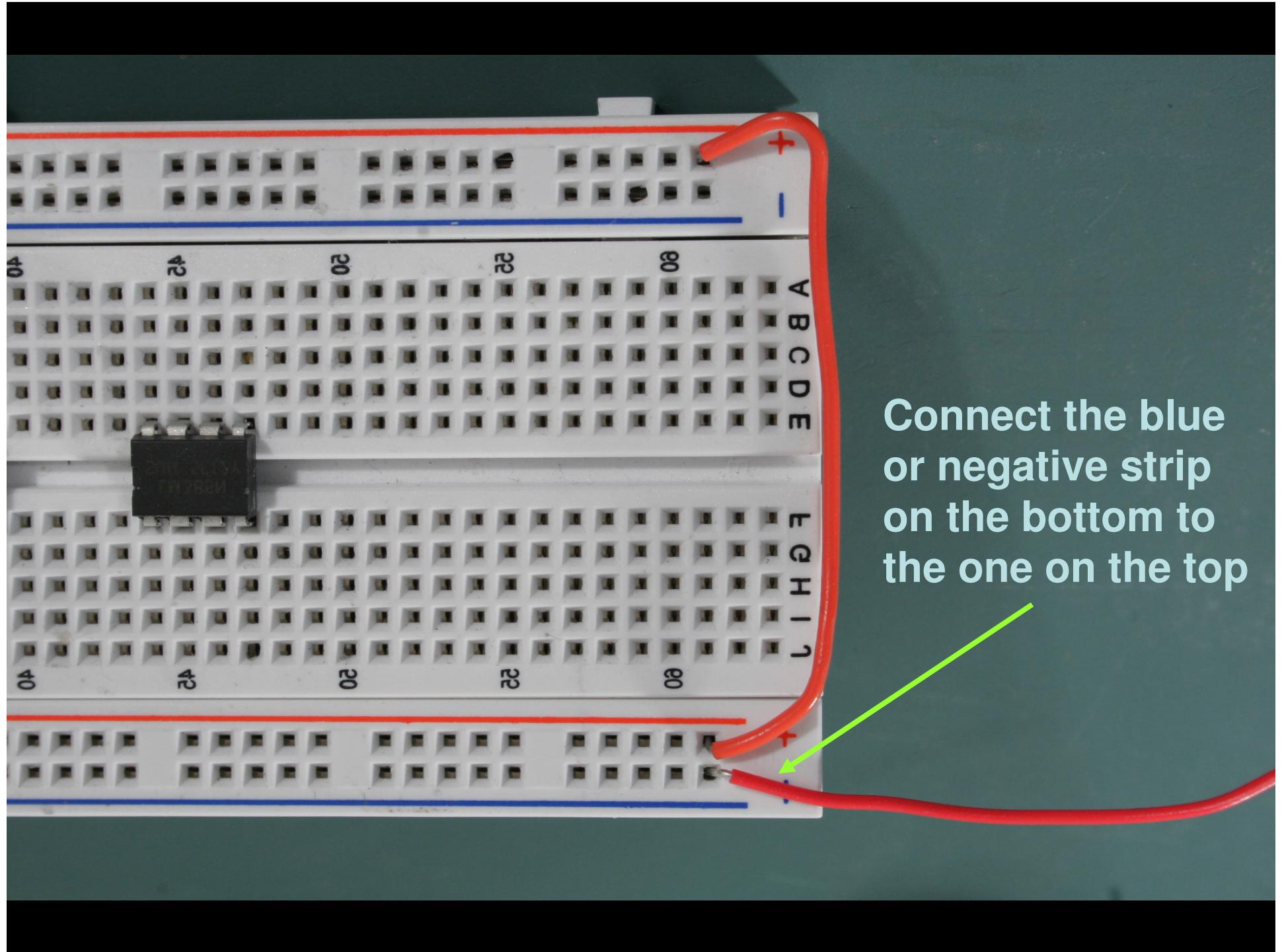Connect the red or positive strip on the top to the one on the bottom



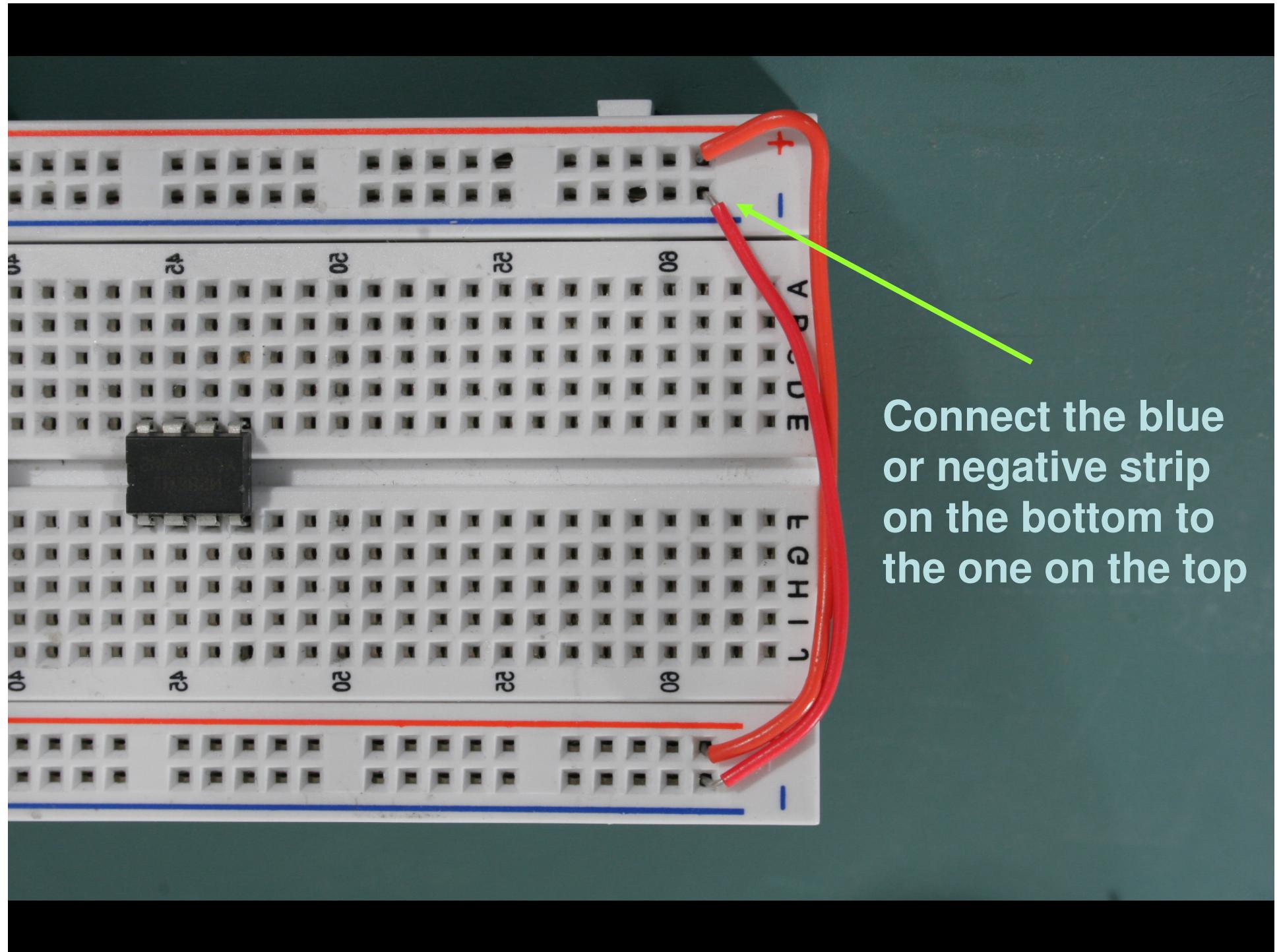


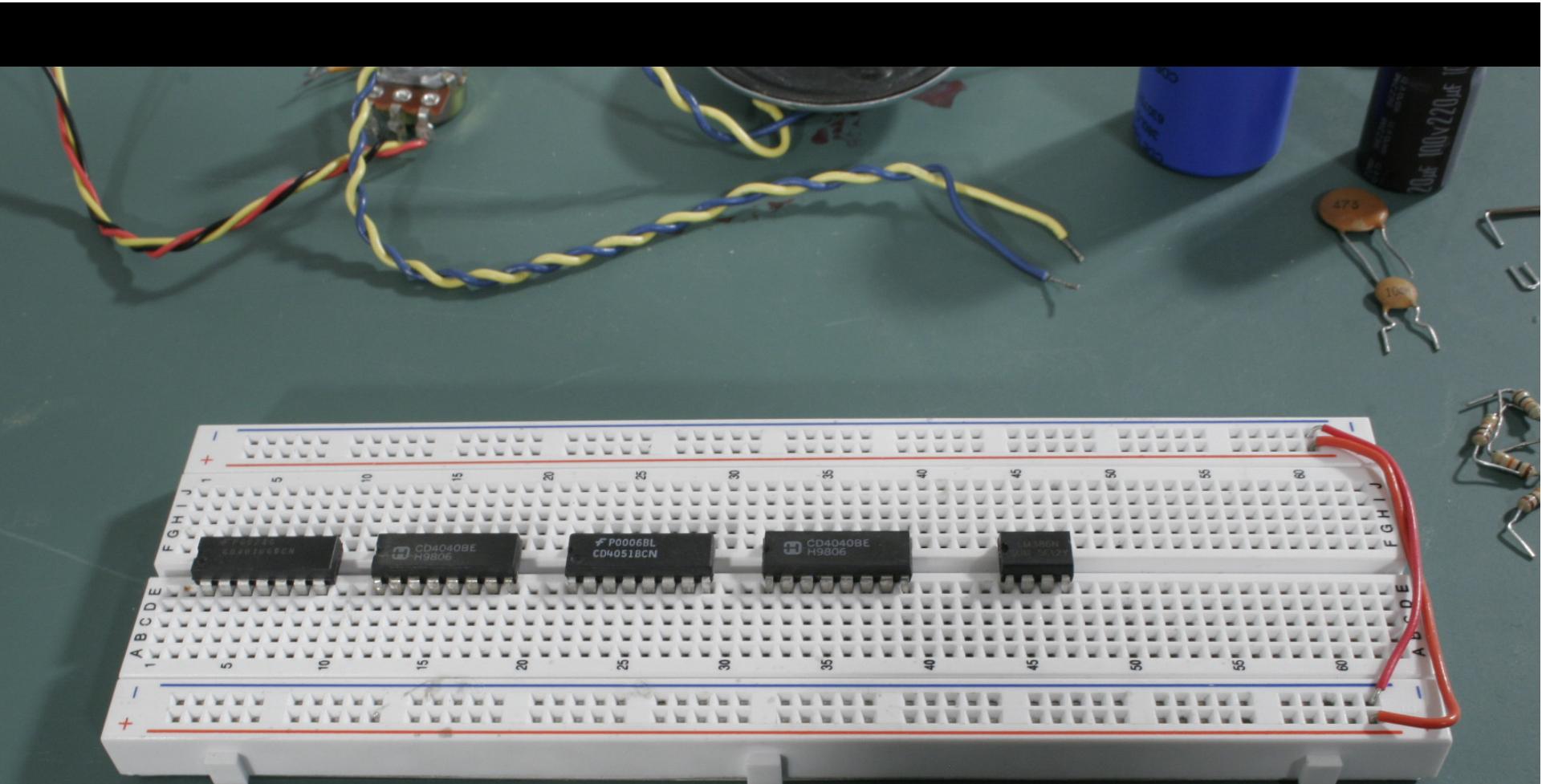Connect the blue or negative strip on the bottom to the one on the top





Gather 10 blue (or green) jumpers
to make ground connections.

The 40106 Inverting Buffer

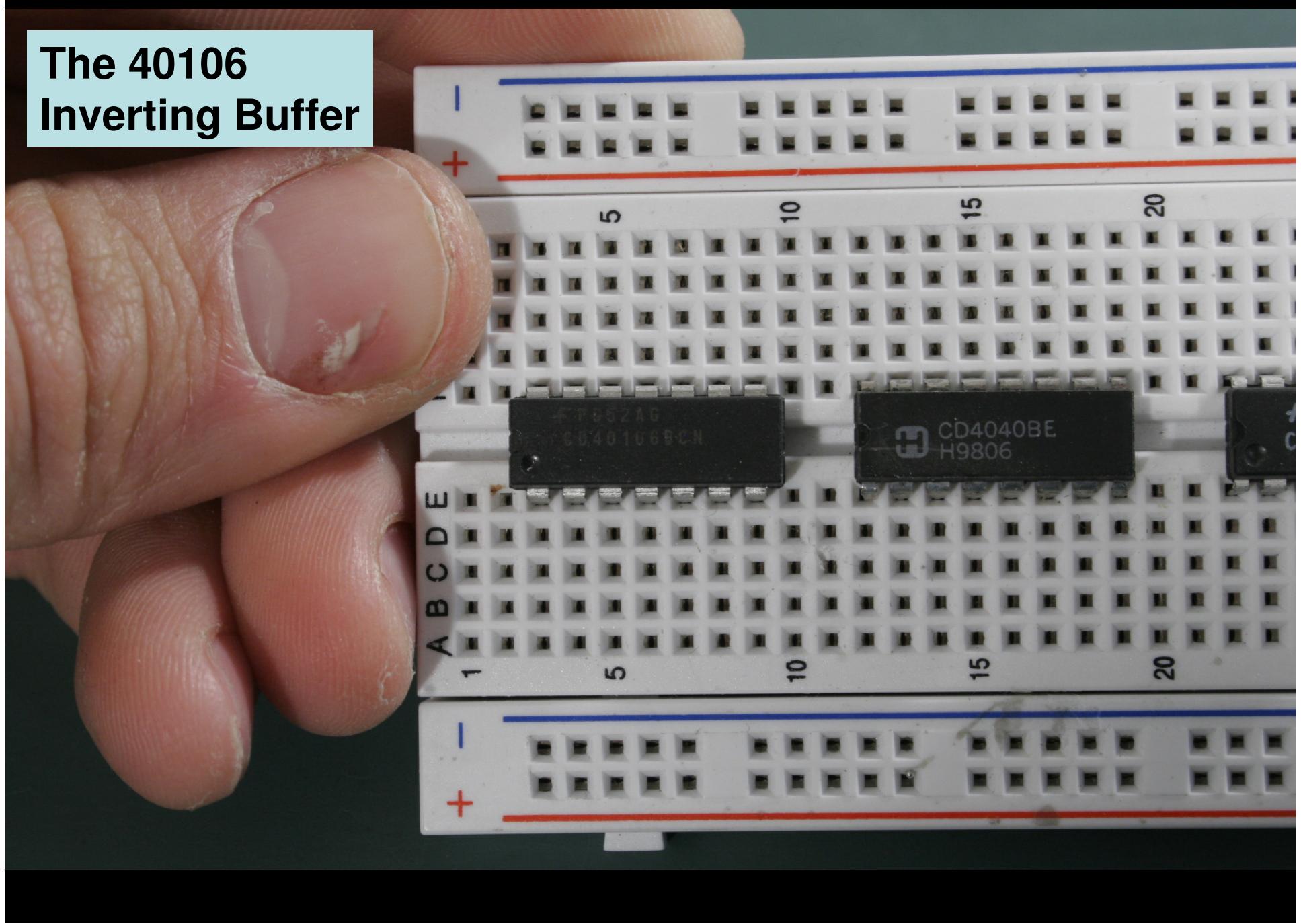


HEX SCHMITT TRIGGER

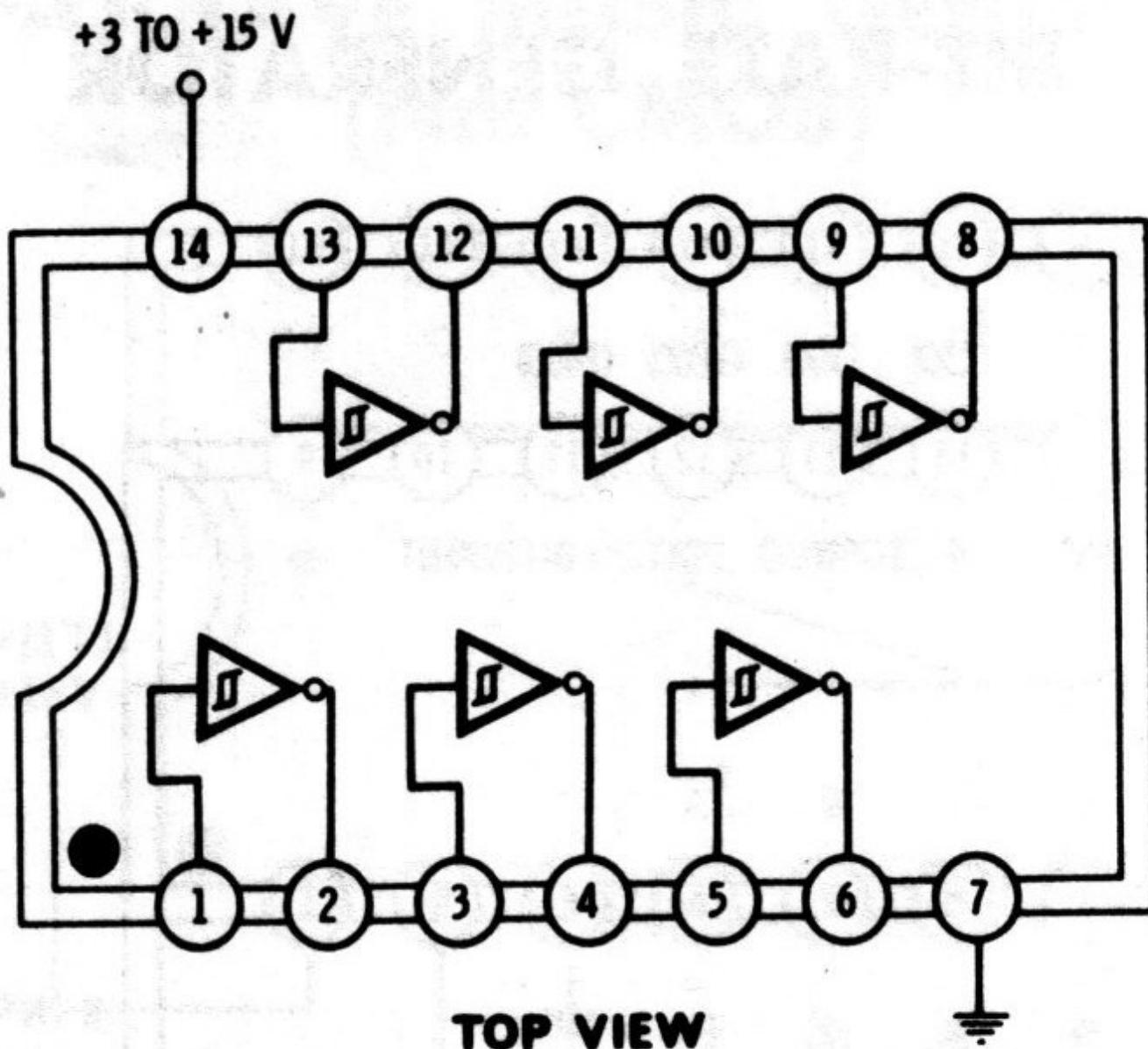

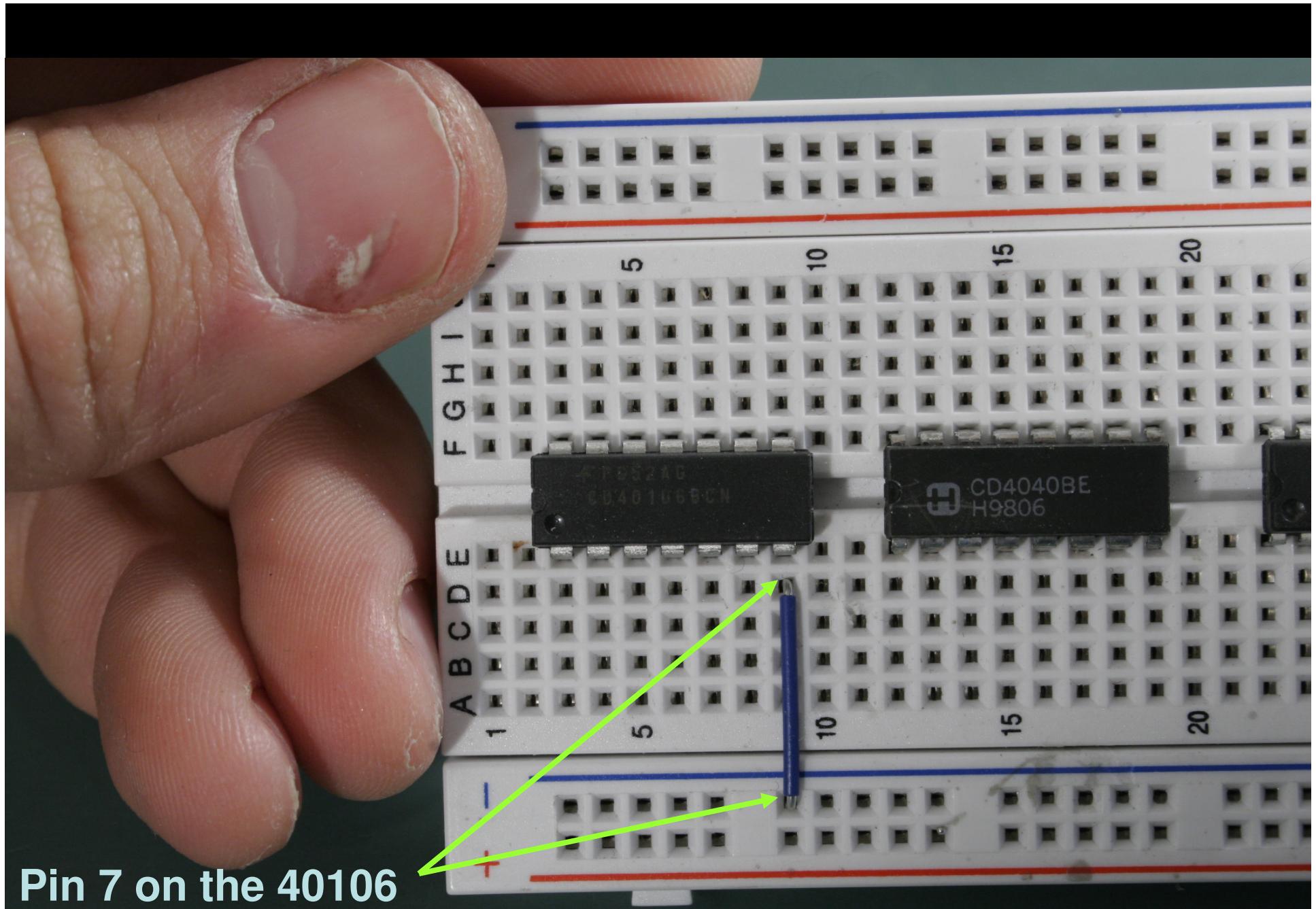


The 4040: 12 bit ripple counter

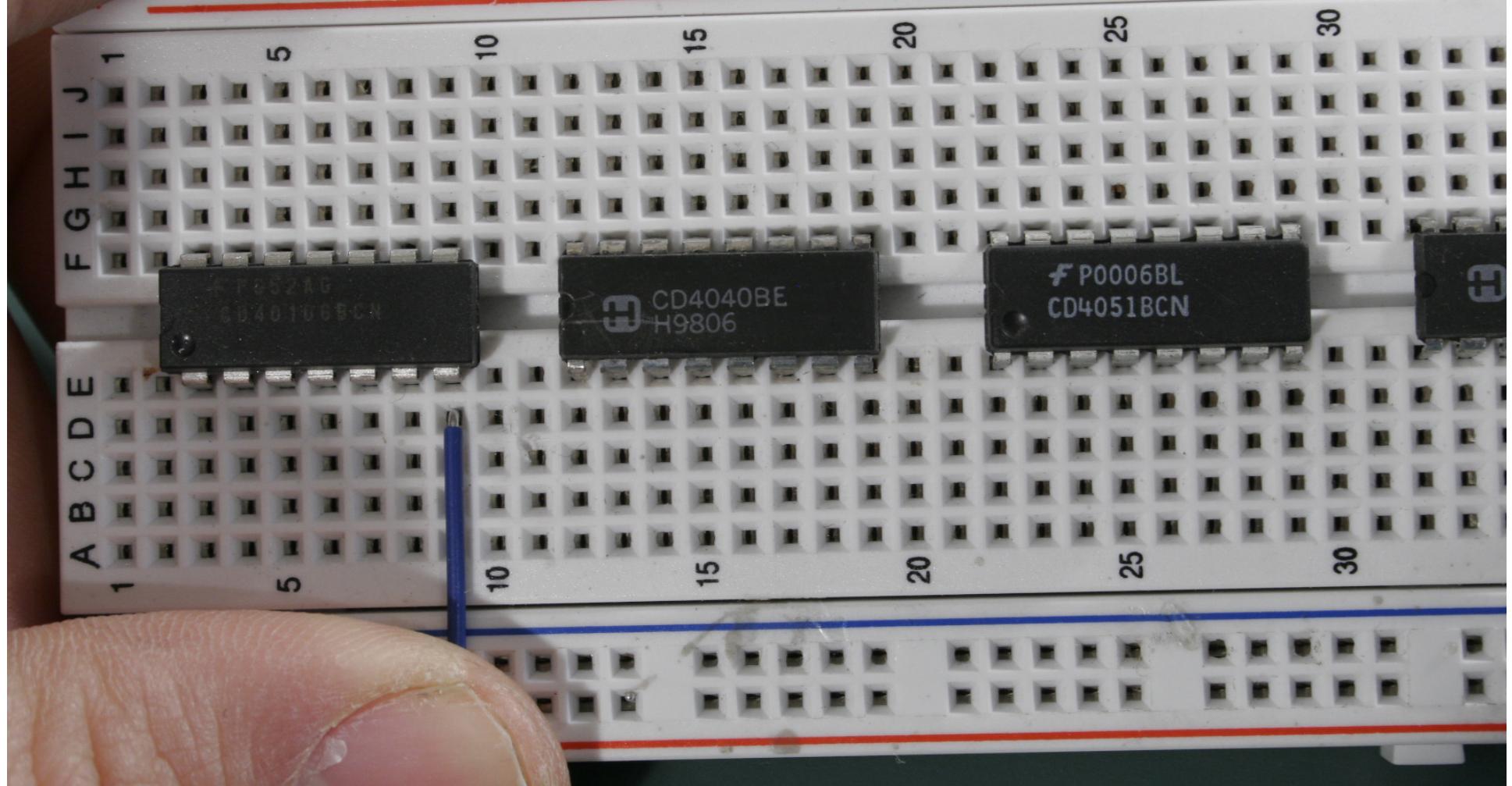


12-STAGE ($\div 4096$) BINARY RIPPLE COUNTER

+3 TO +15 V

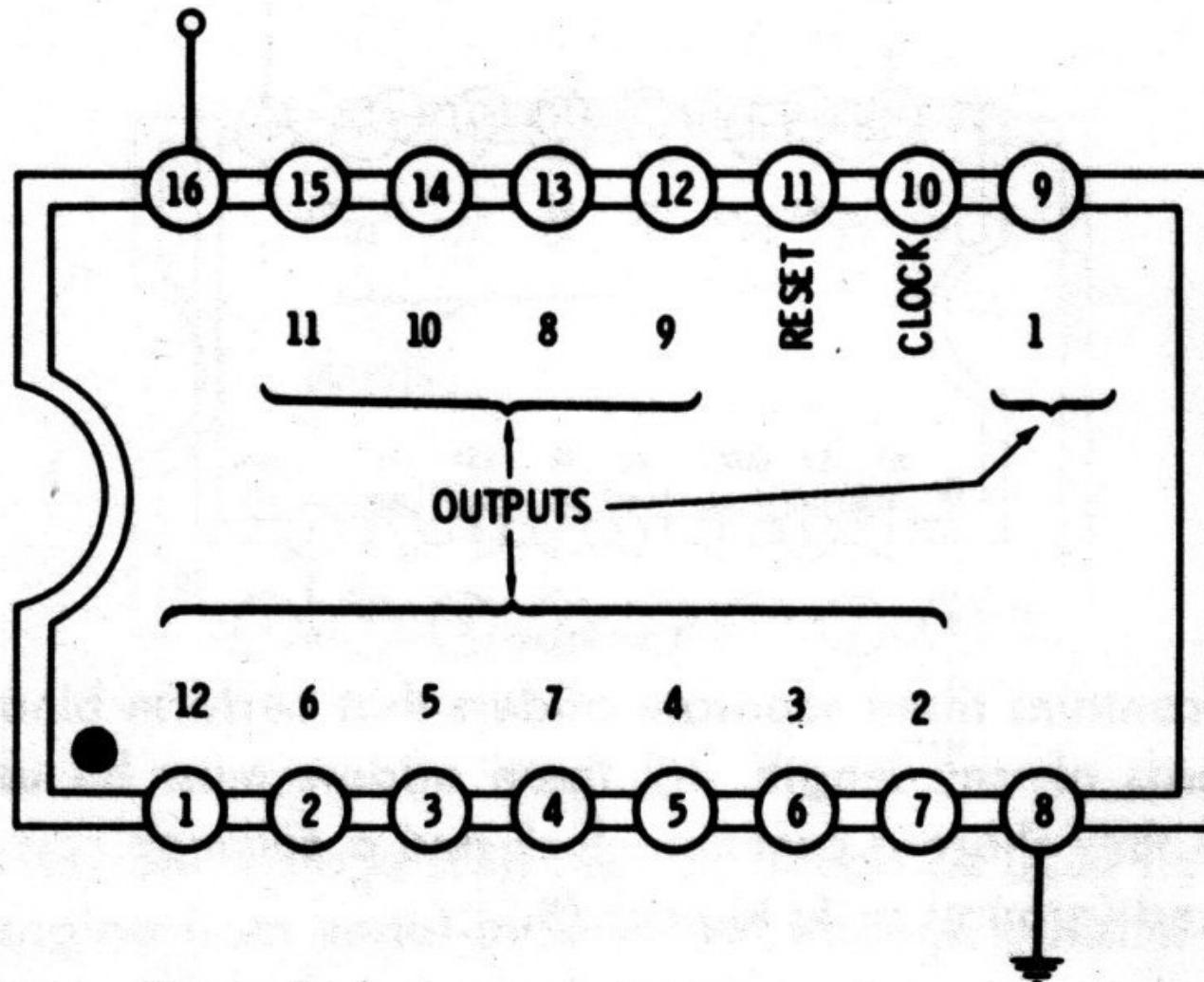

TOP VIEW

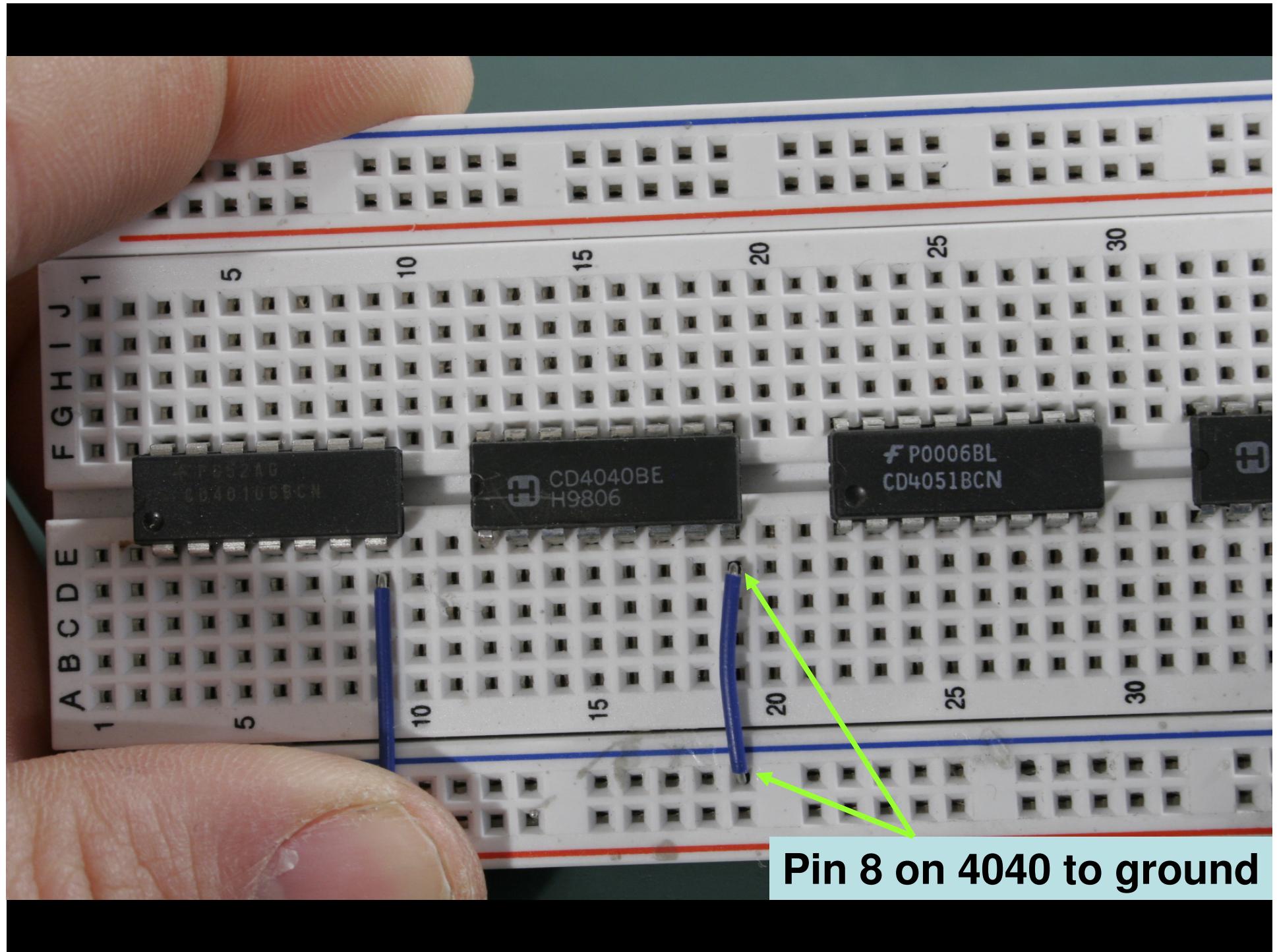


Pin 11 to ground



Pin 8 on 4040 to ground




The 4051: 1 of 8 multiplexer

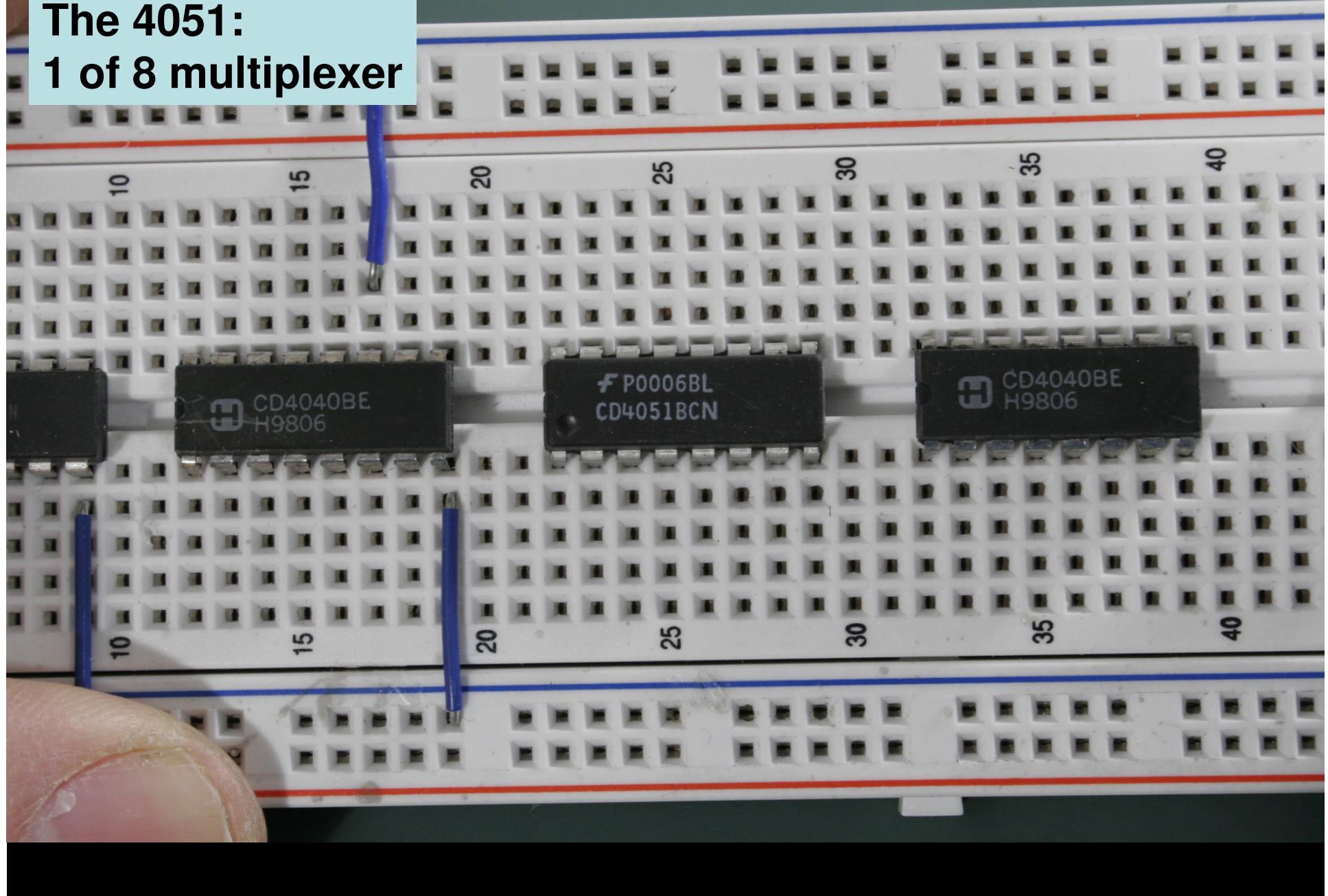

1-OF-8 SWITCH


+5 V (ANALOG)


+5 TO +15 V (DIGITAL)

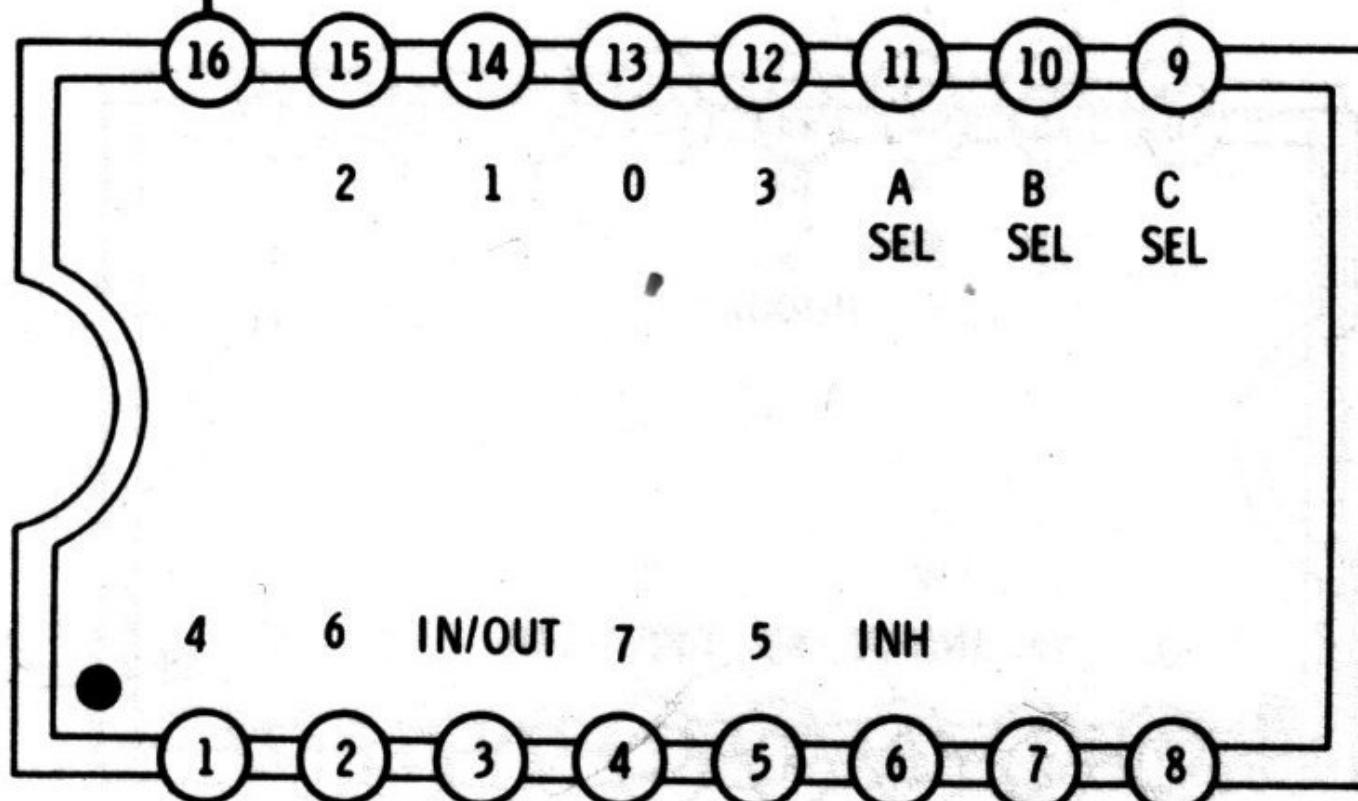


TOP VIEW


-5 V (ANALOG)
GND (DIGITAL)

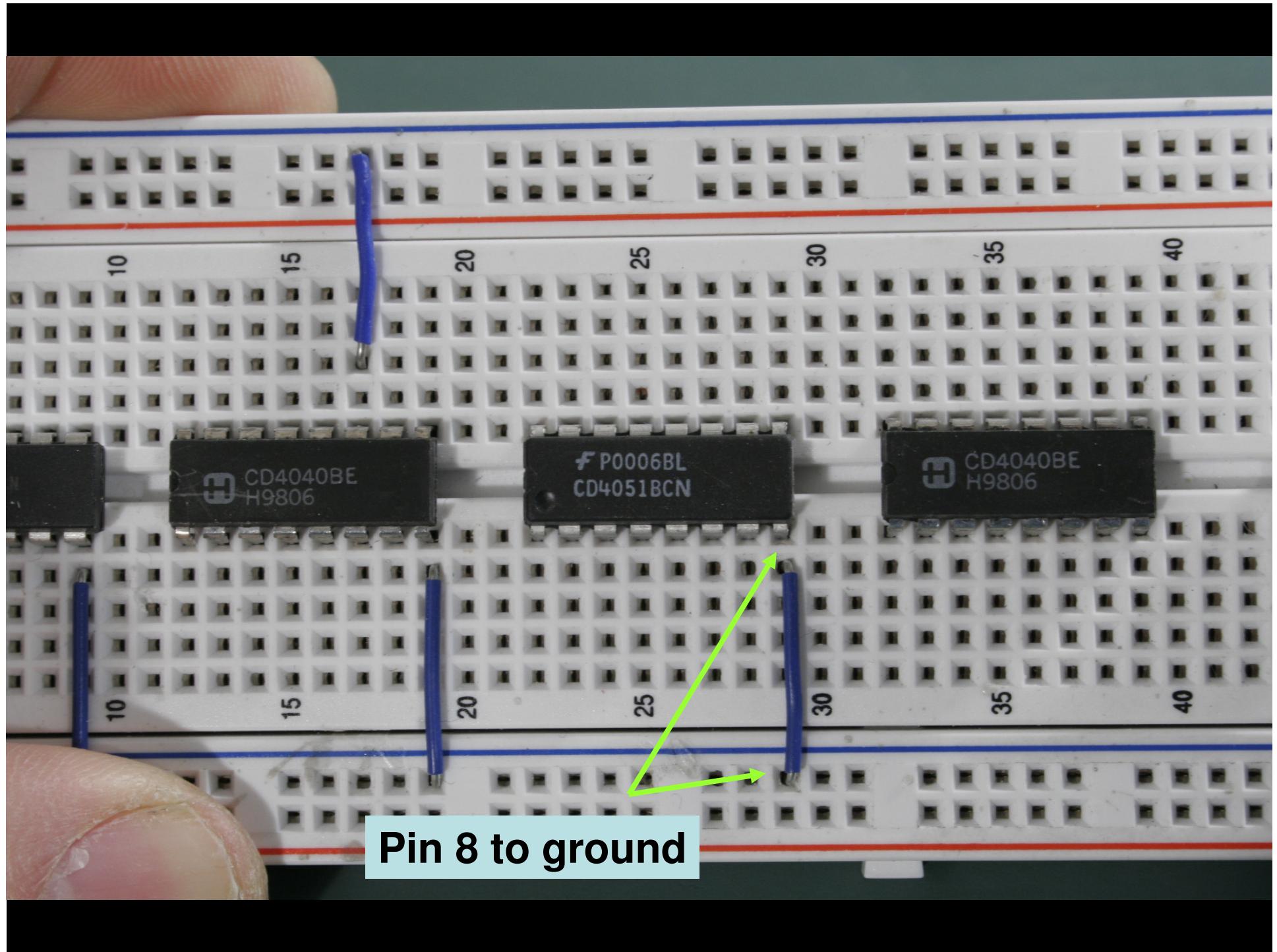

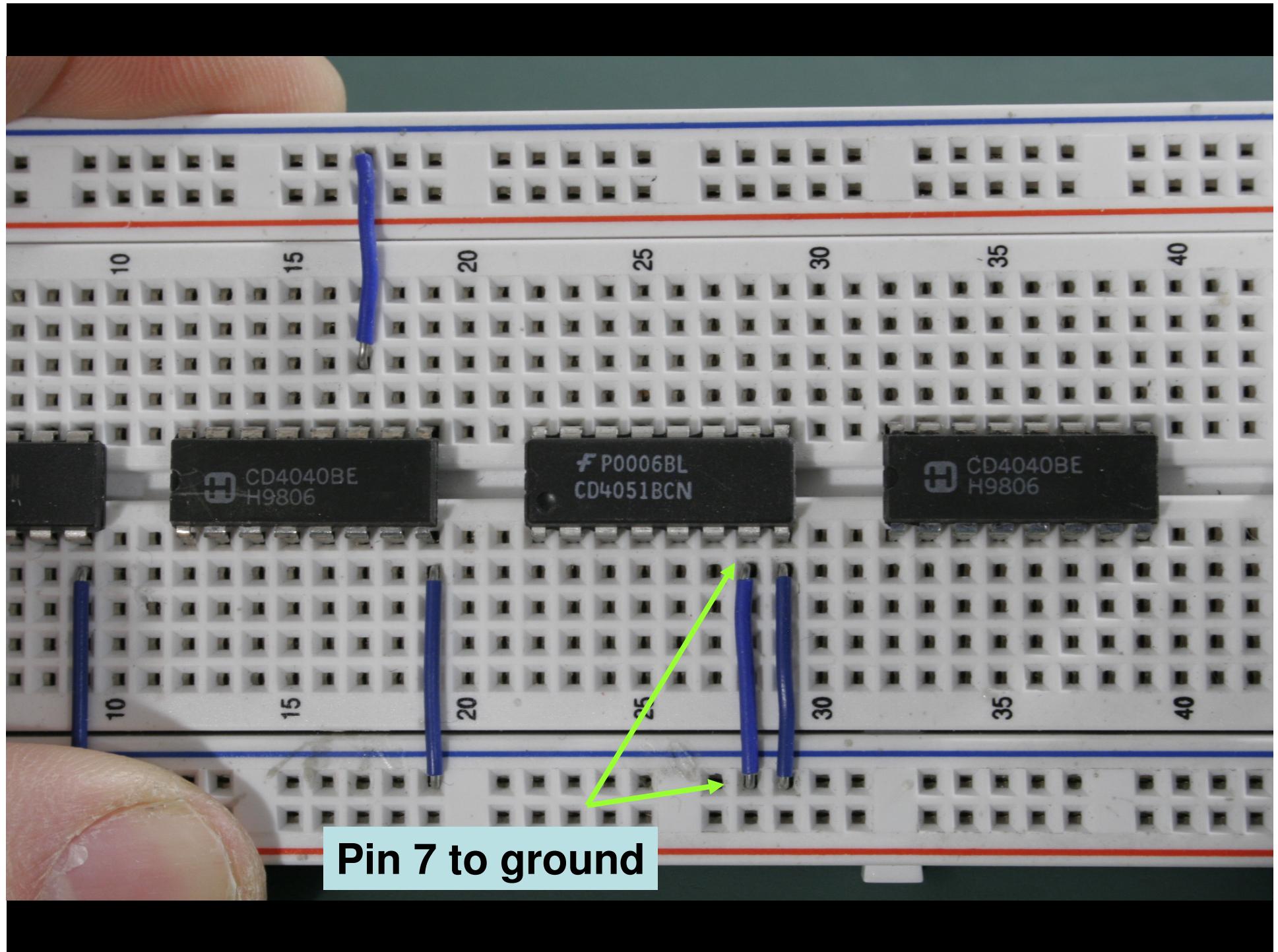


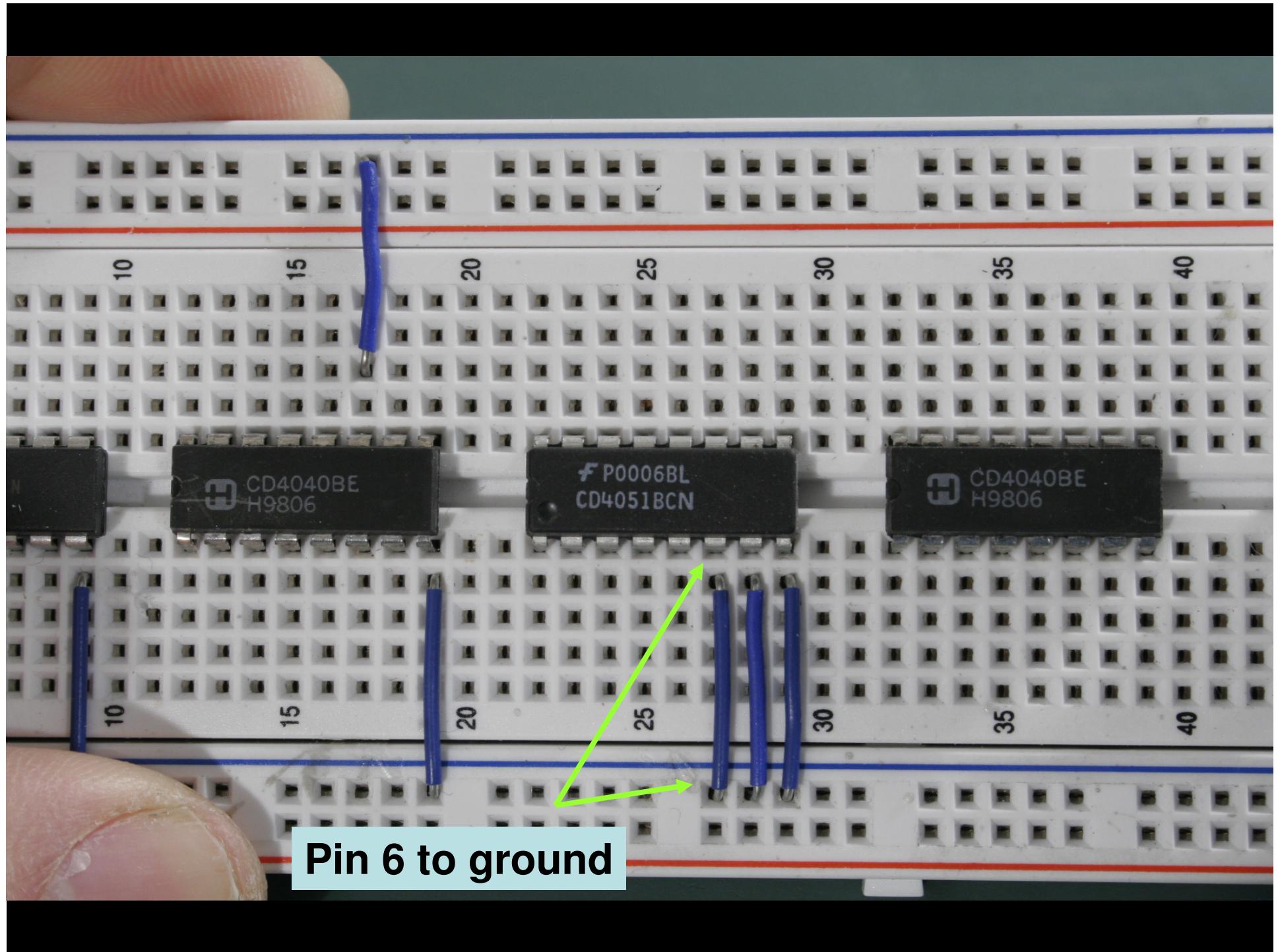


The 4040: 12 bit ripple counter

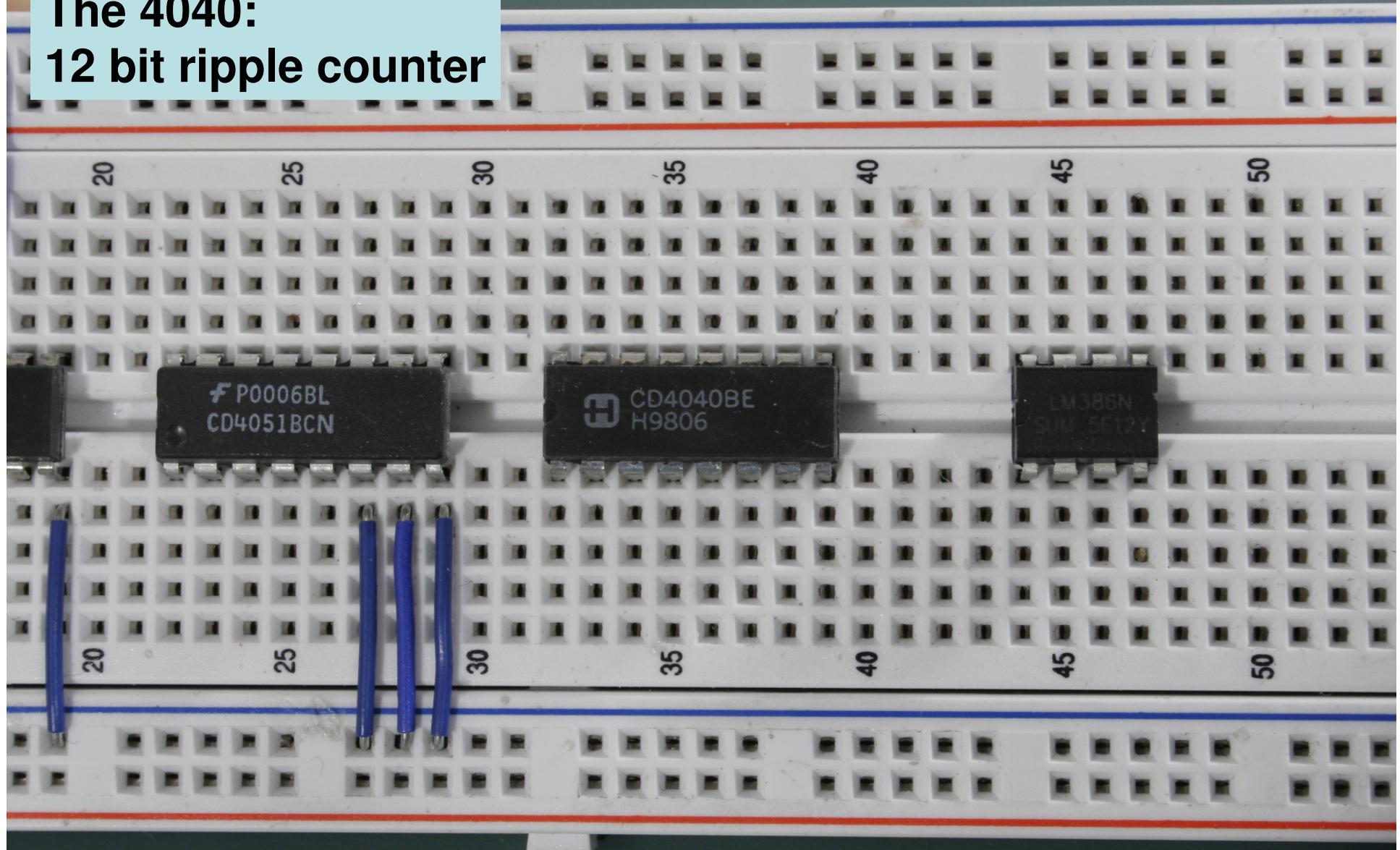

Pin 11 to ground

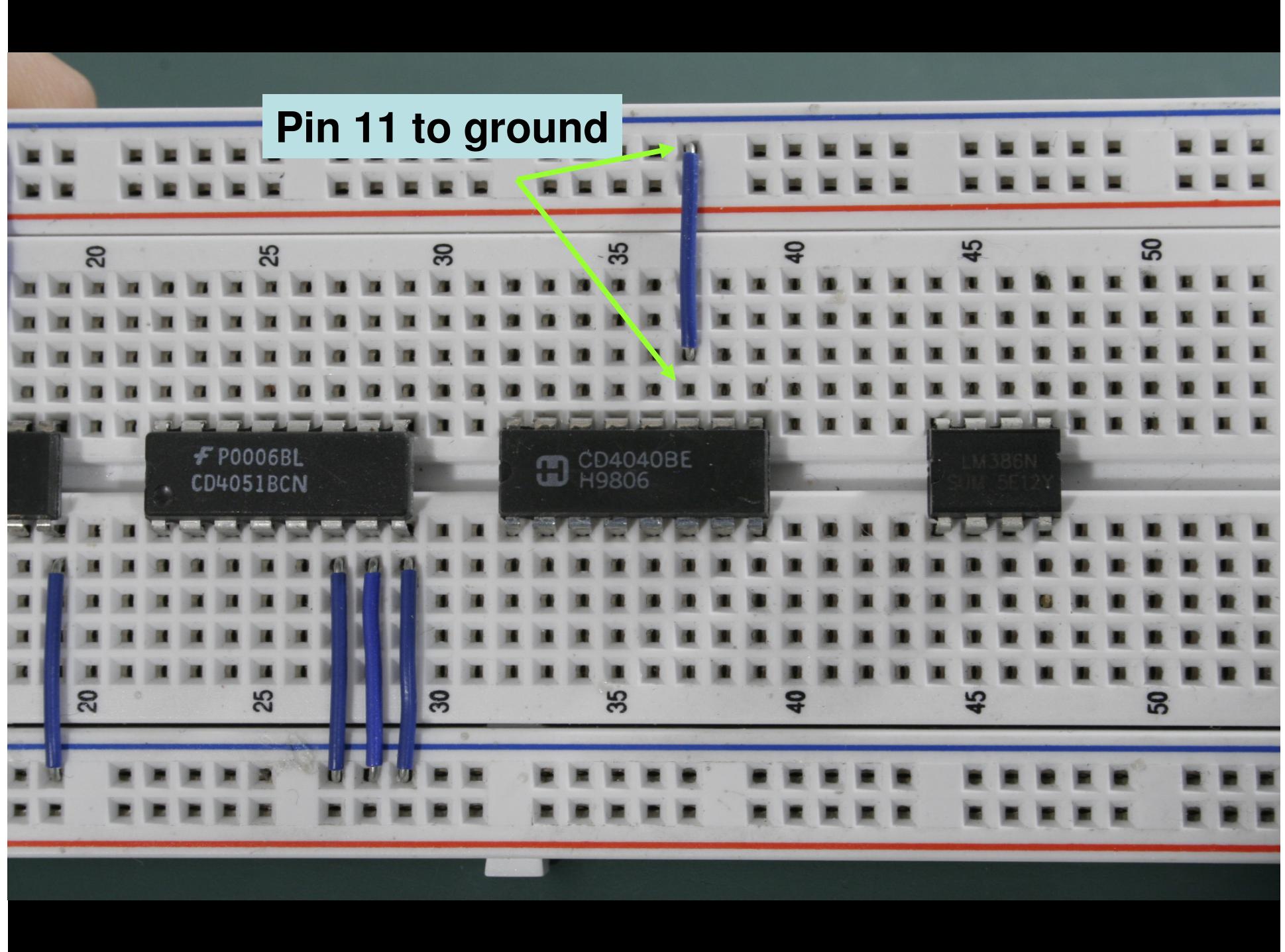


Pin 11 to ground


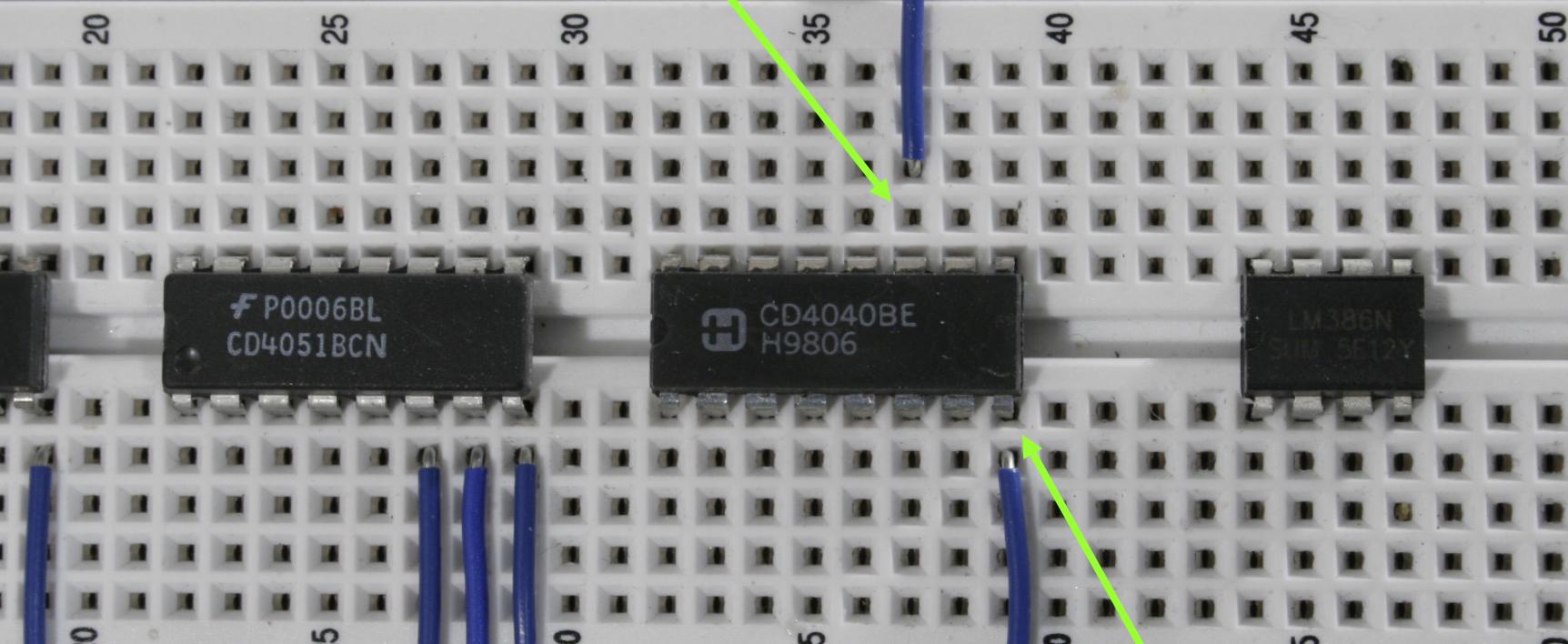



Pin 8 to ground


The LM386 Amplifier IC

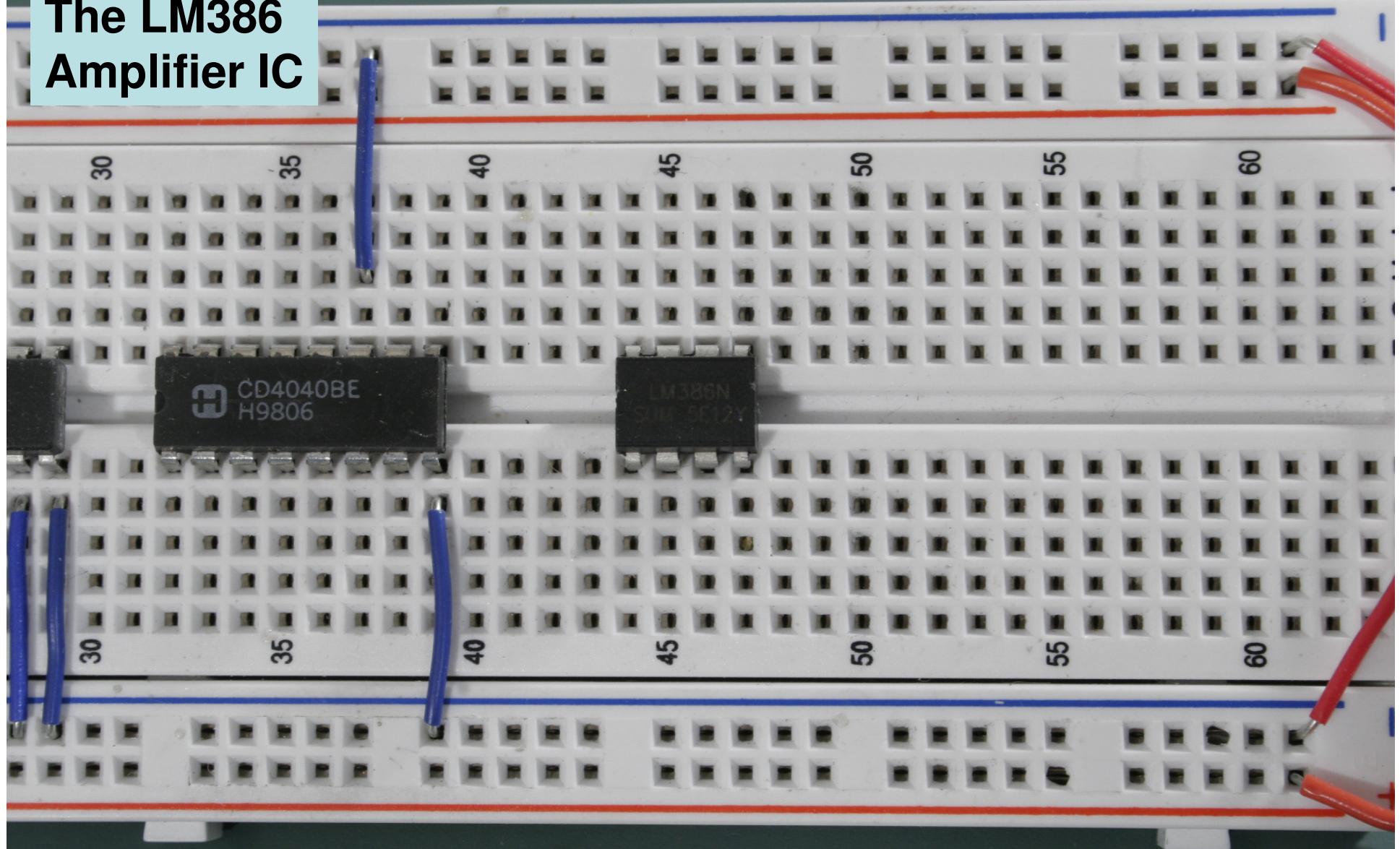


LM 386 Audio Amplifier

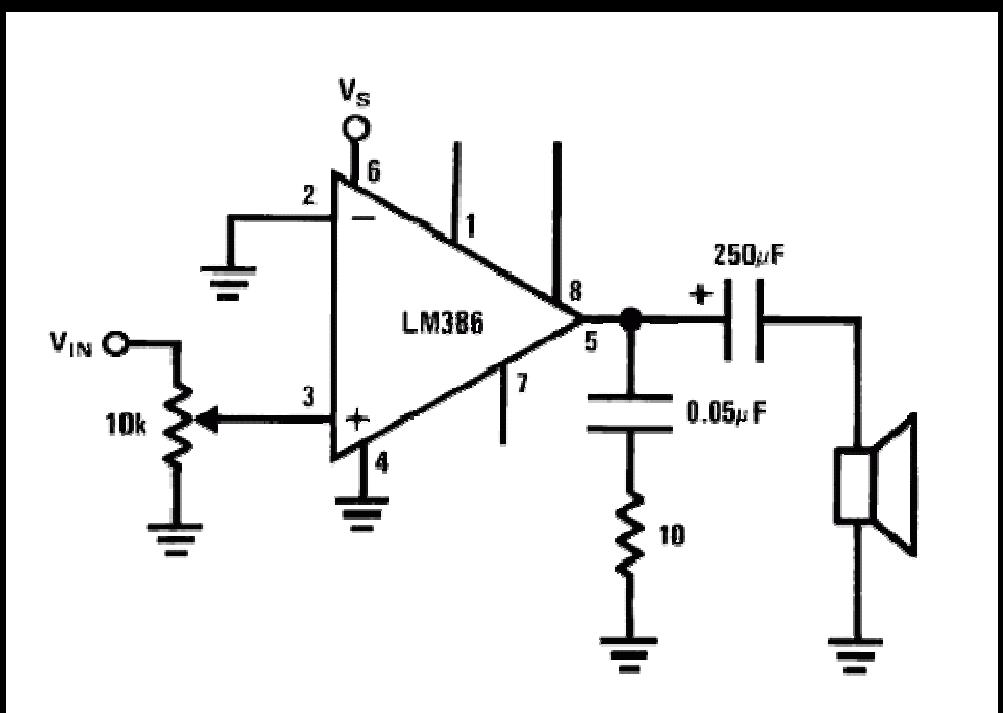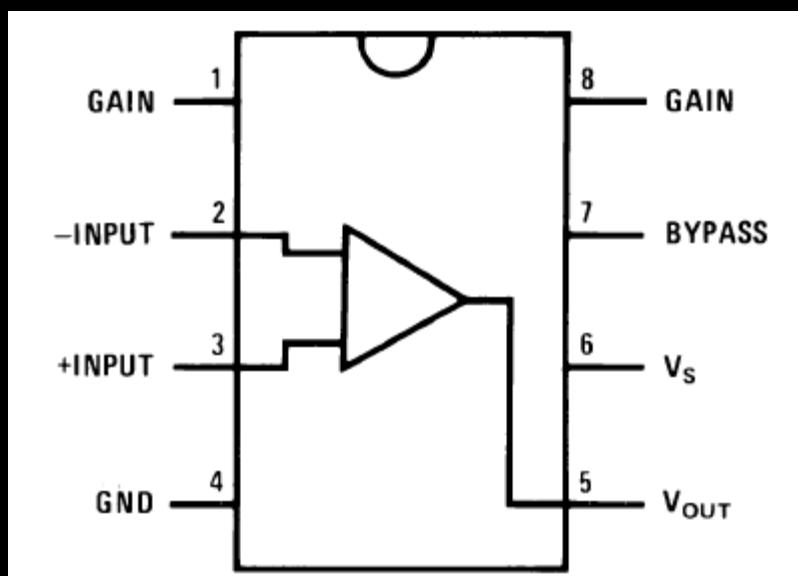

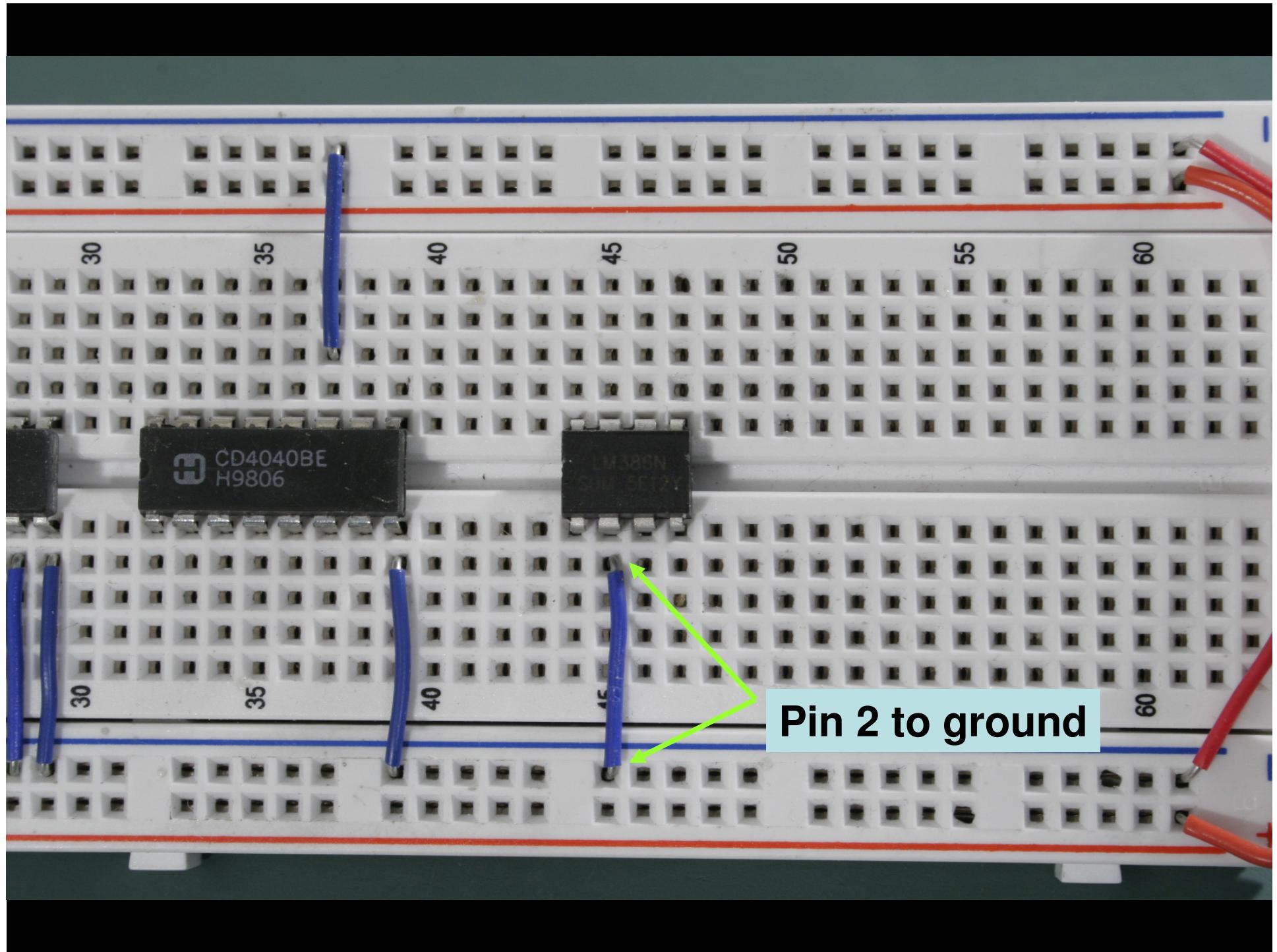


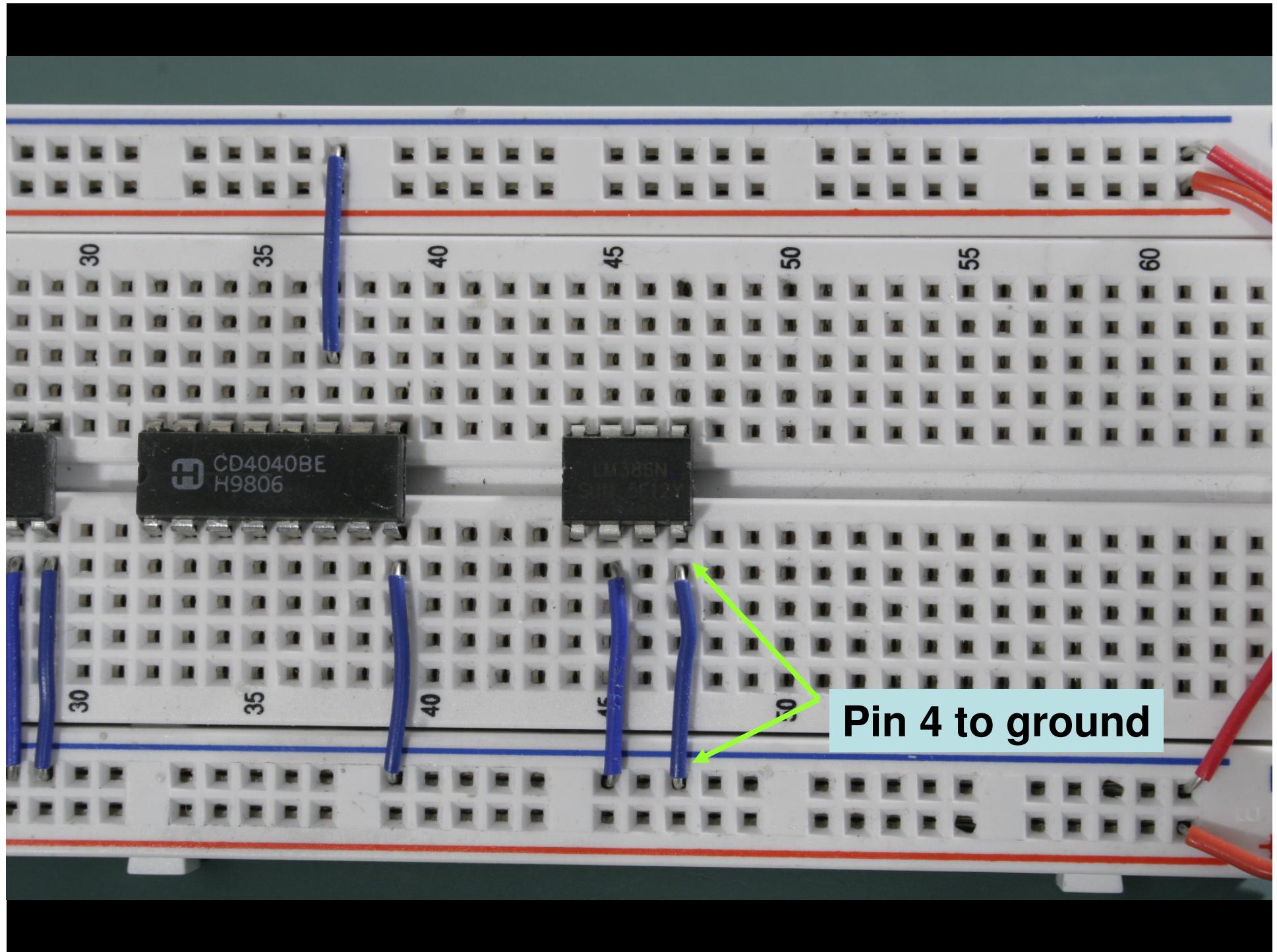

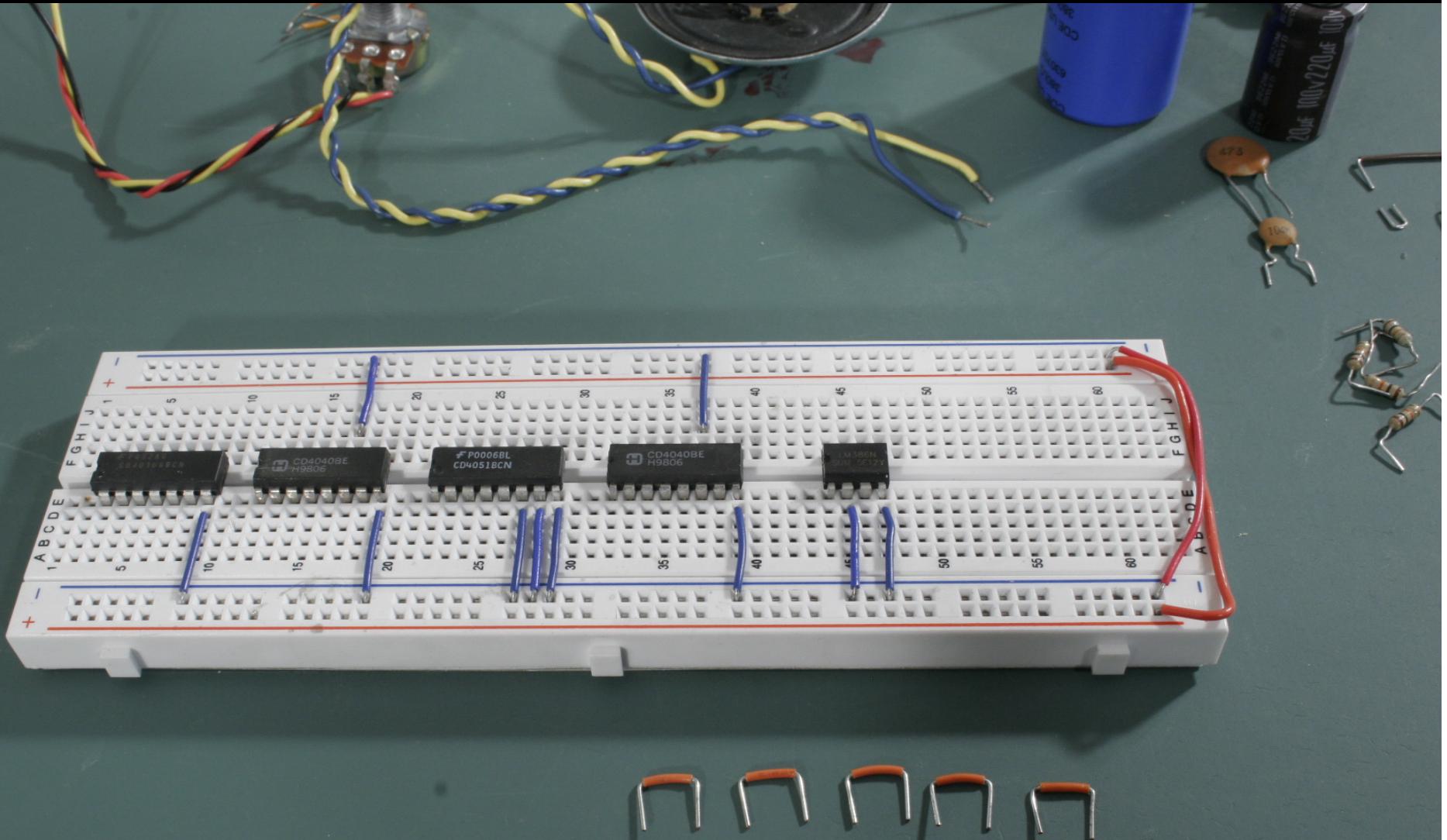


Get 5 orange jumpers
to connect the chips to the positive voltage rail.


Pin 14 goes to
the positive supply

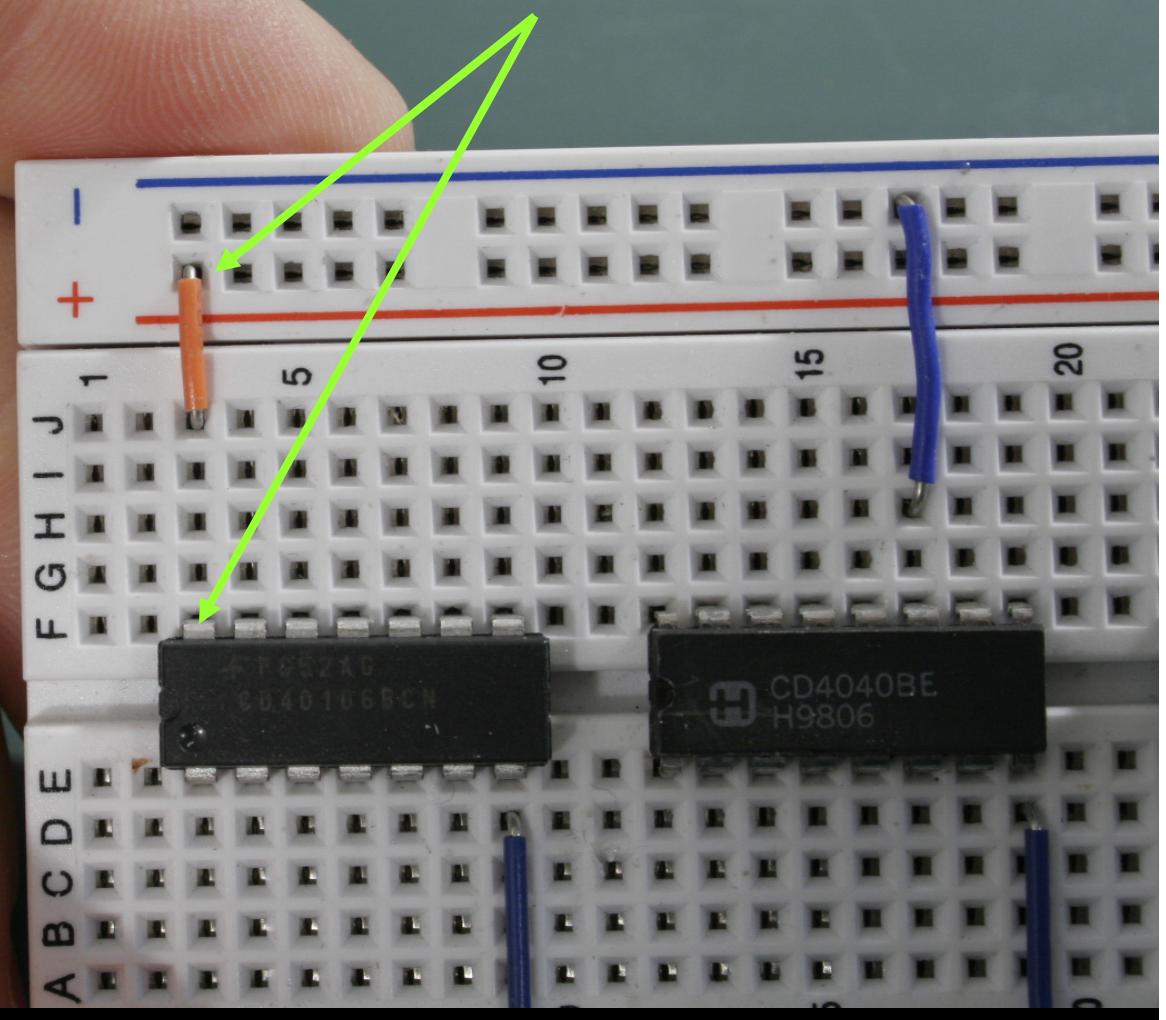


Pin 16 goes to
the positive supply

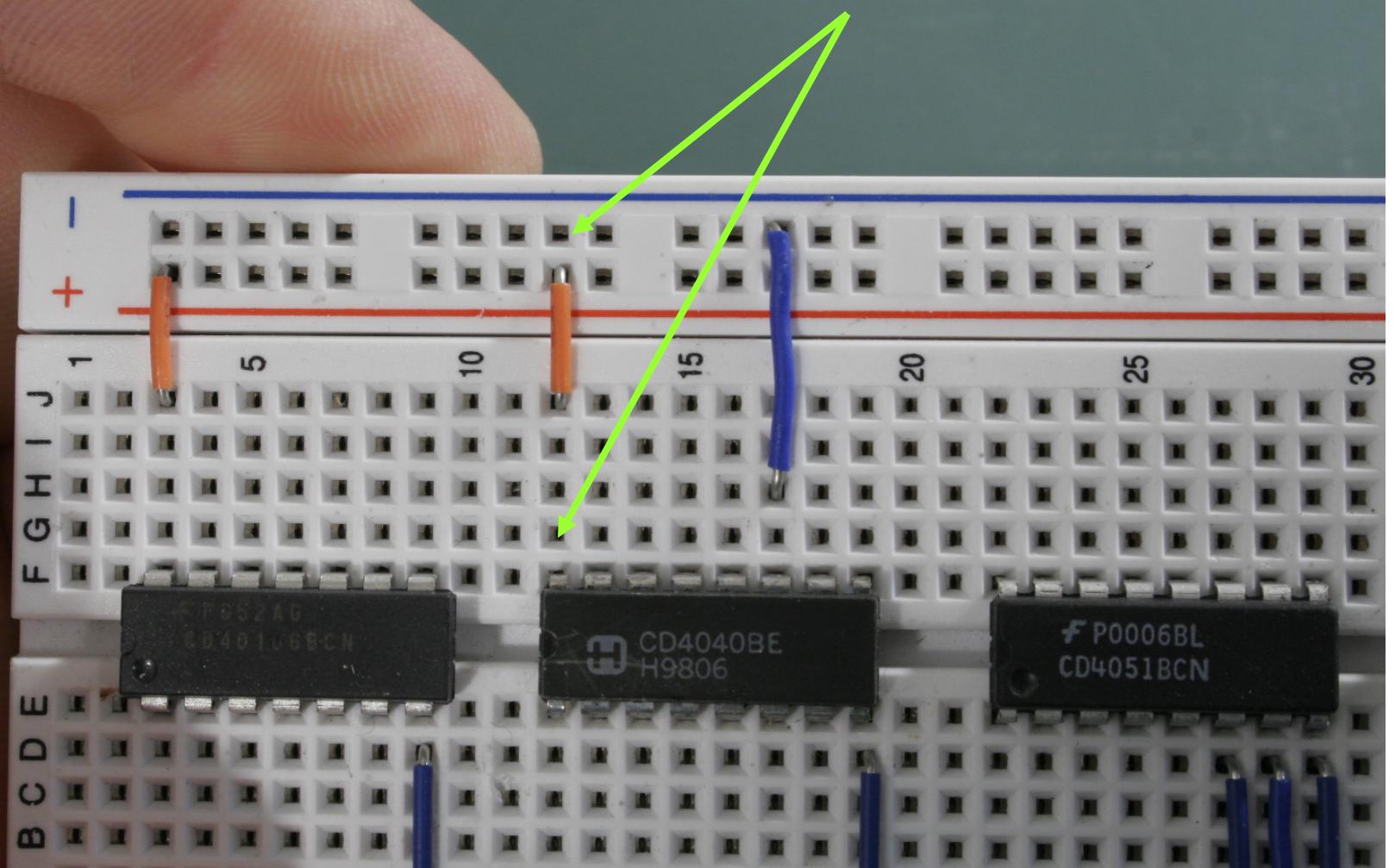


Pin 16 goes to
the positive supply

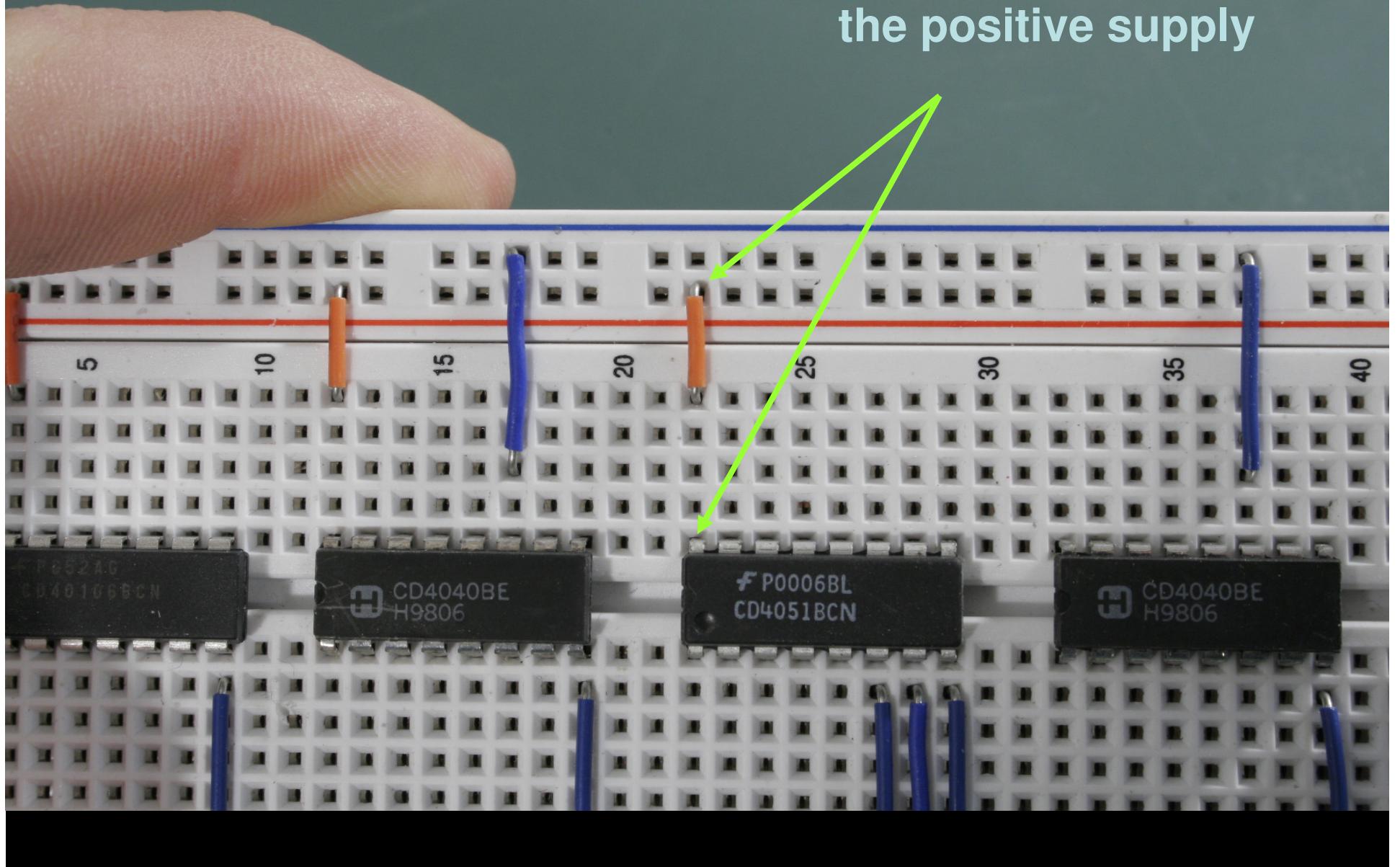


Pin 16 goes to
the positive supply

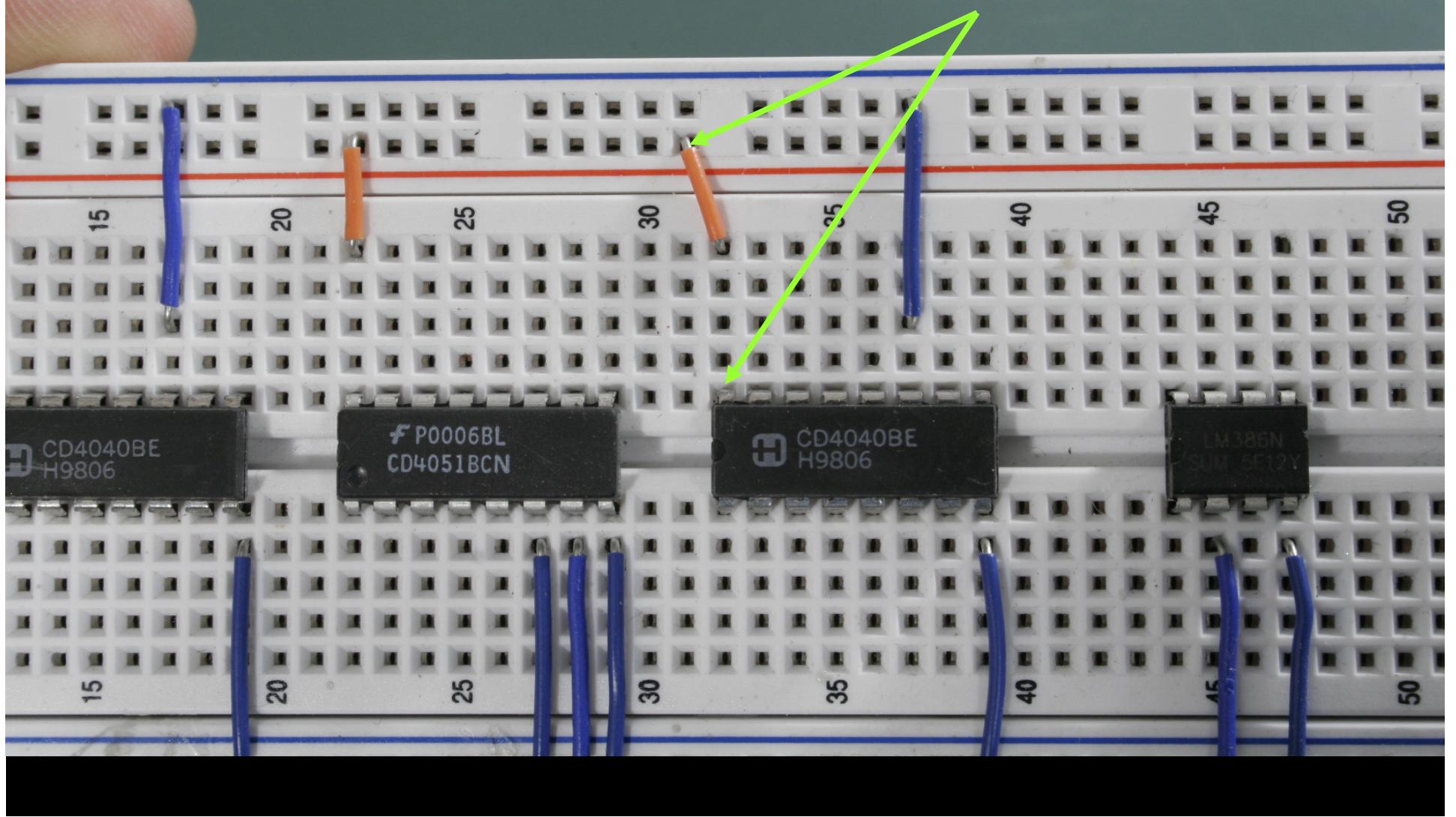


Pin 6 goes to
the positive supply

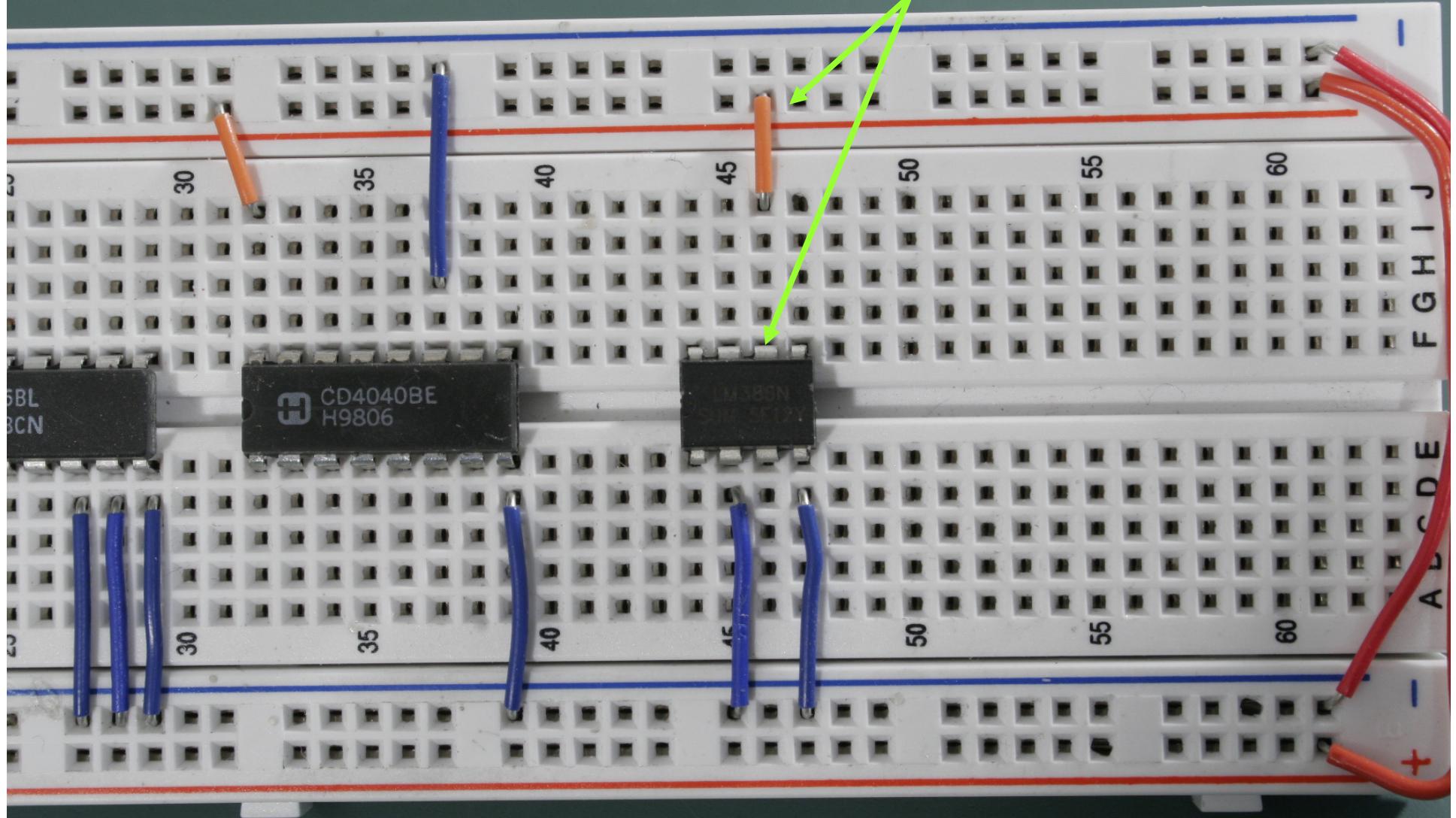

40106: RC Relaxation Oscillator

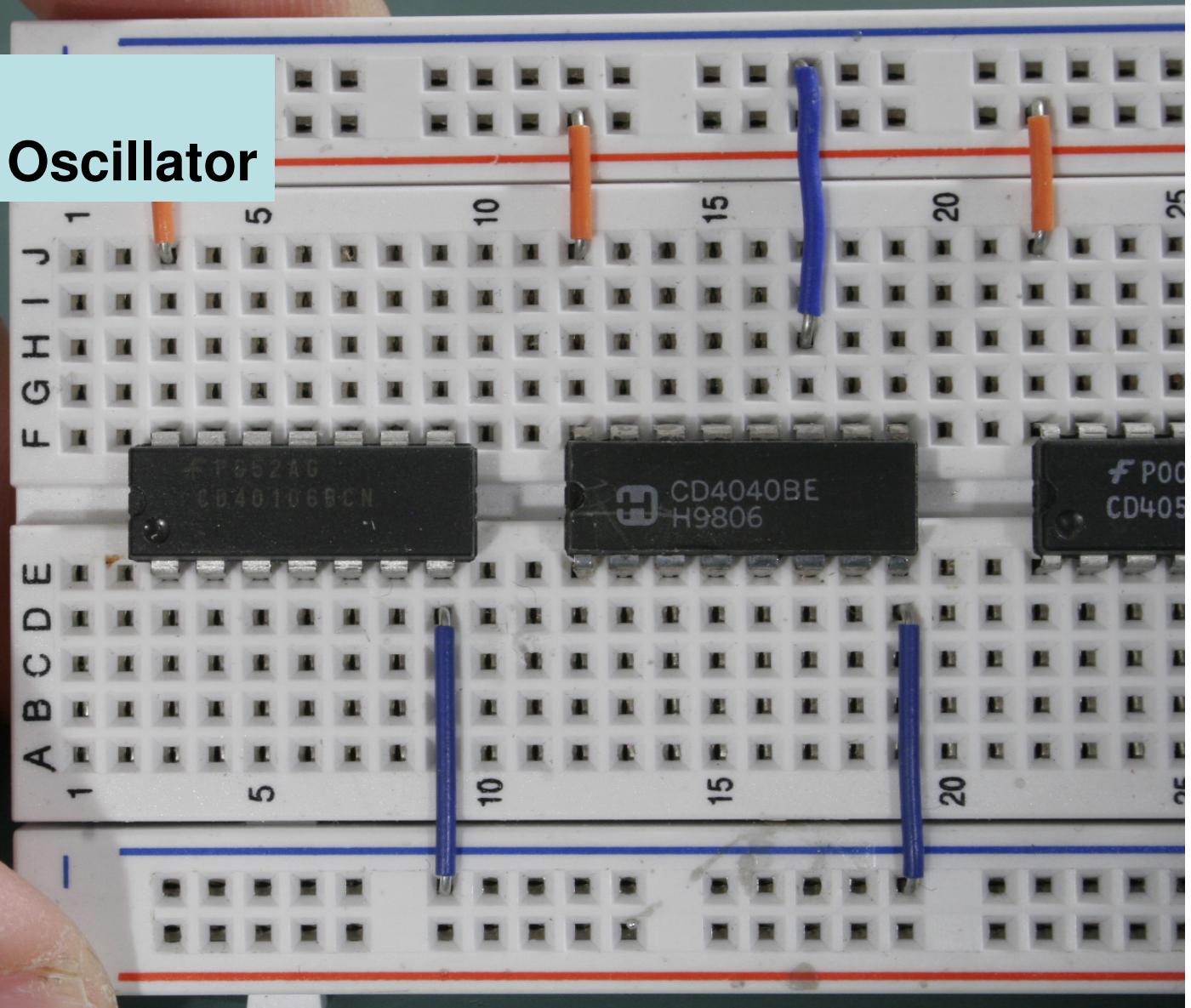

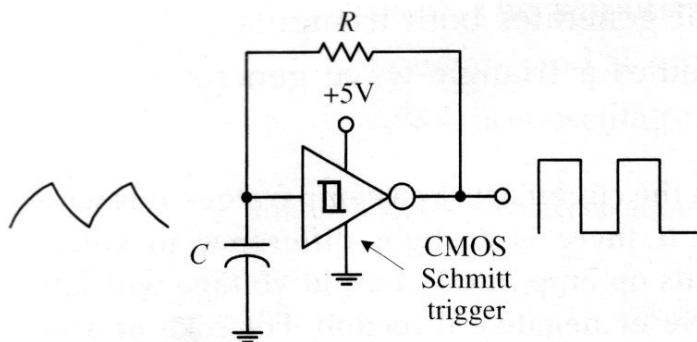
Digital oscillator
(using a Schmitt trigger inverter)




Digital oscillator (using inverters)

Here a simple relaxation oscillator is built from a Schmitt trigger inverter IC and an RC network. (Schmitt triggers are used to transform slowly changing input waveforms into sharply defined, jitter-free output waveforms (see Chap. 12). When power is first applied to the circuit, the voltage across C is zero, and the output of the inverter is high (+5 V). The capacitor starts charging up toward the output voltage via R. When the capacitor voltage reaches the positive-going threshold of the inverter (e.g., 1.7 V), the output of the inverter goes low (~0 V). With the output low, C discharges toward 0V. When the capacitor voltage drops below the negative-going threshold voltage of the inverter (e.g., 0.9V), the output of the inverter goes high. The cycle repeats. The on/off times are determined by the positive- and negative-going threshold voltages and the RC time constant.


How does it work?

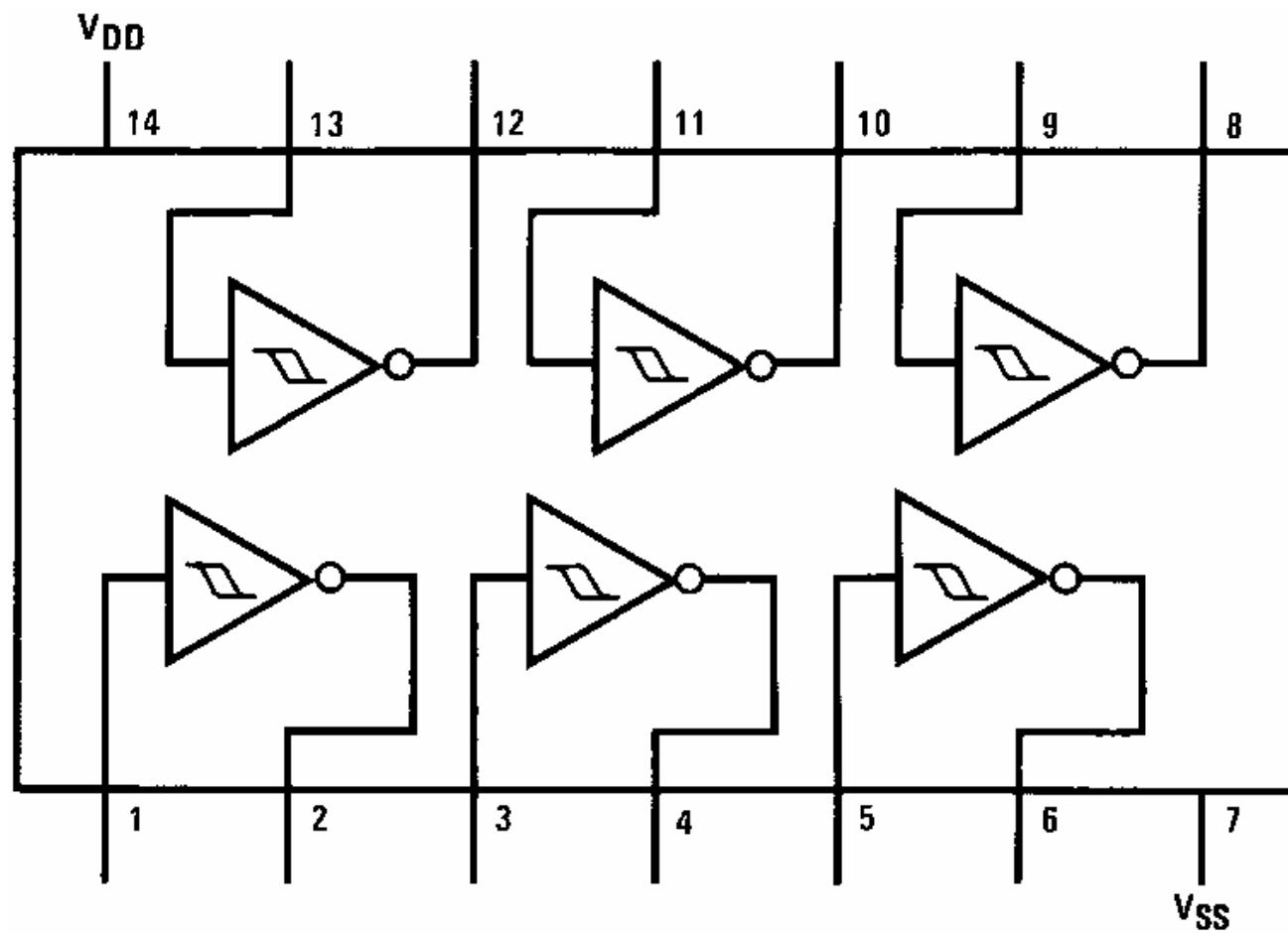

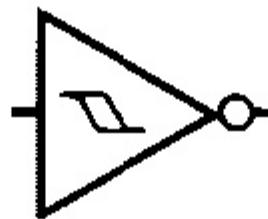**One of Six digital logic gates:
Inverter**



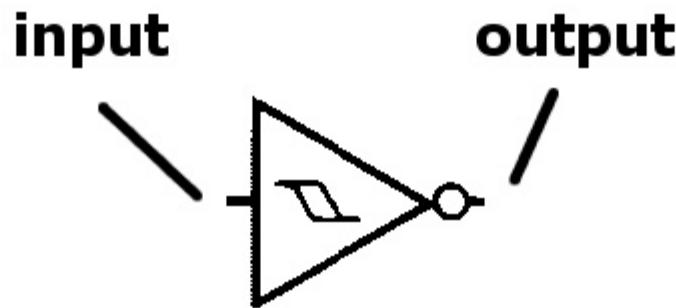
In digital circuits, positive logic interprets a positive voltage as logical 1, on or "yes". Zero volts or ground is interpreted as logical 0, off or "no."




This inverter returns the logical inverse, or opposite, of the signal presented at its output.

**Input +V: Logical 1
(typically 5 volts)**

**Output GND: Logical 0
(zero volts)**

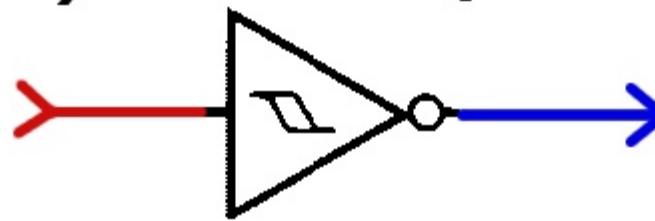

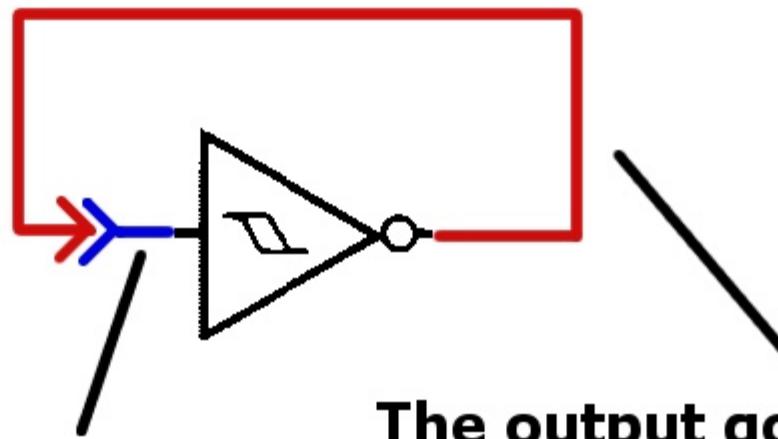
What happens when we connect the input to the output?



the input starts off as floating, or at ground


The output goes positive, then becomes the input.

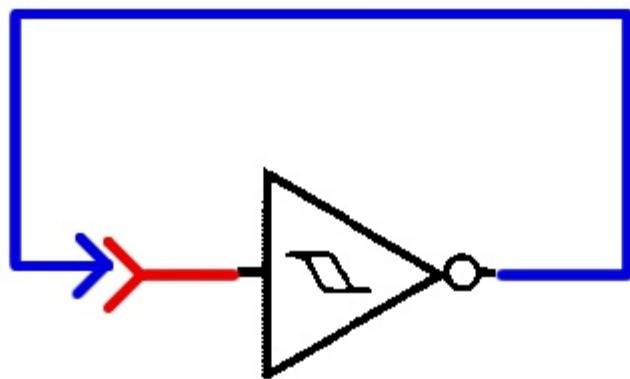What happens when we connect the input to the output?




The positive signal forces the output to ground, which becomes the input, thus forcing the output positive... and so on....

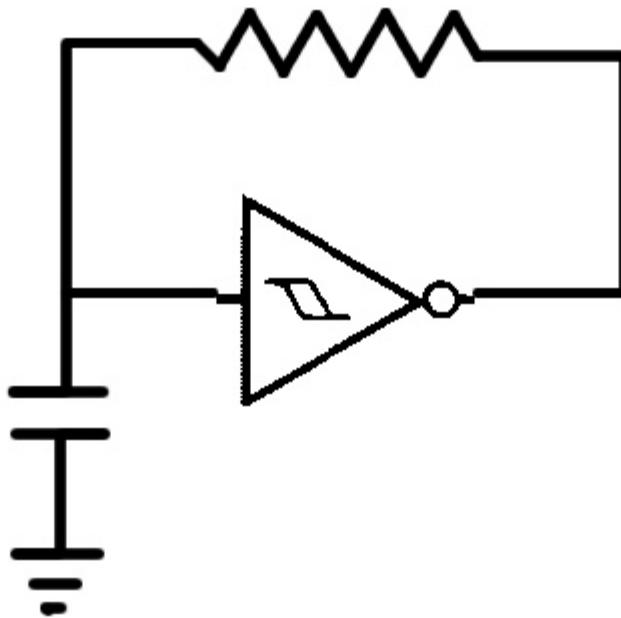By inserting a resistor into the feedback loop and by connecting a capacitor between the input and ground, we can control the rate of the oscillations.




This is called a RC relaxation oscillator. R for resistances and C for capacitance.

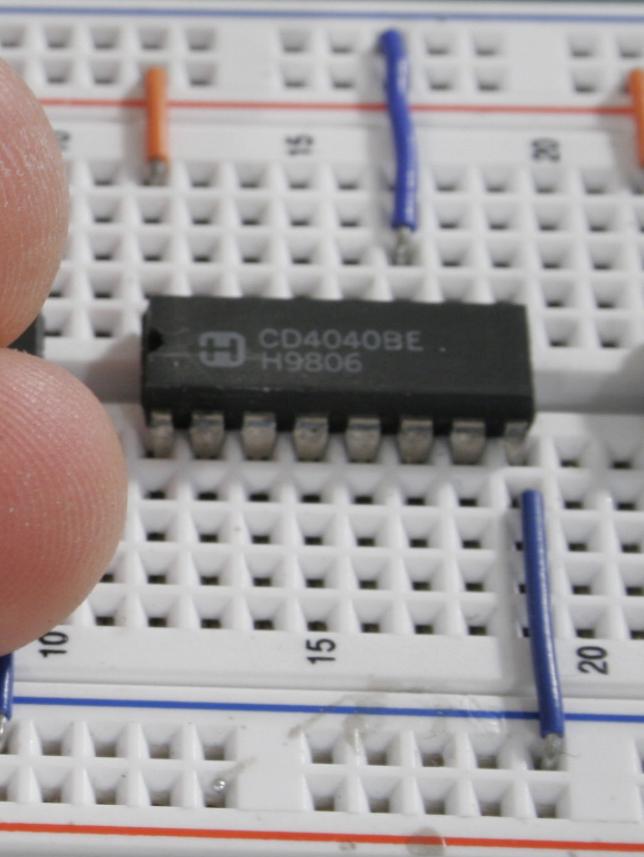**Find the 3.9k ohm resistor.
That's 3900 ohms.**




Find the 3.9k ohm resistor.
That's 3900 ohms.

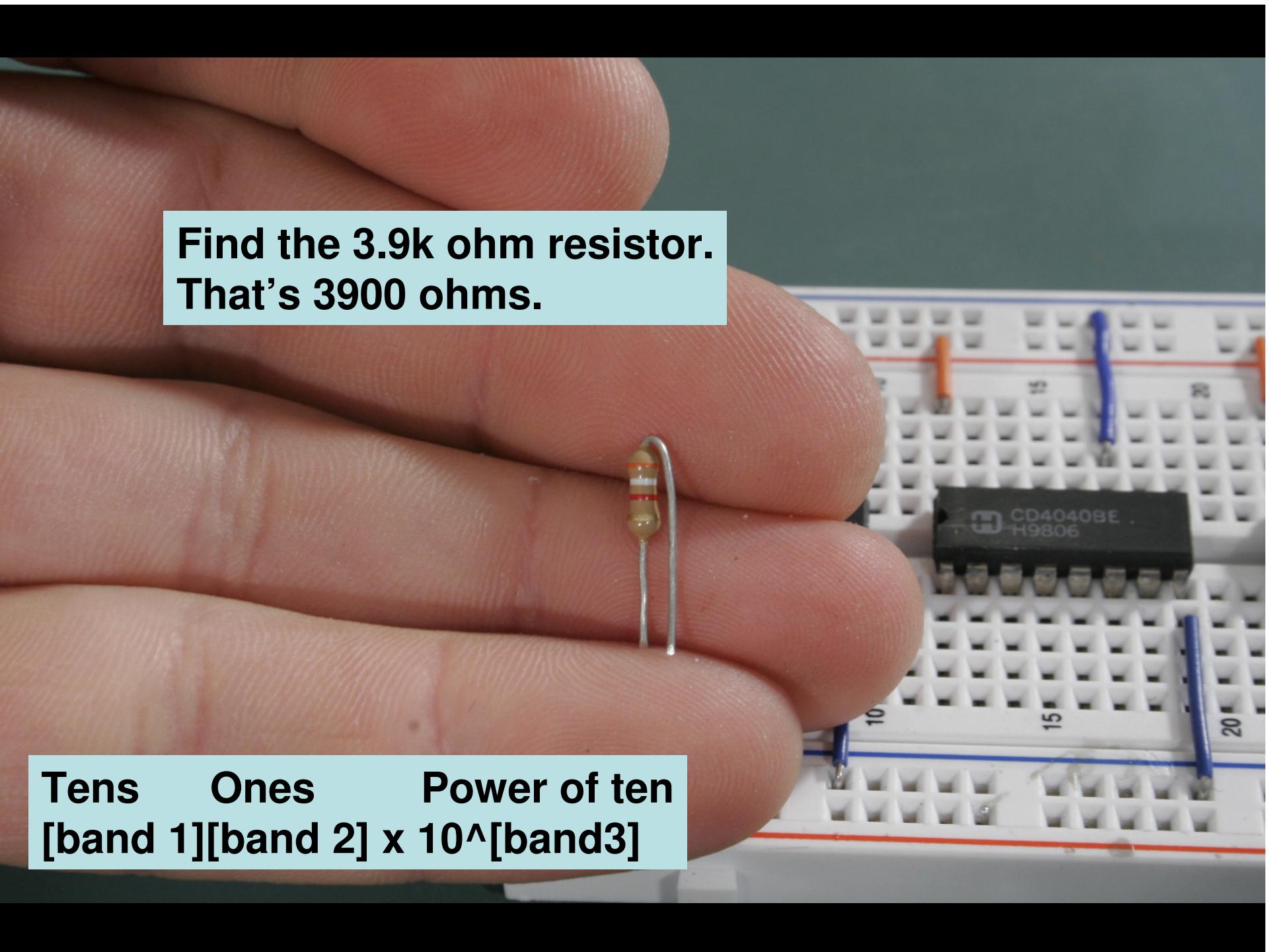Tens Ones Power of ten
[band 1][band 2] x 10^[band3]




Find the 3.9k ohm resistor.
That's 3900 ohms.

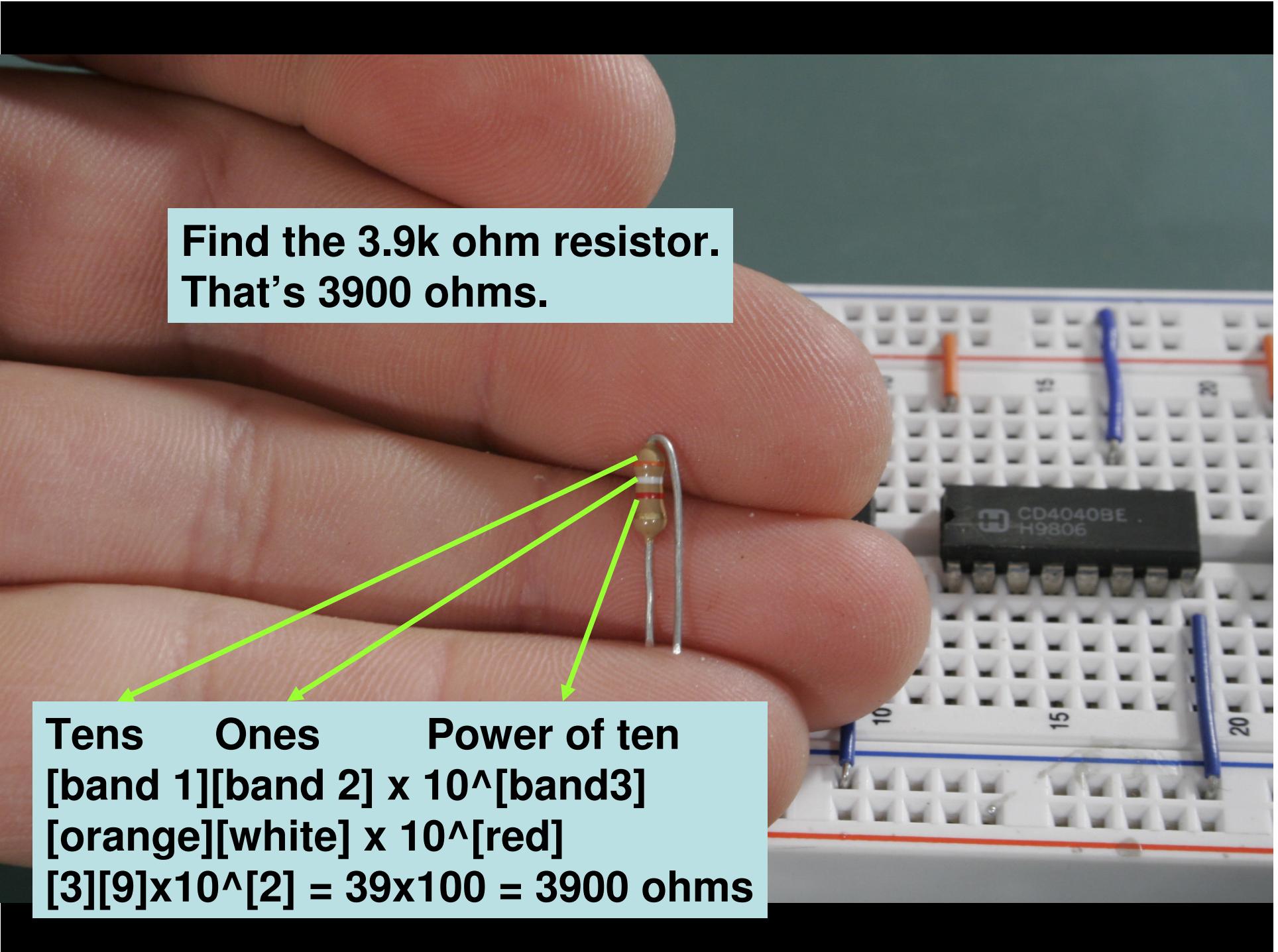
Tens Ones Power of ten
[band 1][band 2] x 10^[band3]
[orange][white] x 10^[red]
[3][9]x10^[2] = 39x100 = 3900 ohms




Place across pins 1 and 2 of the 40106

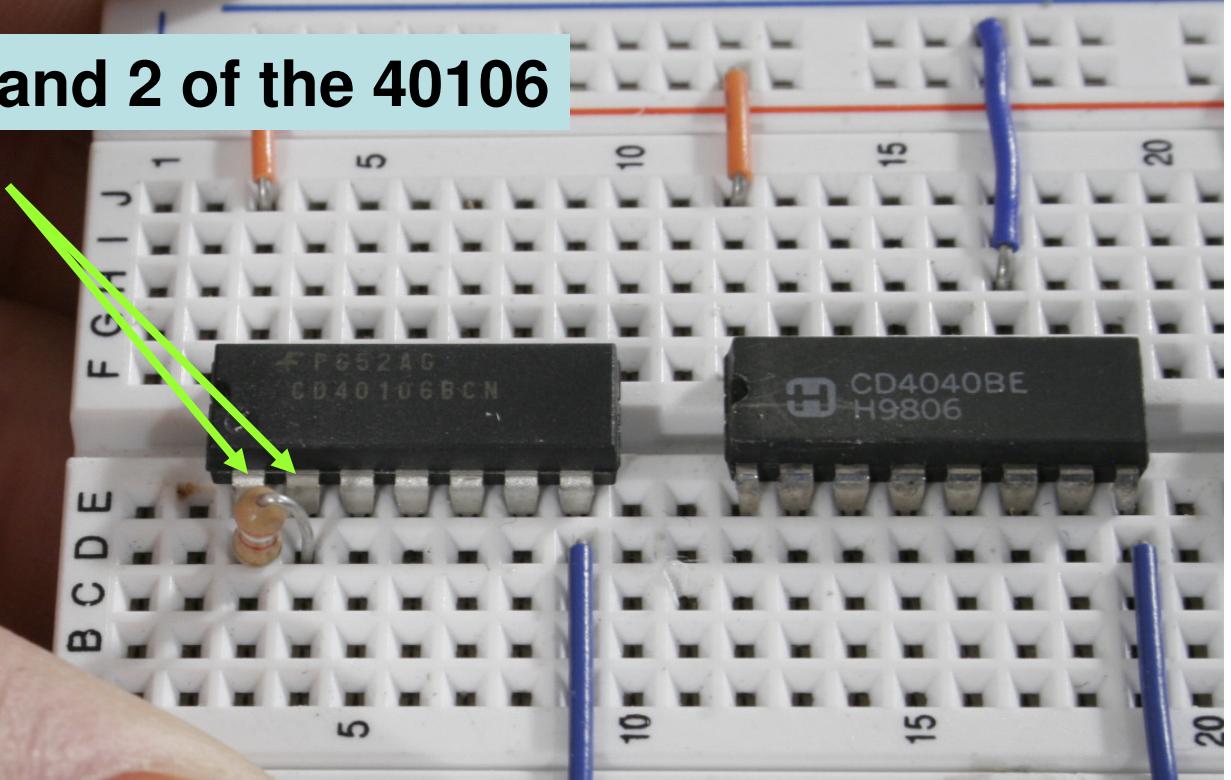

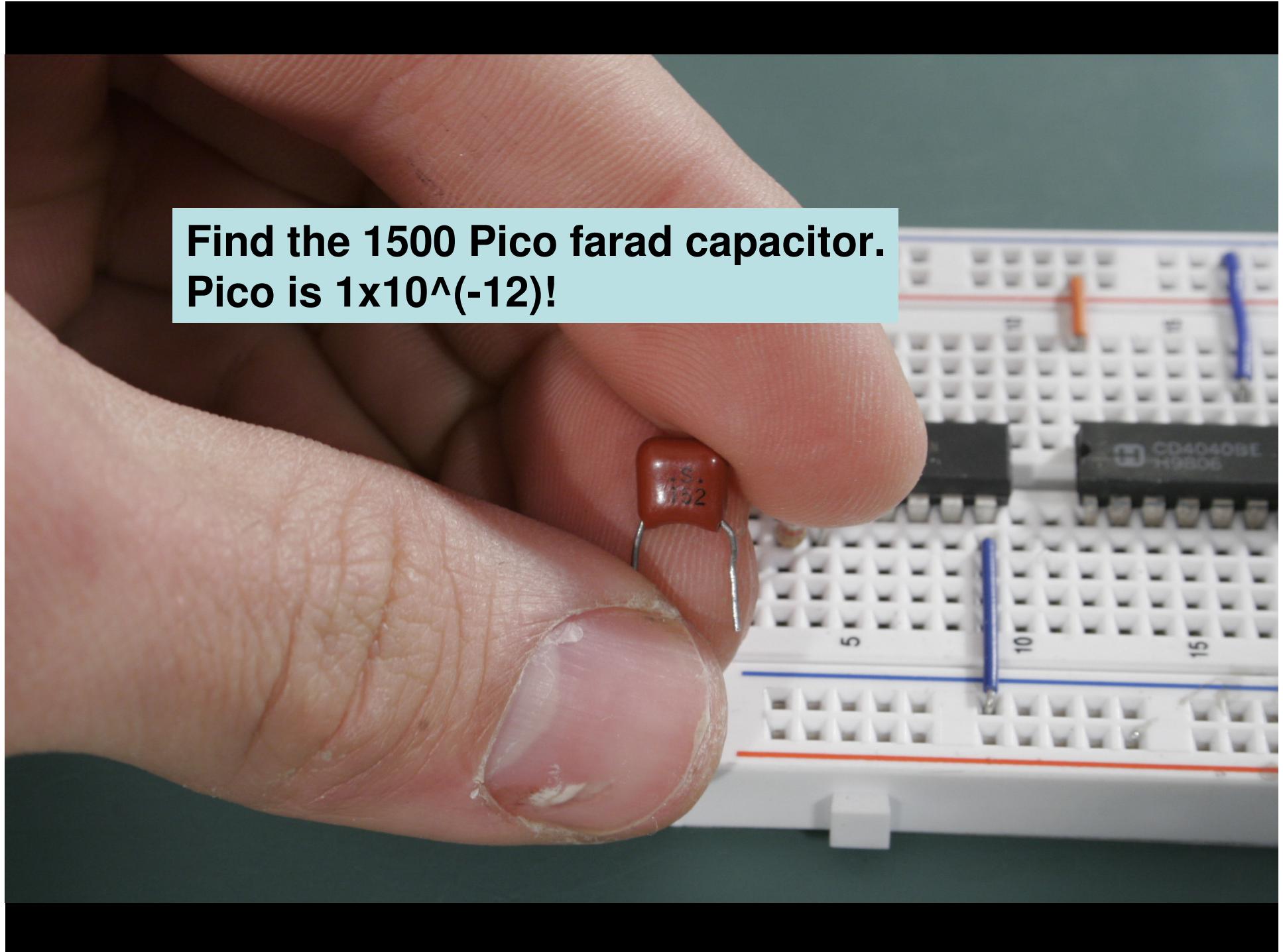**Find the 1500 Pico farad capacitor.
Pico is 1×10^{-12} !**



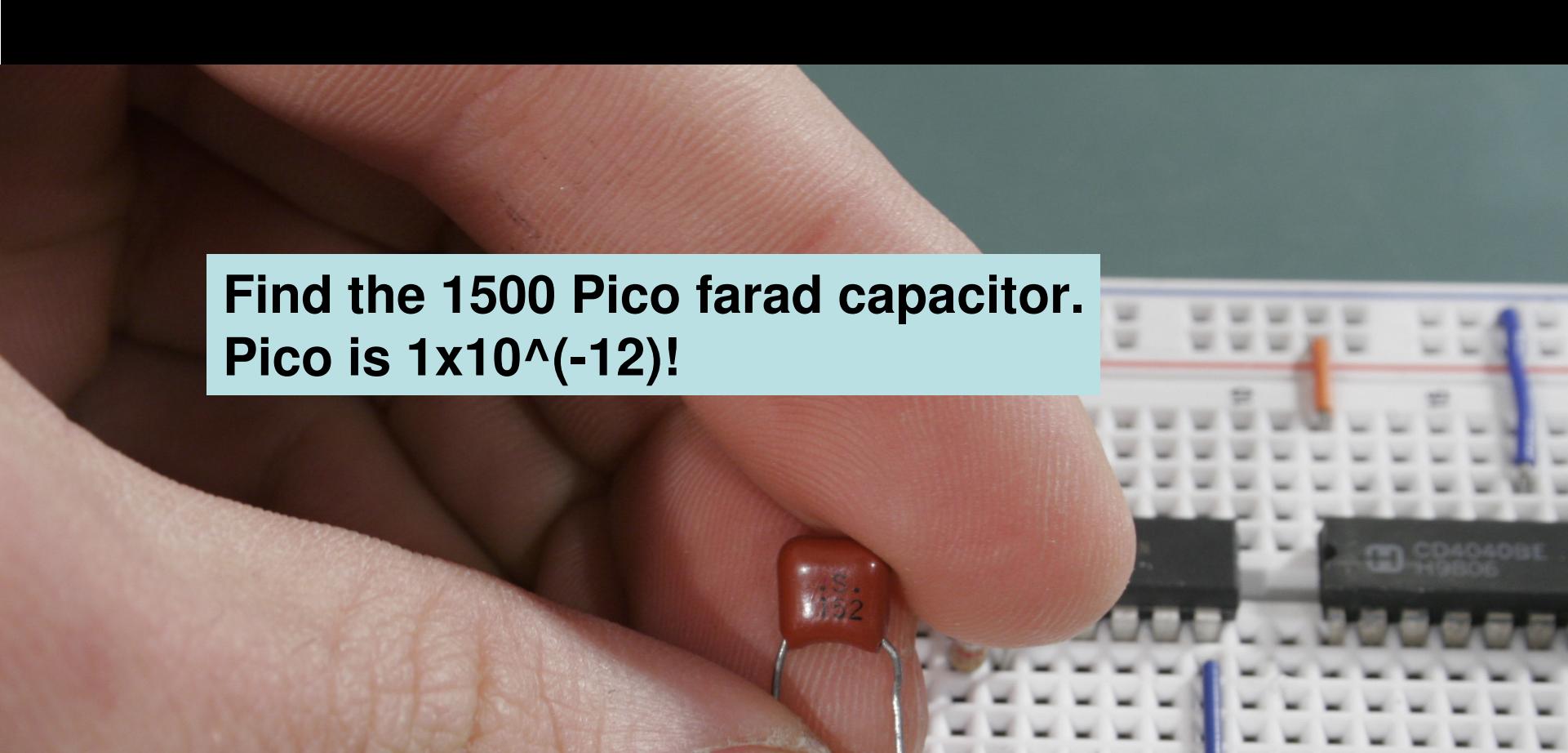


**Find the 1500 Pico farad capacitor.
Pico is 1×10^{-12} !**

Formula:


Tens	Ones	Power of ten
[1st digit]	[2nd digit]	$\times 10^{(-12+[3^rd\ digit])}$

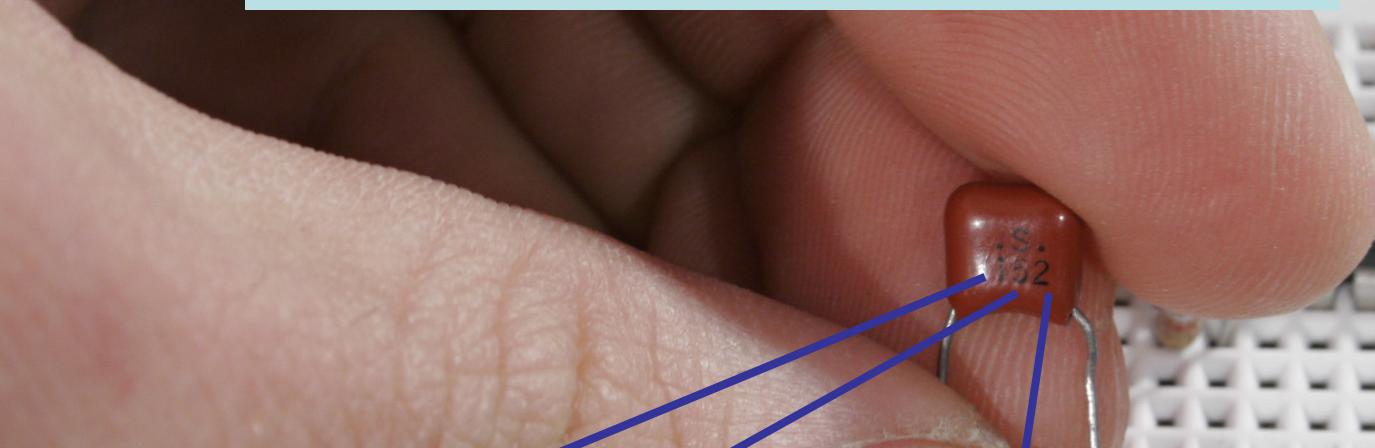
Find the 1500 Pico farad capacitor.
Pico is 1×10^{-12} !




Formula:
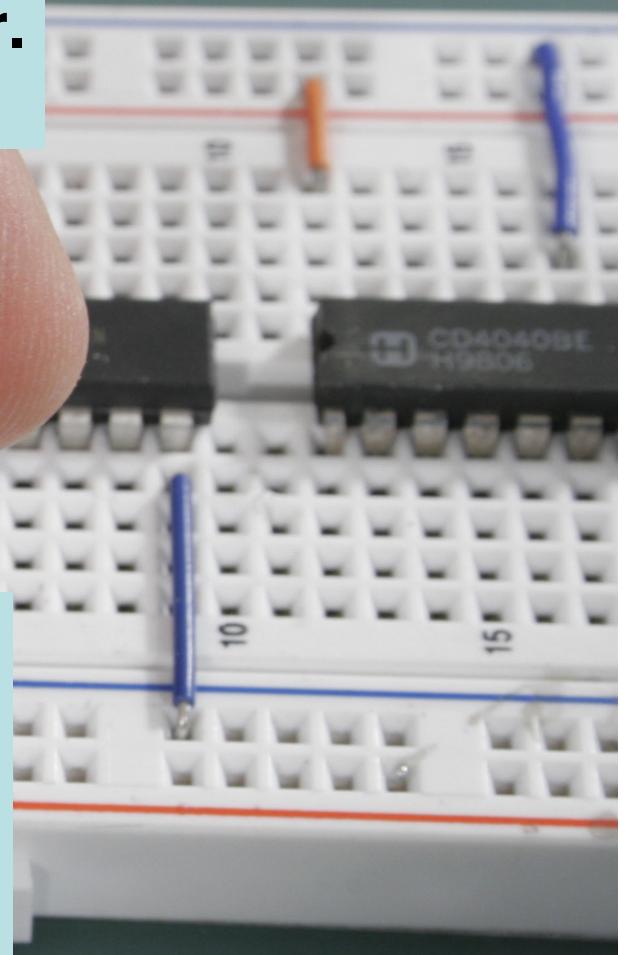
$$\begin{array}{ccc} \text{Tens} & \text{Ones} & \text{Power of ten} \\ [1^{\text{st}} \text{ digit}][2^{\text{nd}} \text{ digit}] \times 10^{(-12+[3^{\text{rd}} \text{ digit}])} \\ [1][5] \times 10^{(-12+[2])} \\ 15 \times 10^{-10} = .0000000015 \text{ farads} = 1500\text{pf} \end{array}$$



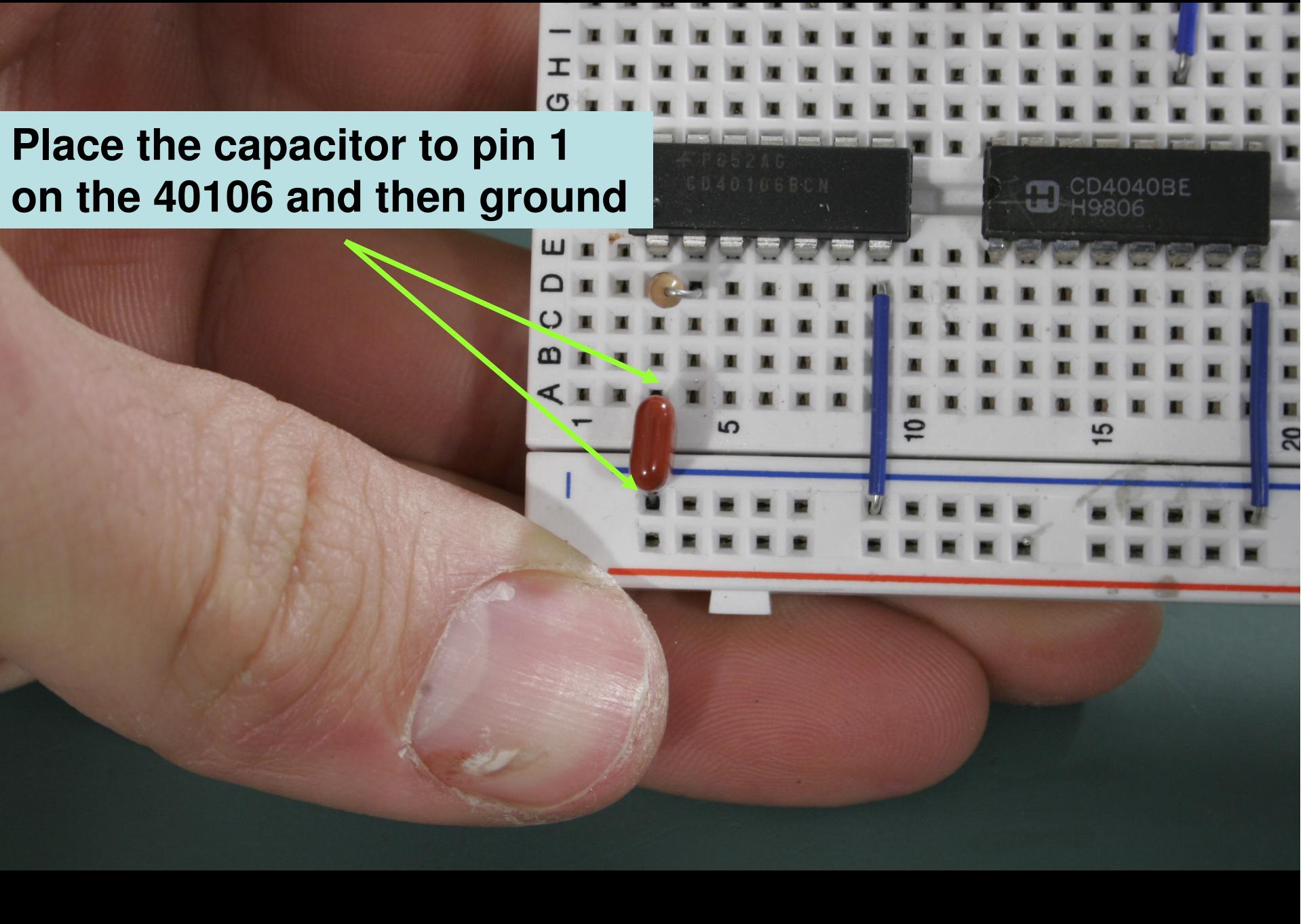


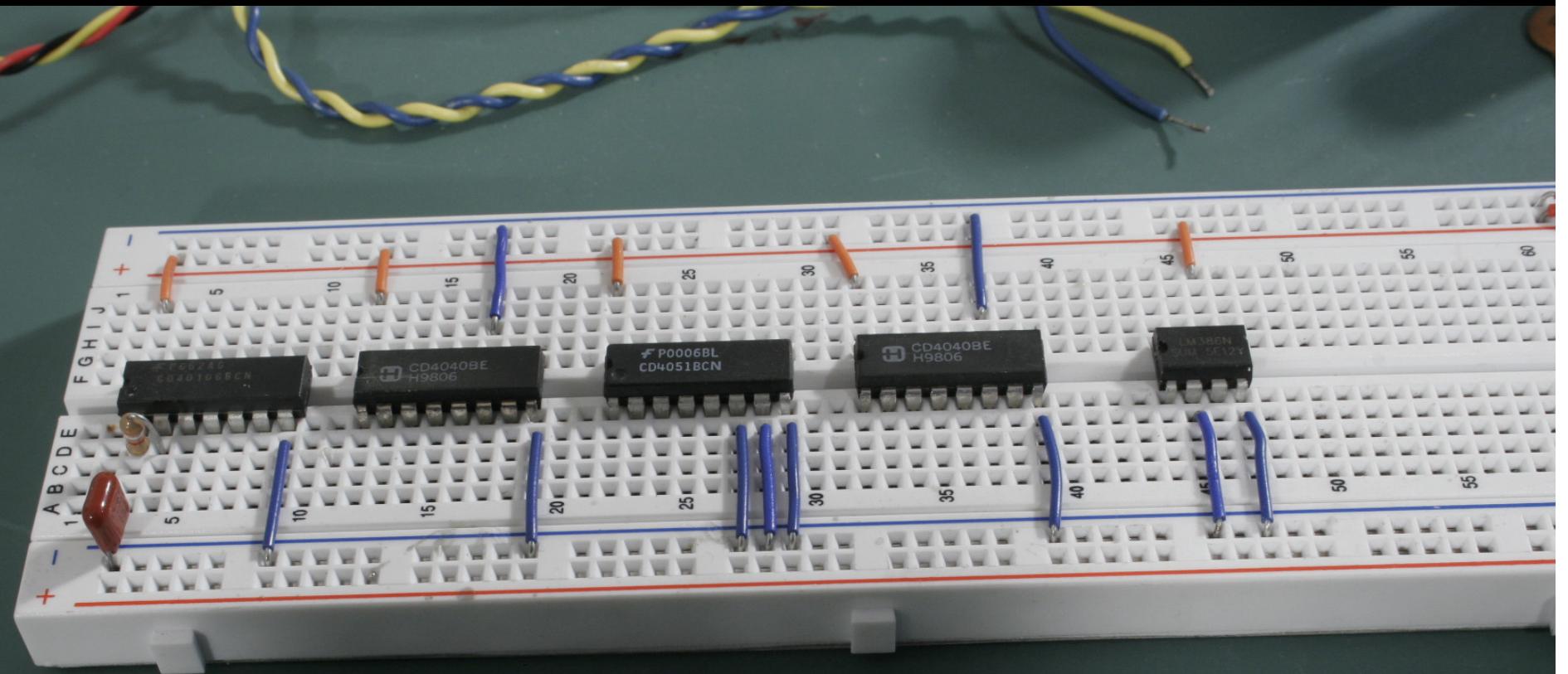


Next we connect the oscillator to one of the 4040 counters



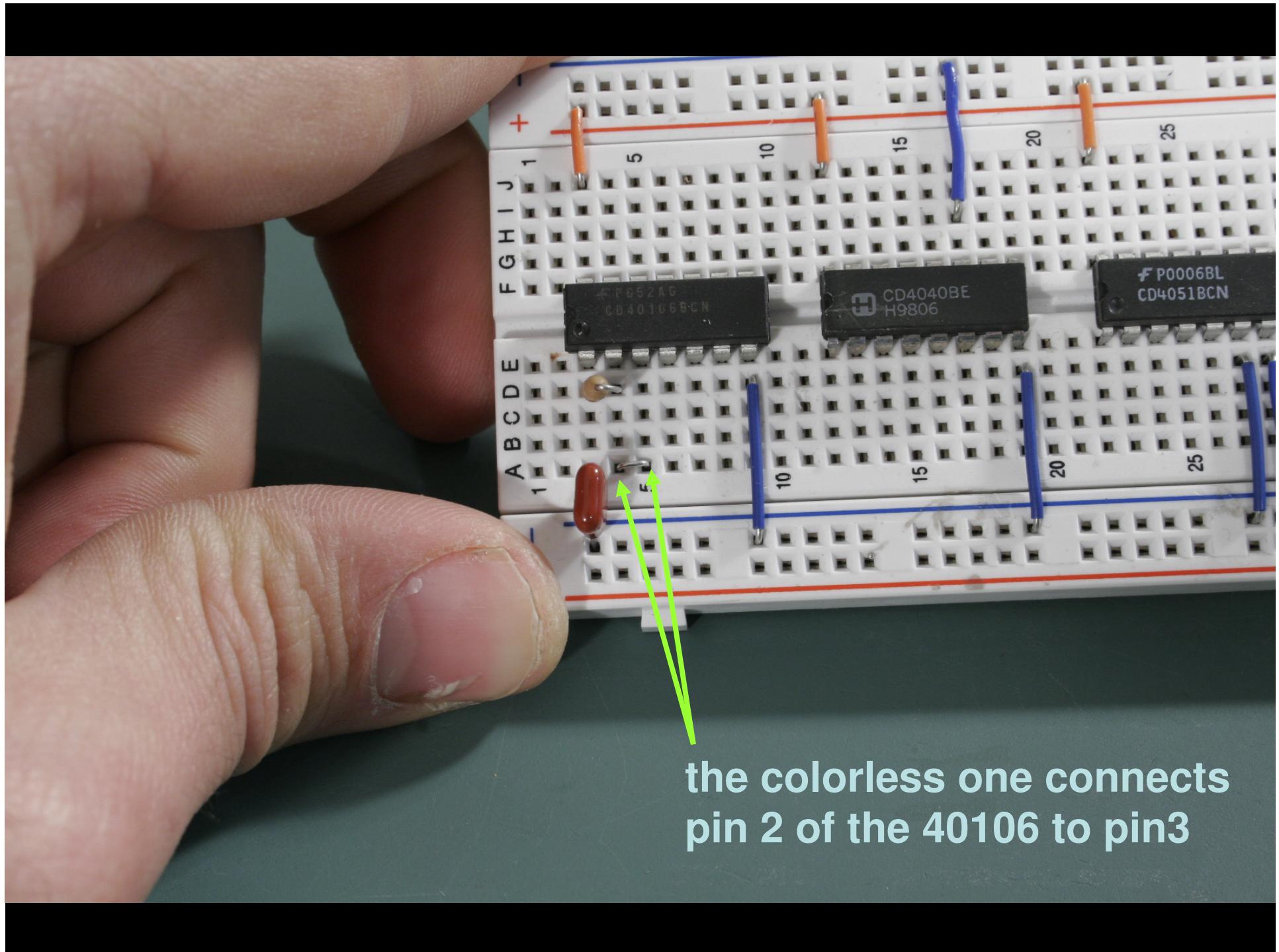
grab one each: purple, green, orange, and colorless jumpers



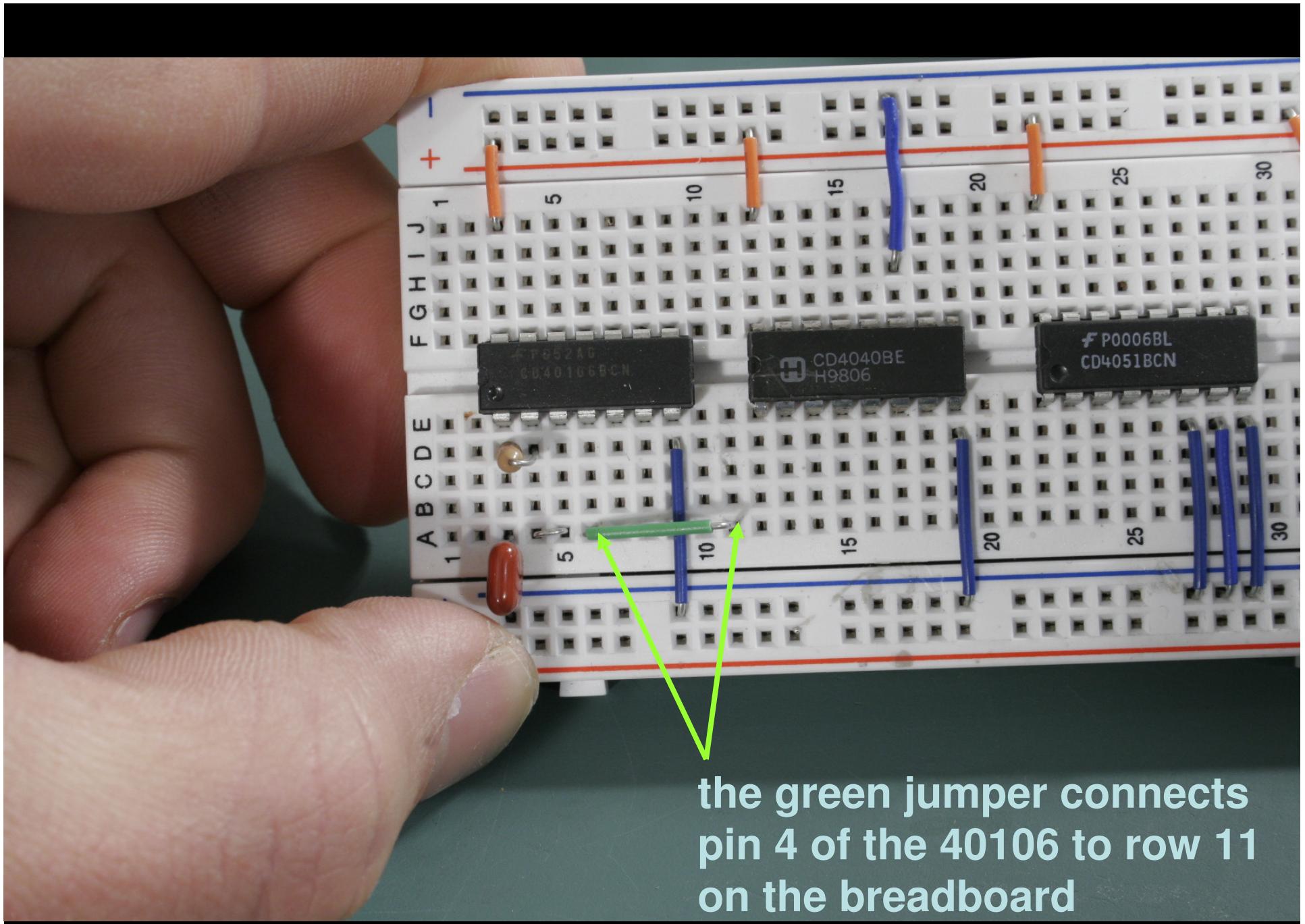



the green jumper connects
pin 4 of the 40106 to row 11
on the breadboard

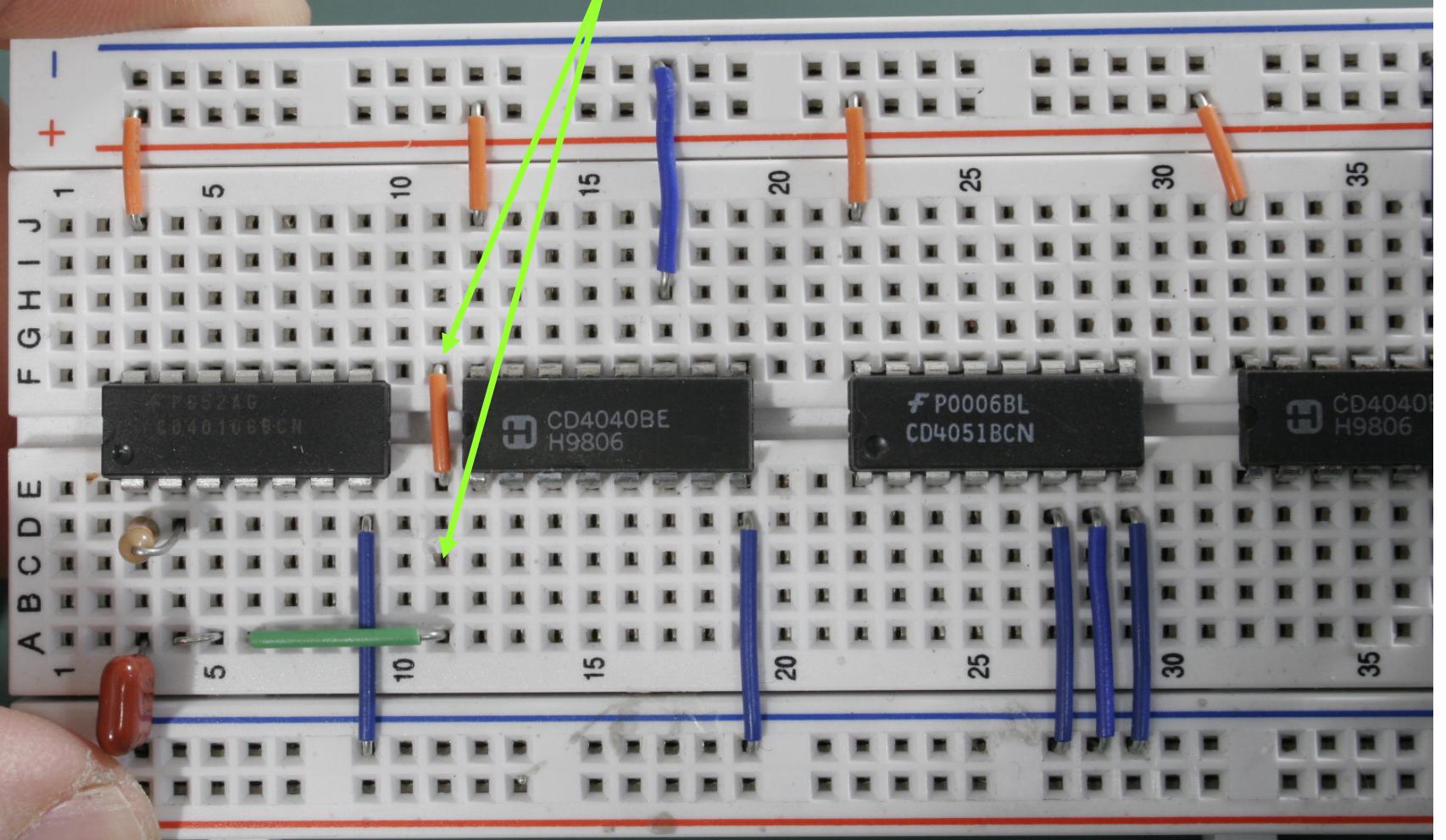
the orange jumper bridges
row 11 across the trough
of the breadboard




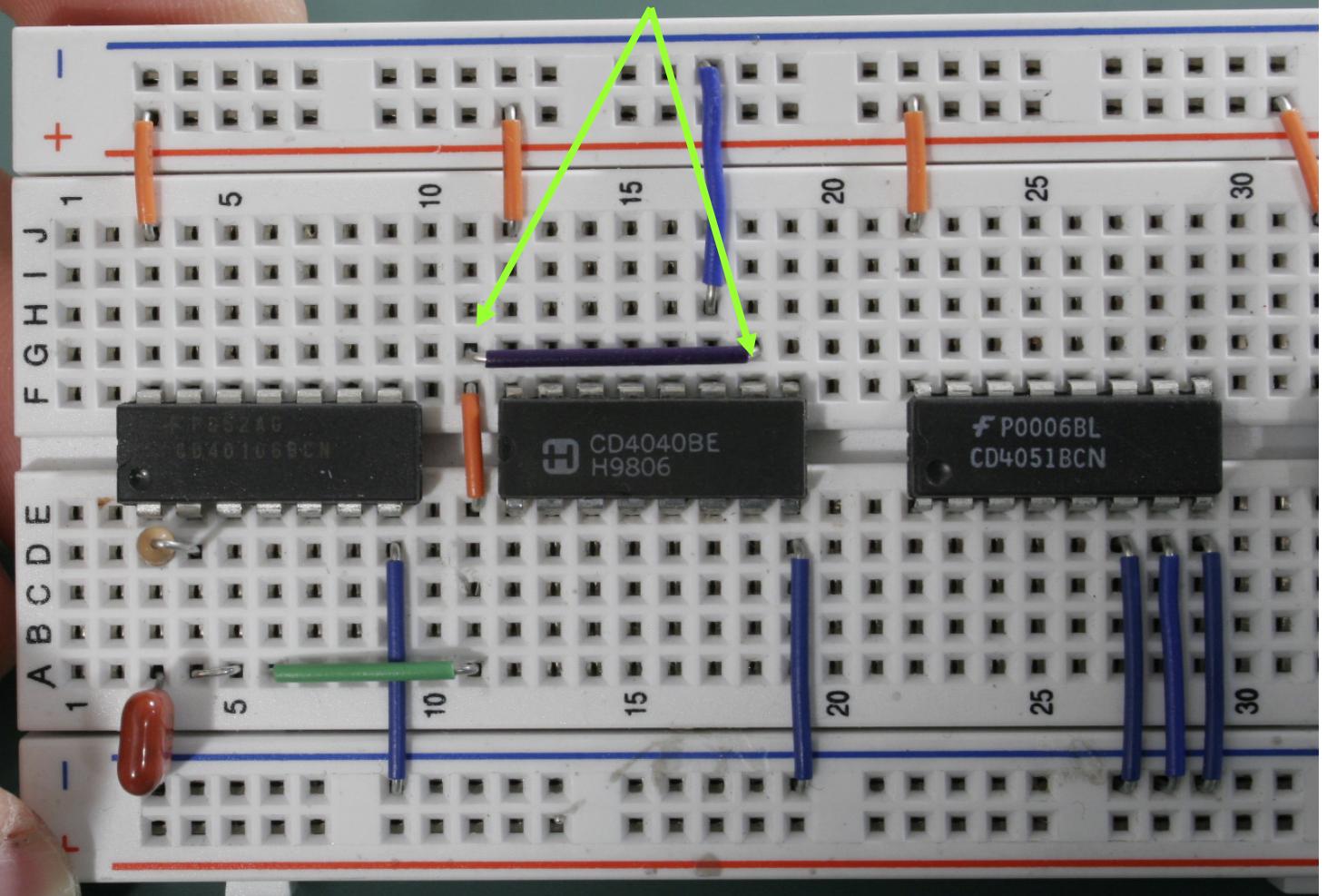
the purple jumper connects
row 11 to pin 10 on the 4040



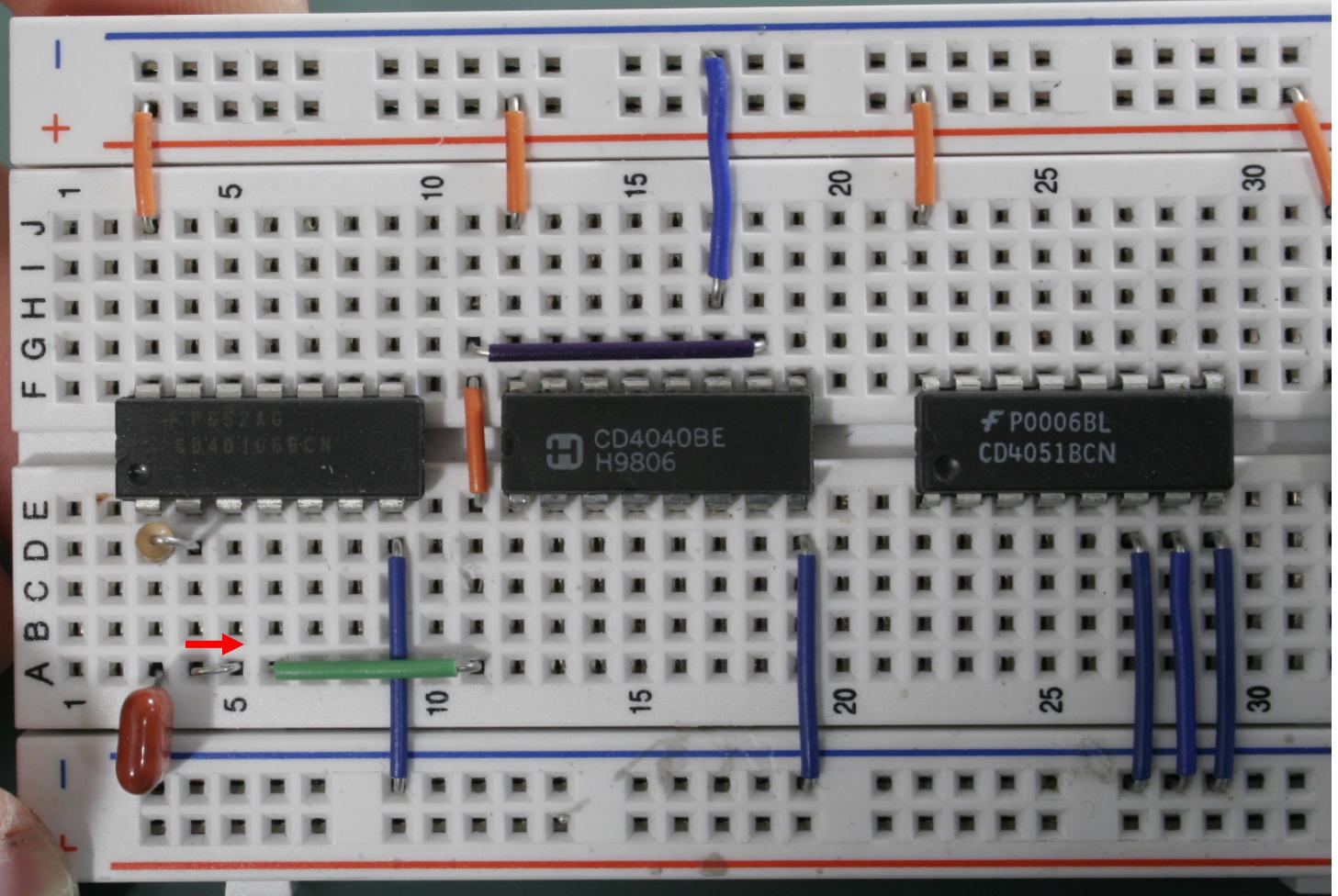


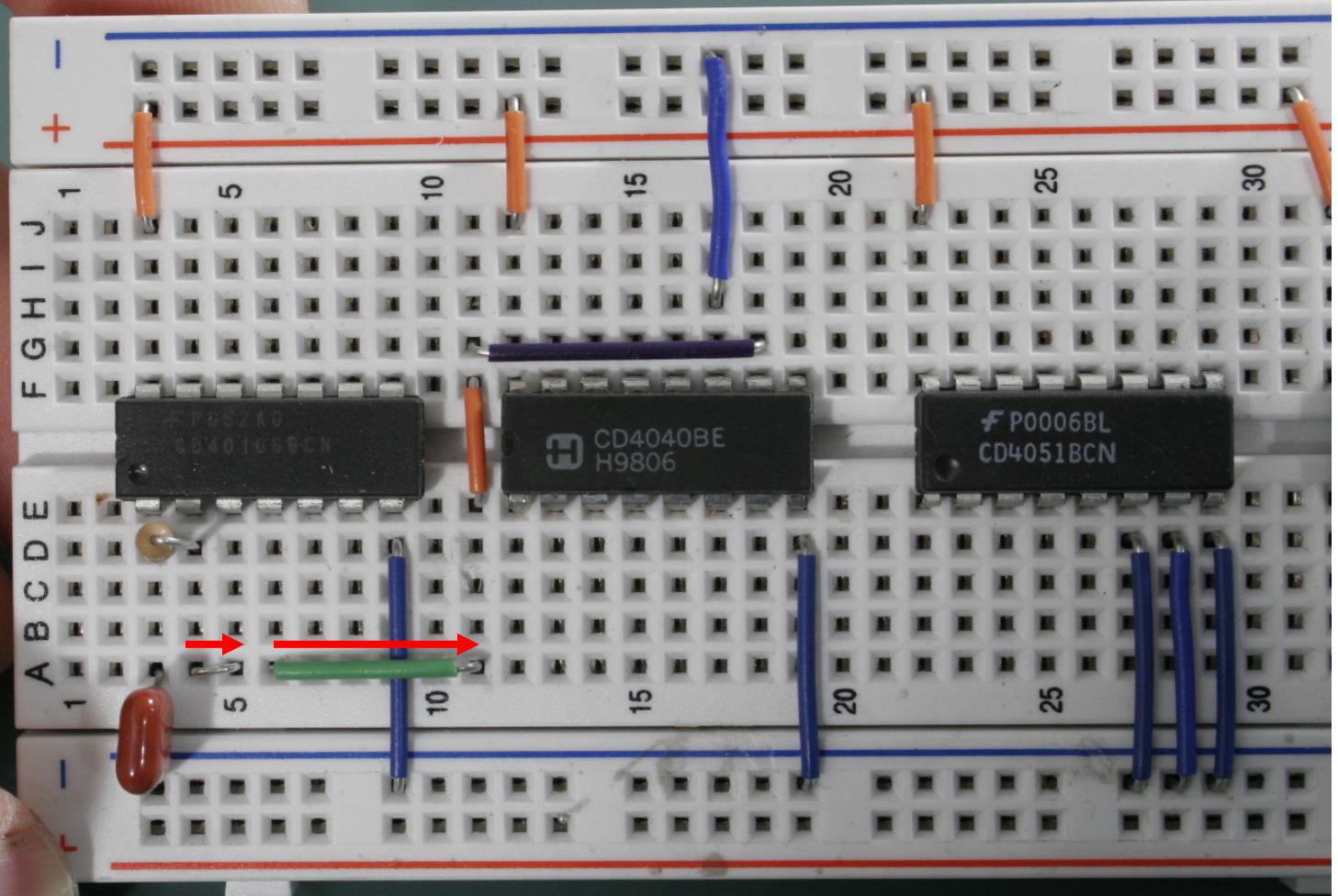

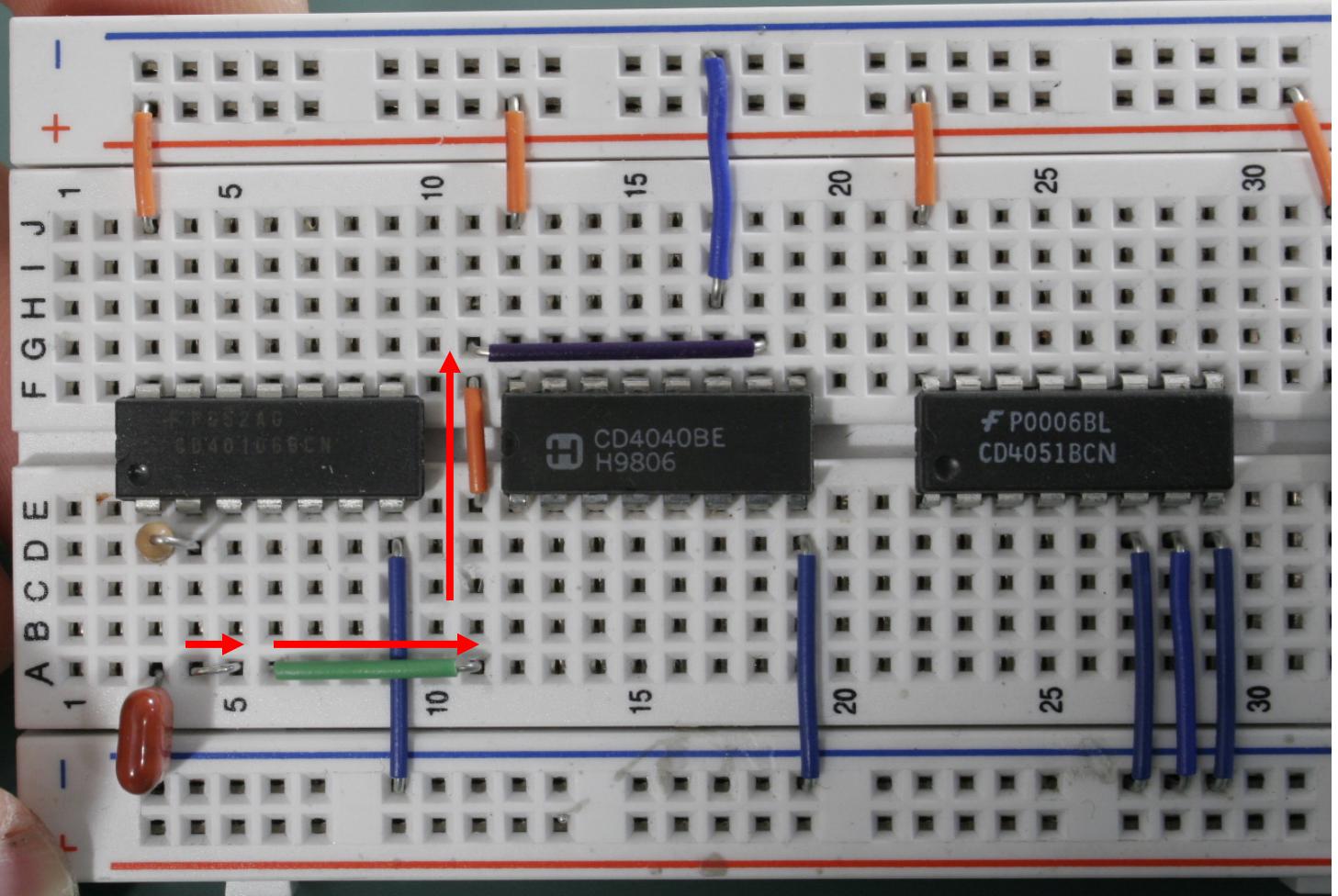


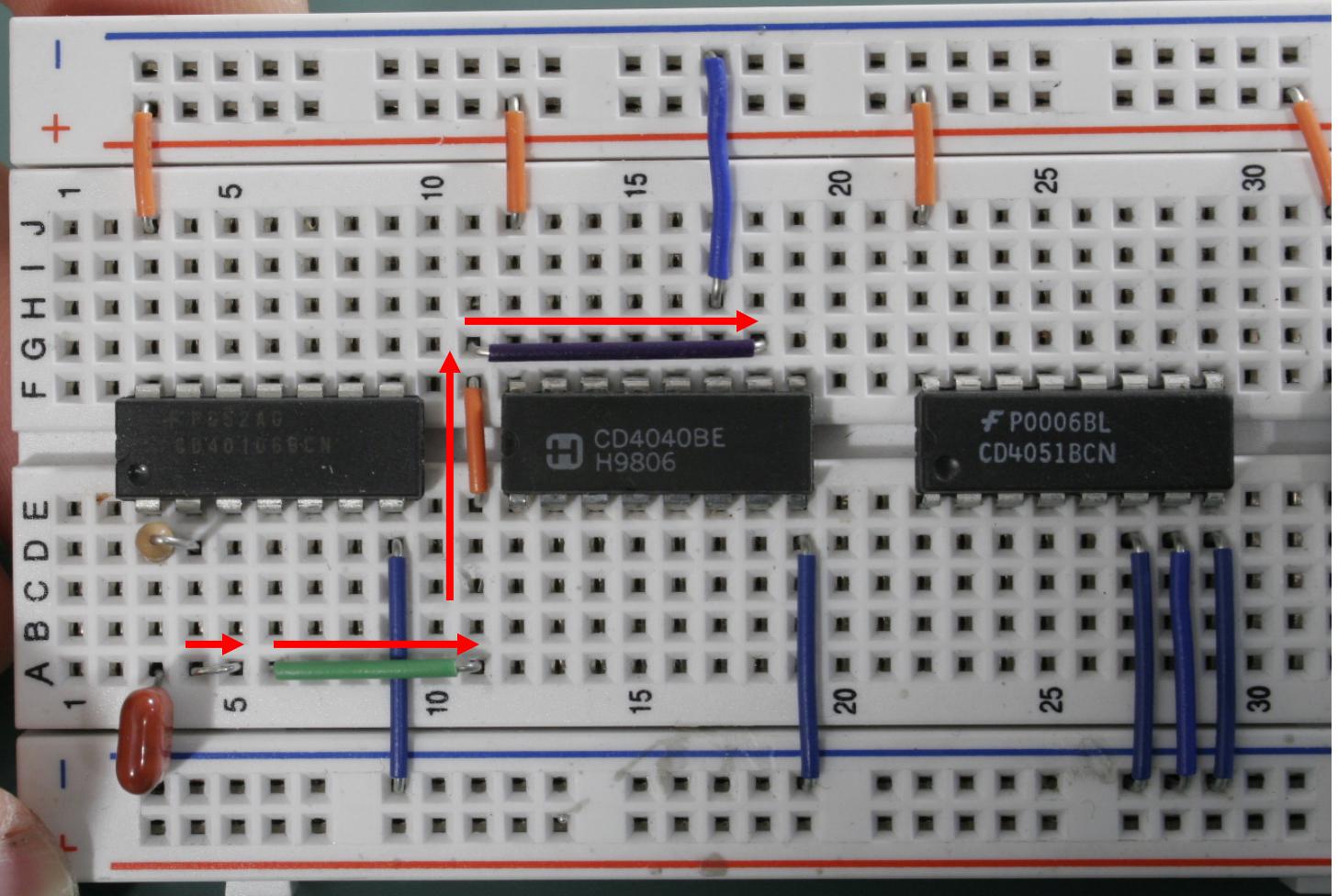

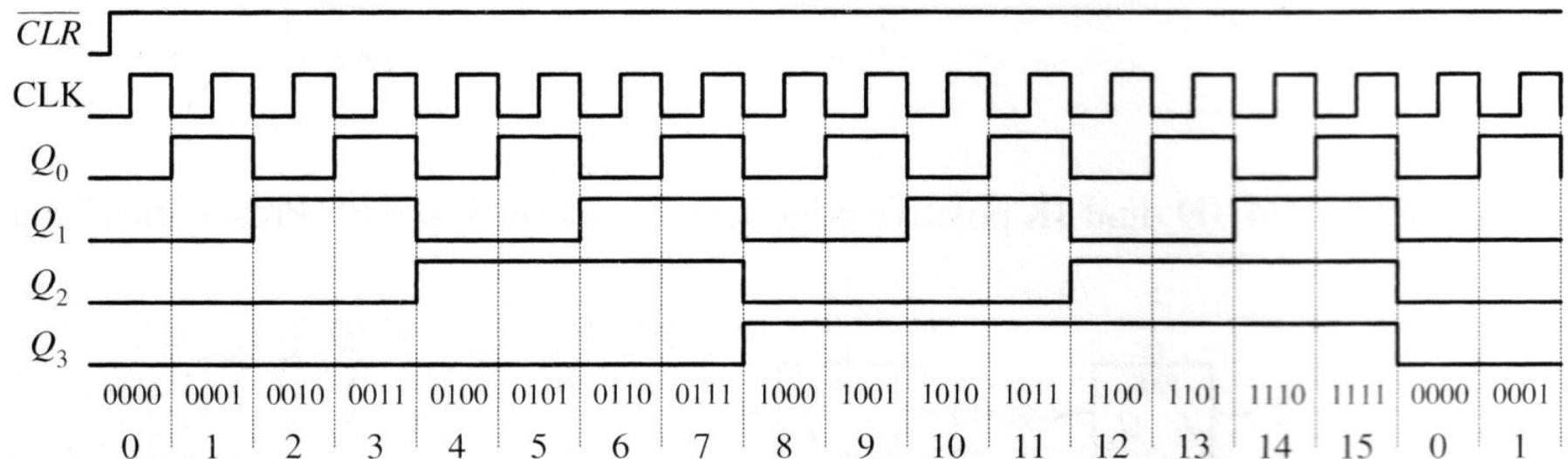**The 4040 binary counter has the following output.
The frequency of output Q0 is $\frac{1}{2}$ the clock,
Q1 is $\frac{1}{4}$, Q2 is 1/8th, Q3 is 1/16th, and so on...**



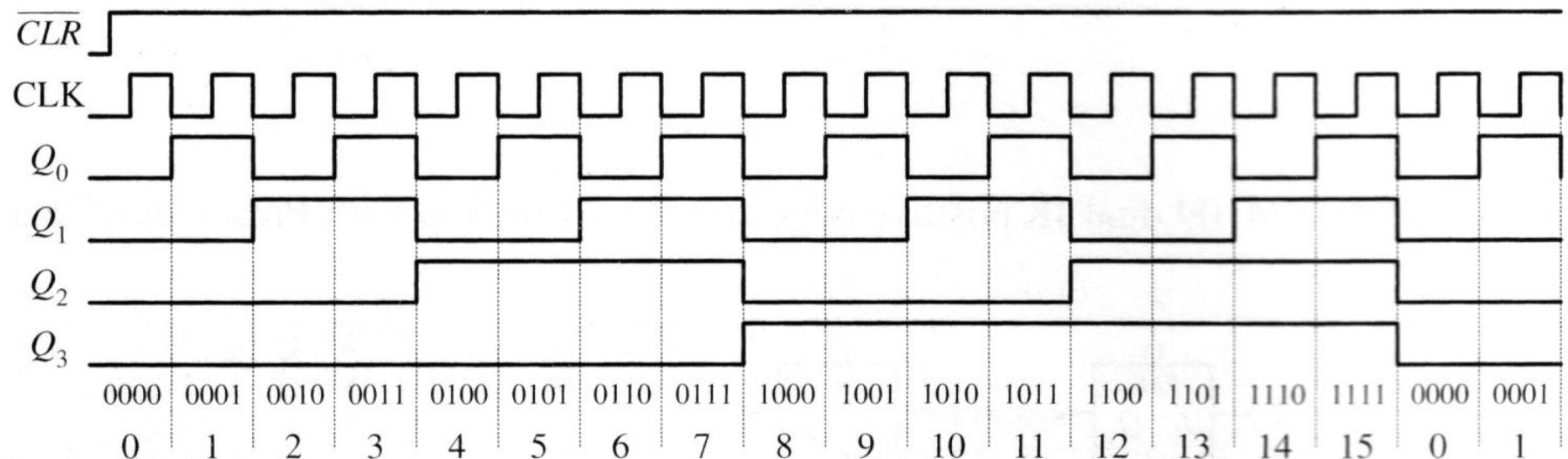**Each output is a sub-octave of the clock input.
Each output is one octave lower than the previous one.**



**Gather four 10k ohm resistors.
That's 10,000 ohms!**




**Gather four 10k ohm resistors.
That's 10,000 ohms!**




Color Code: Brown Black Orange Gold

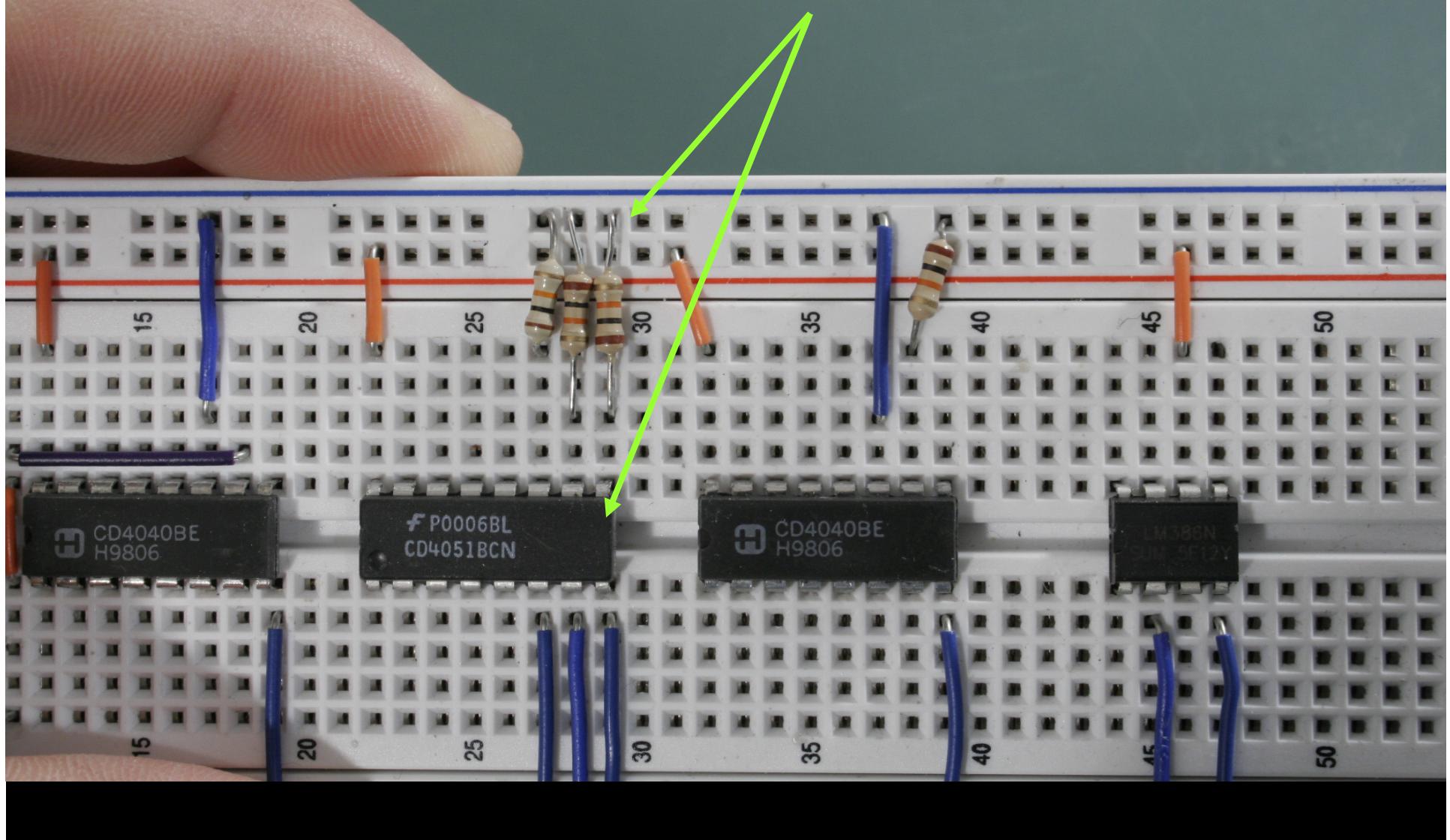
Connect pins 9,10, and 11 on the 4051
to ground via the 10k ohm resistors.



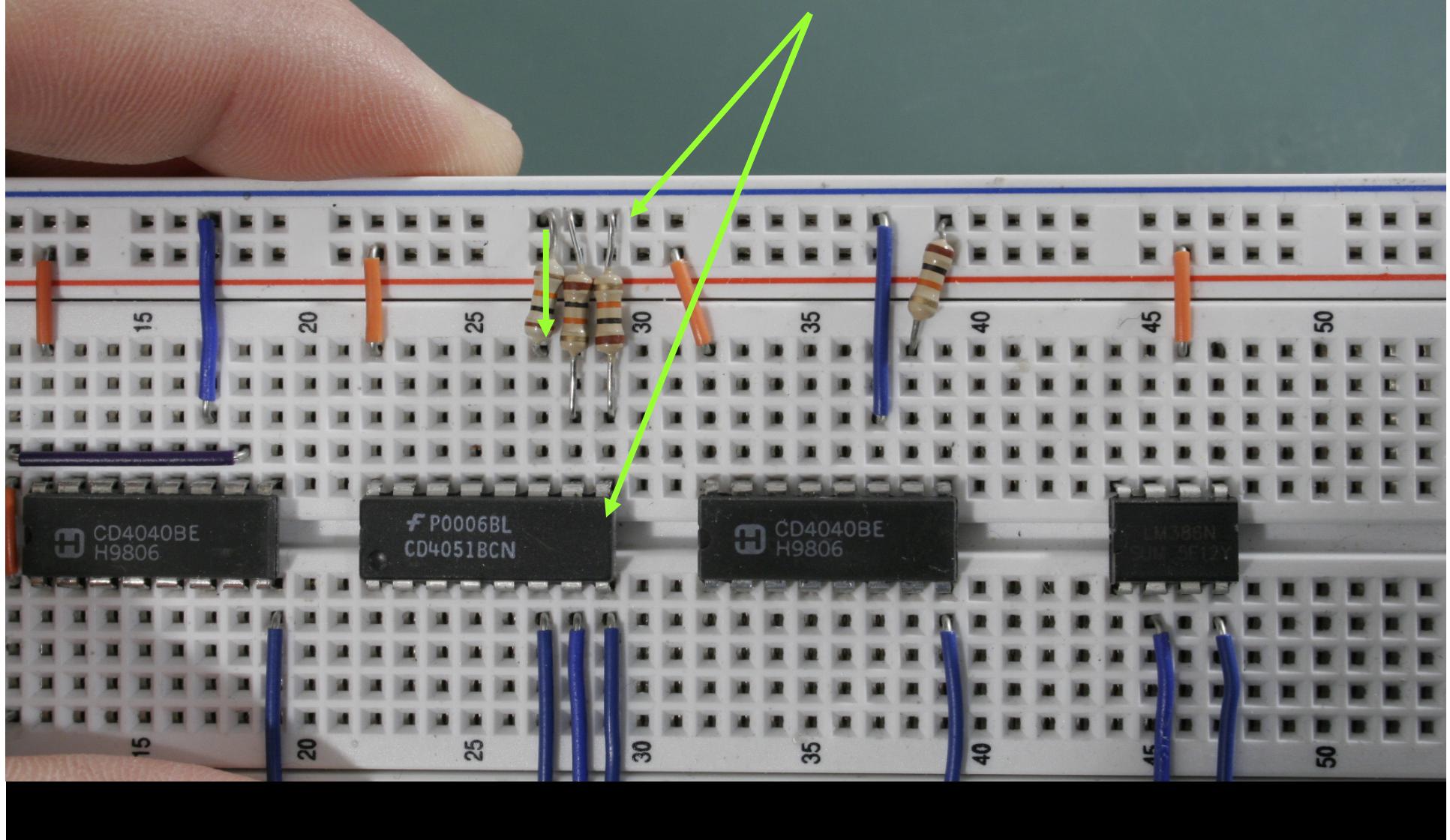
Connect pins 9,10, and 11 on the 4051
to ground via the 10k ohm resistors.



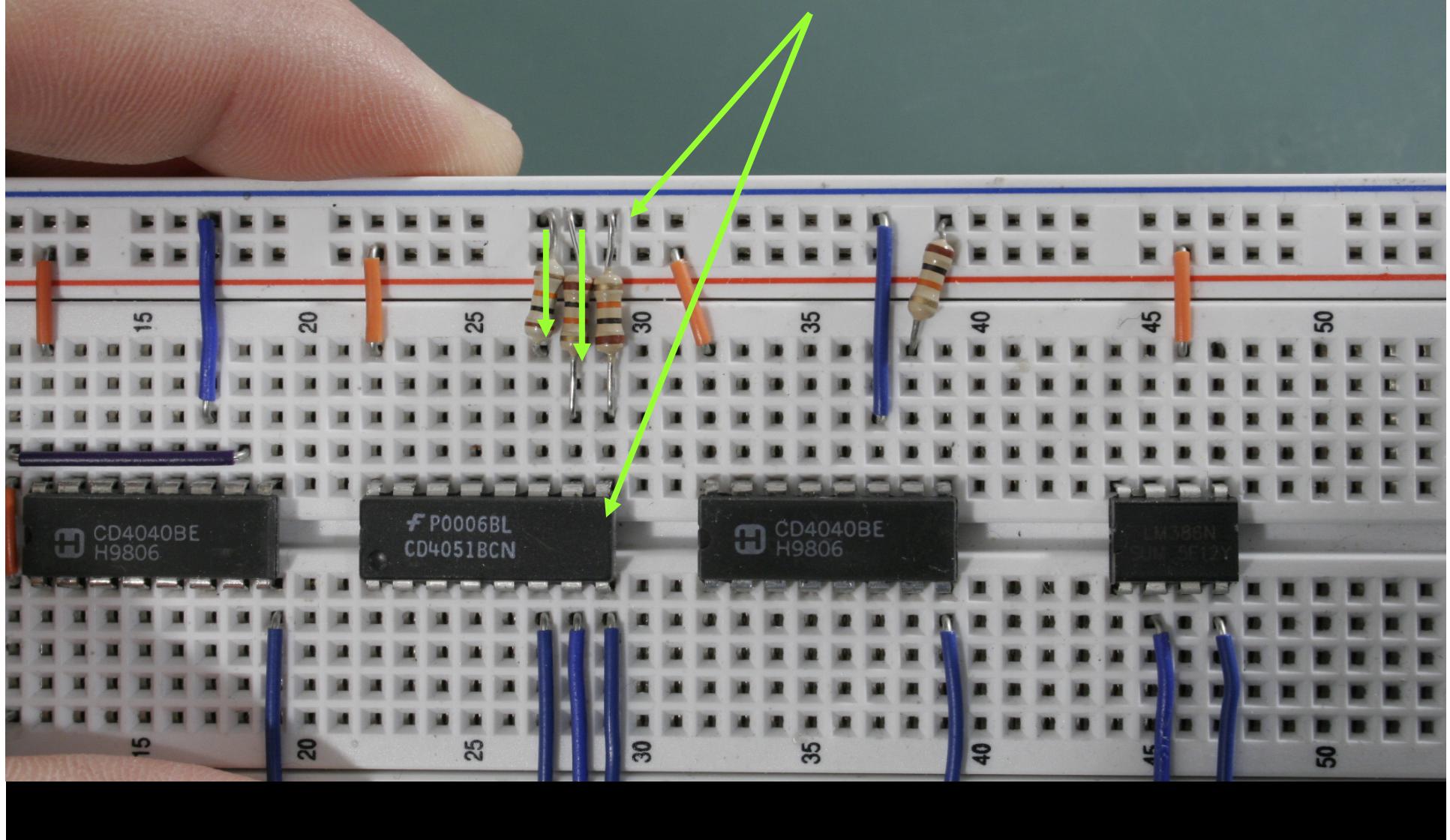
Connect pins 9,10, and 11 on the 4051
to ground via the 10k ohm resistors.




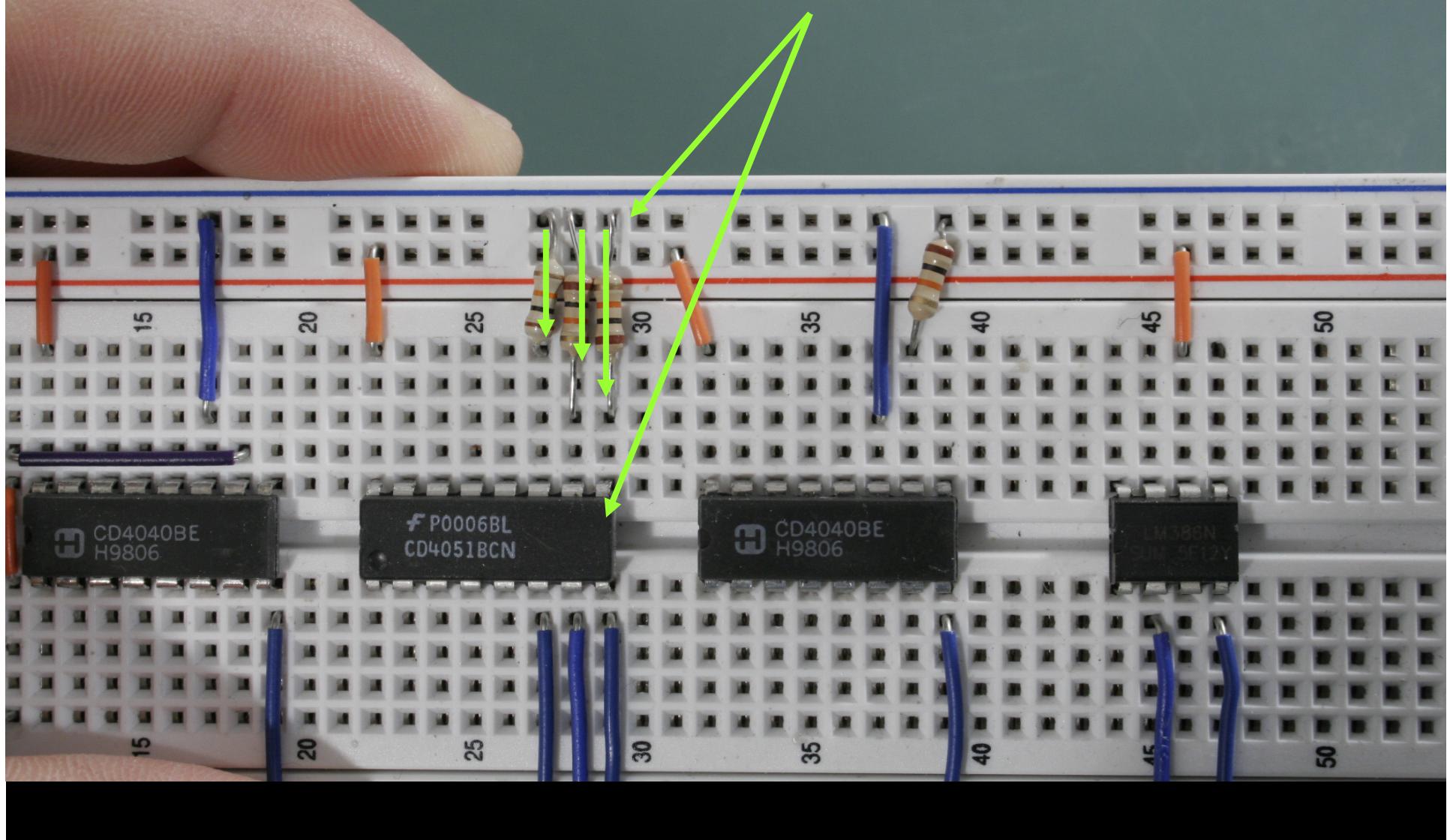Connect pins 9,10, and 11 on the 4051
to ground via the 10k ohm resistors.





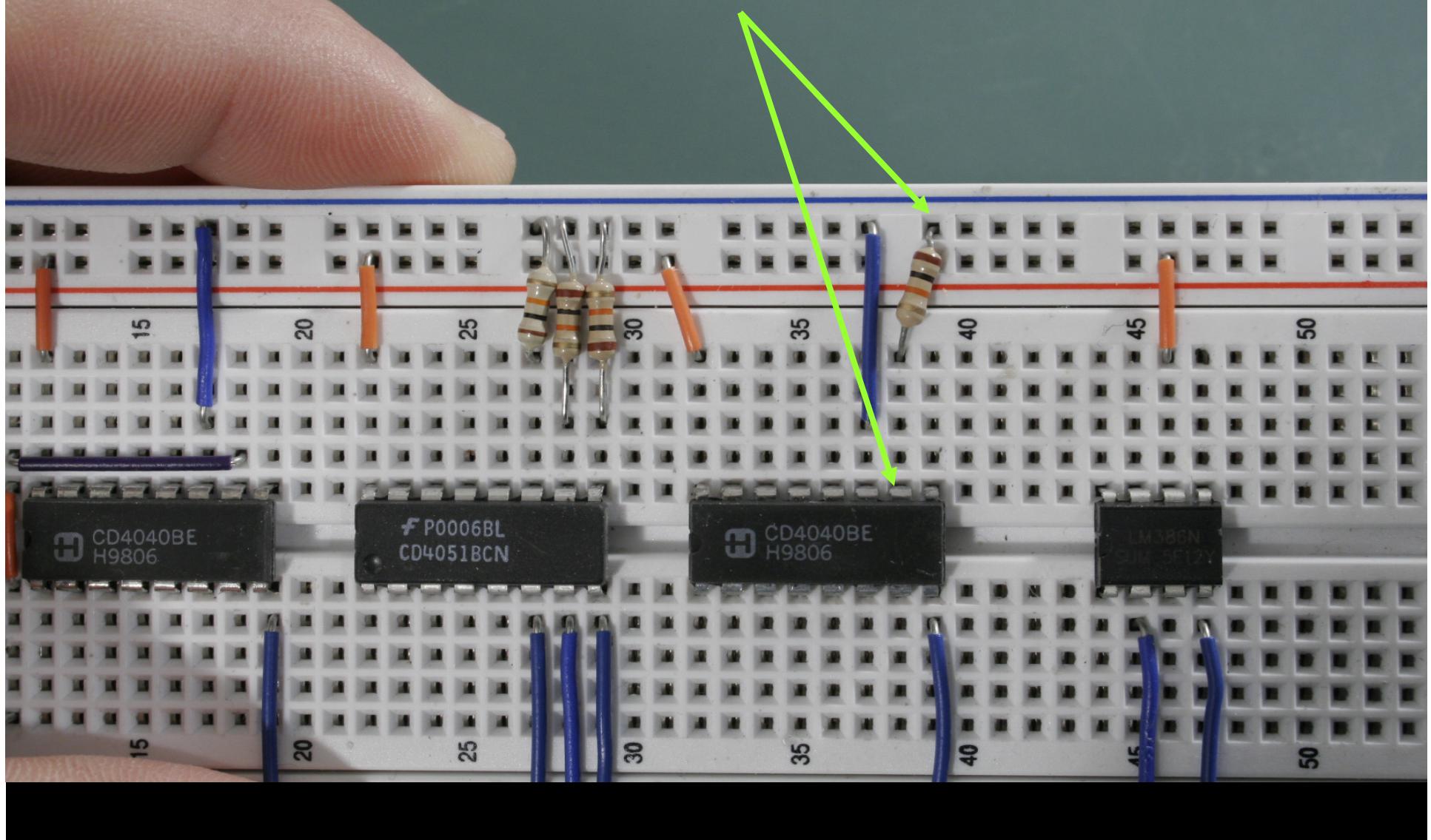Connect pin 10 on the 4040
to ground via the last 10k ohm resistor.






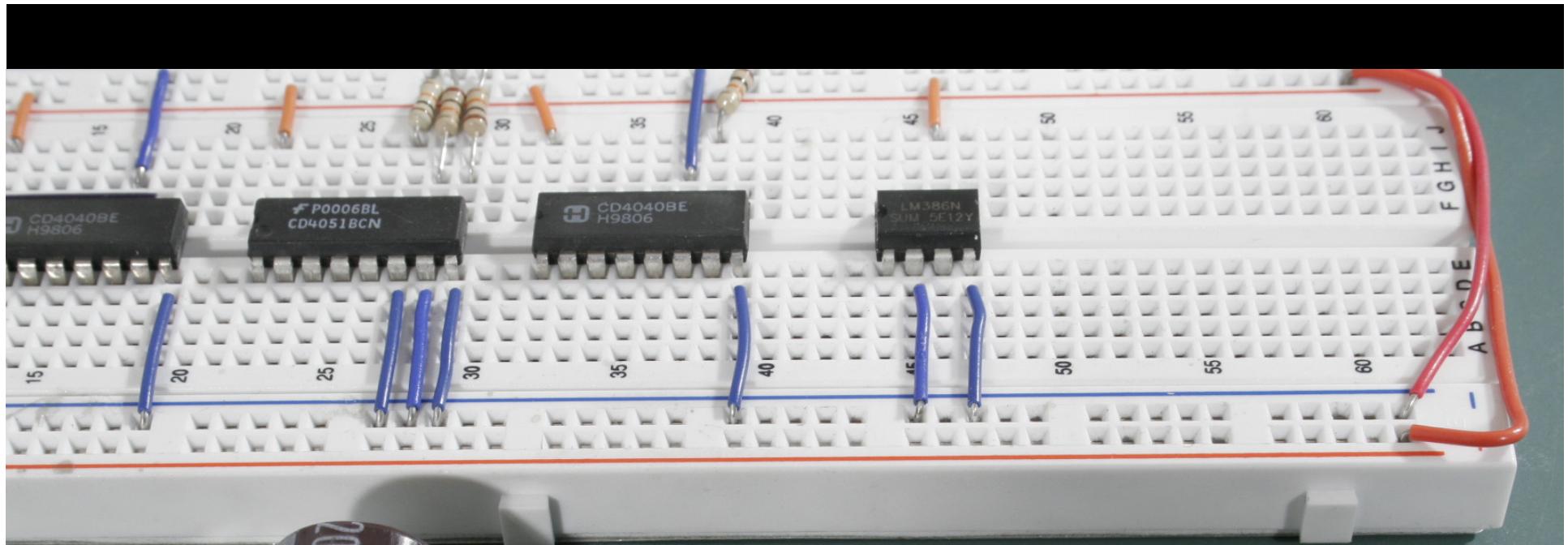




Gather the following:

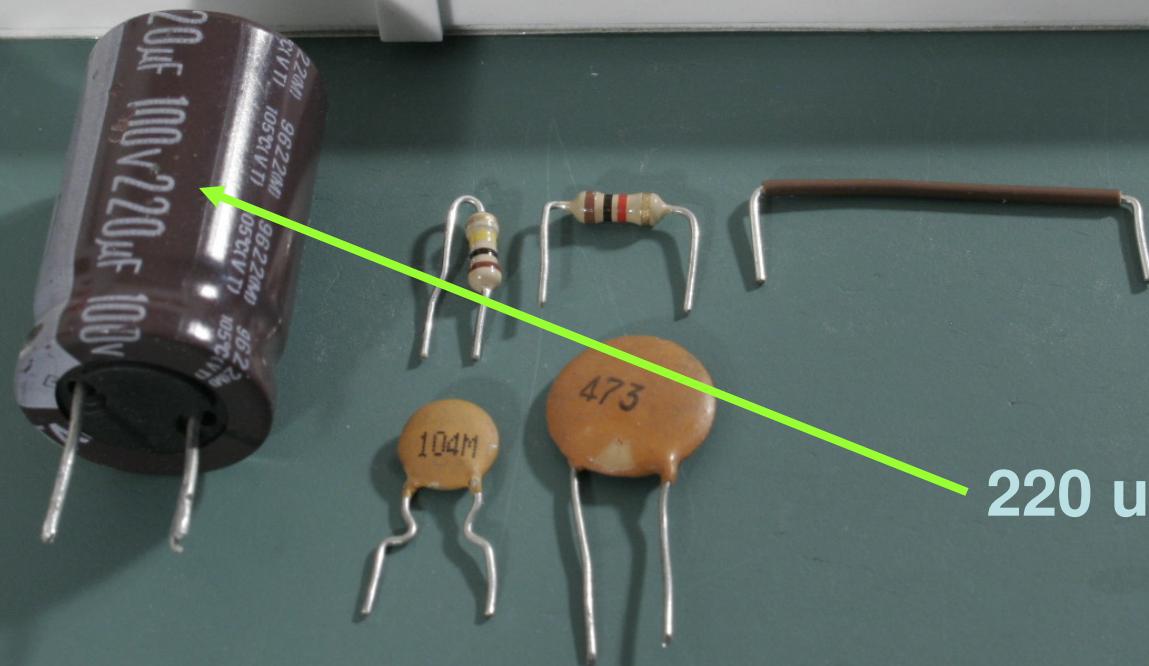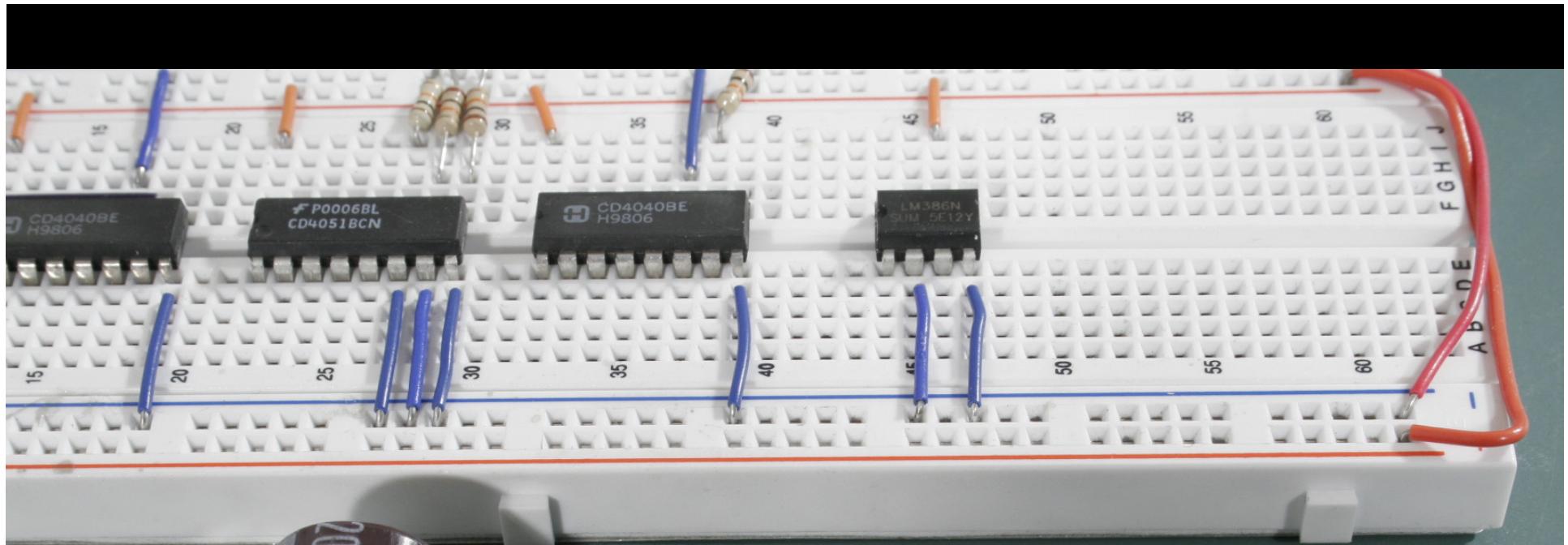



220 uF Capacitor

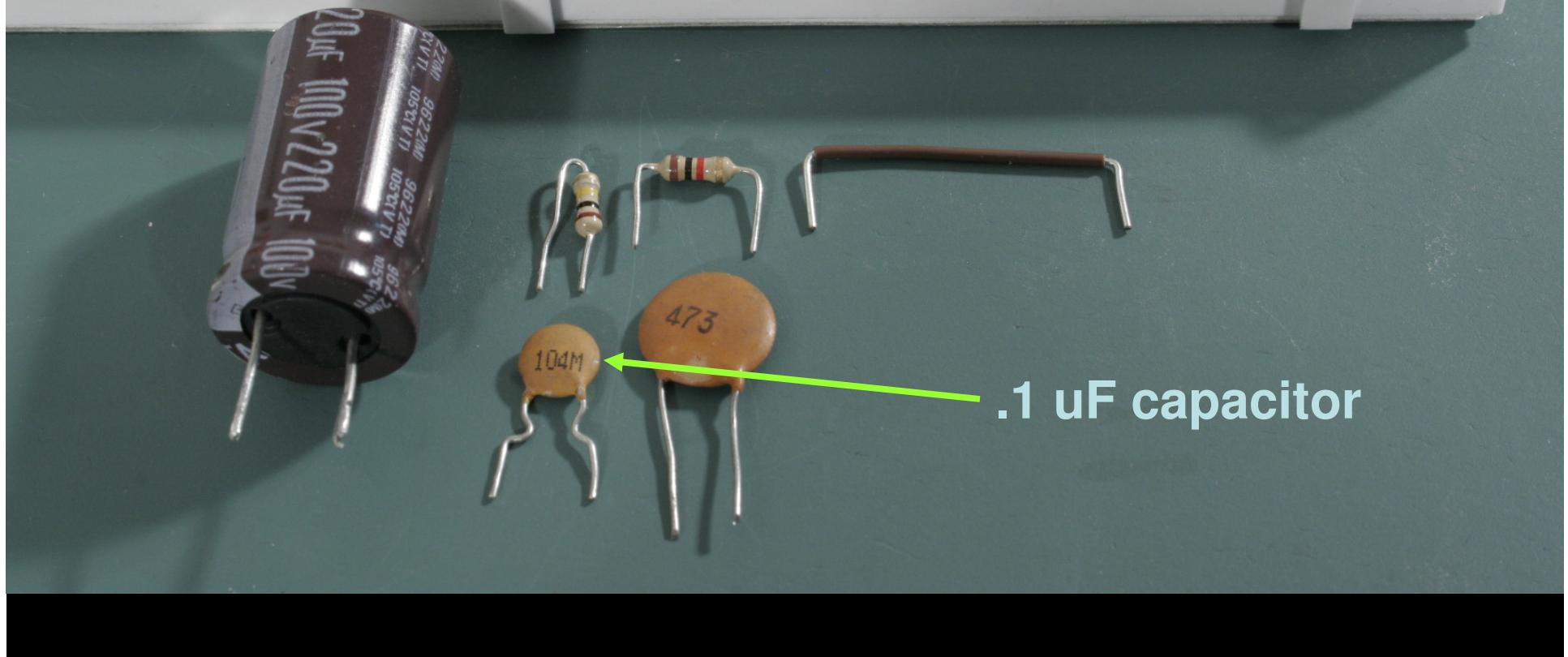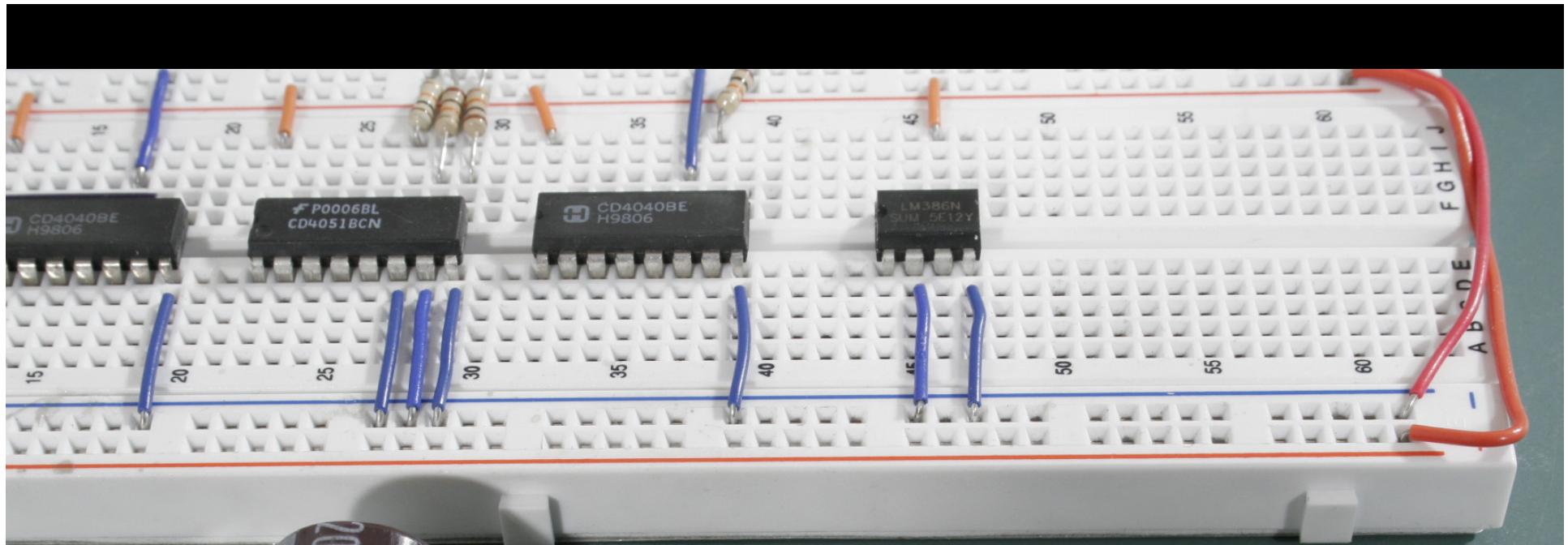

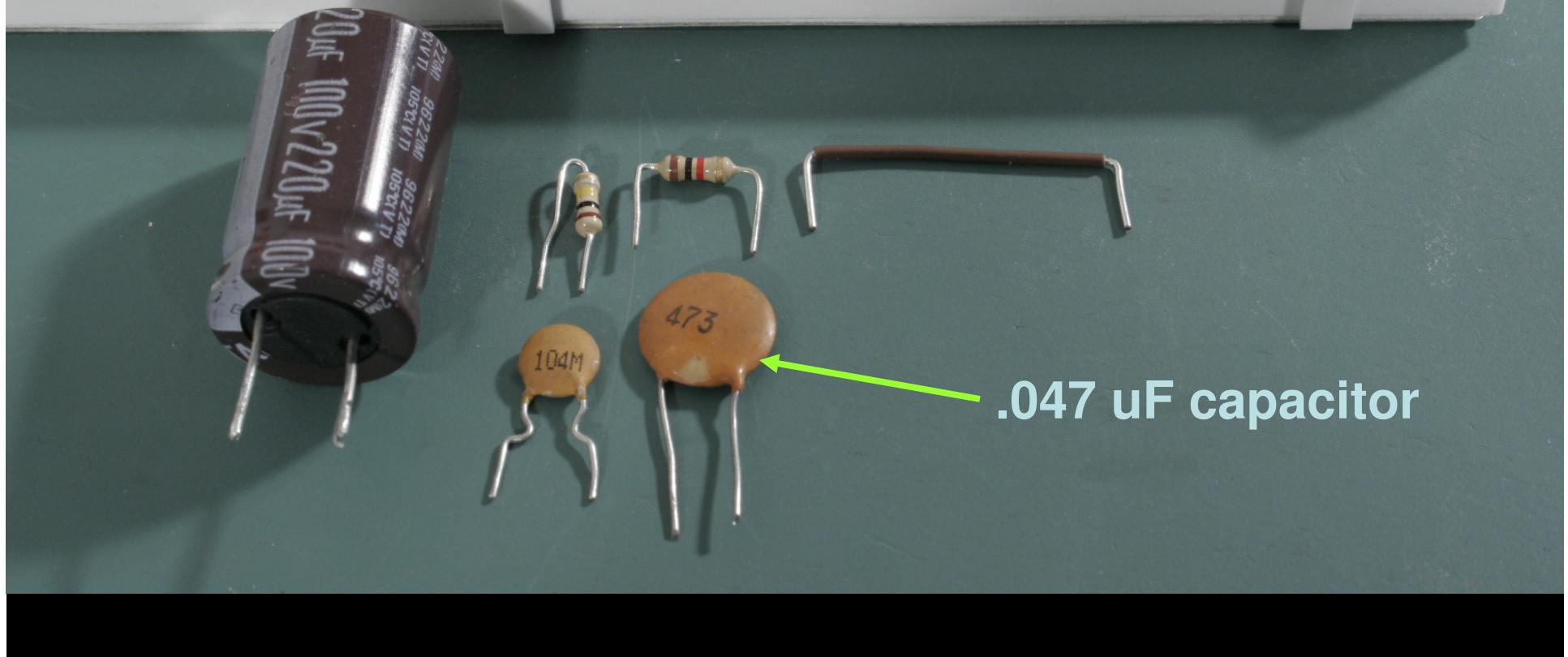
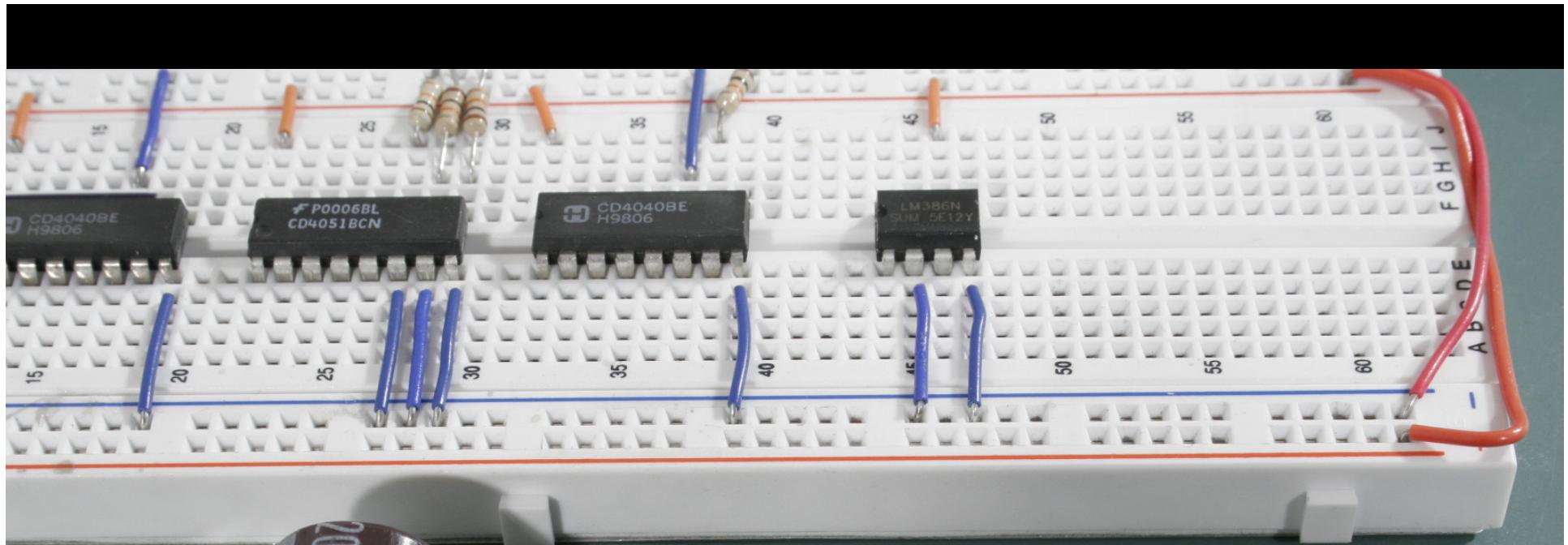


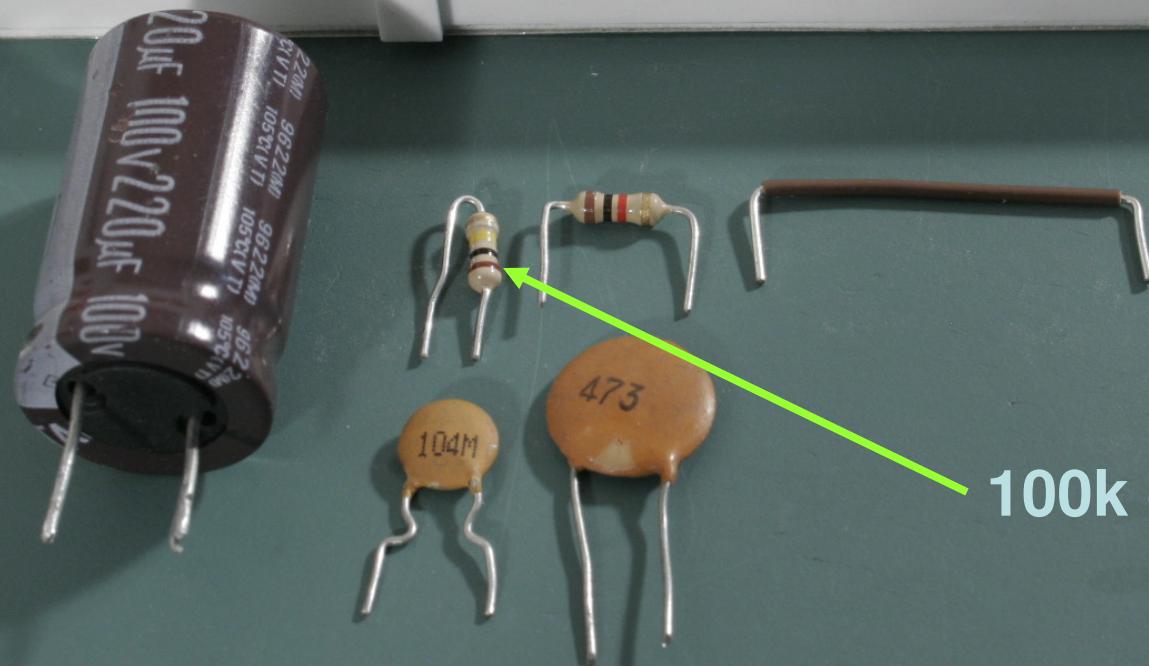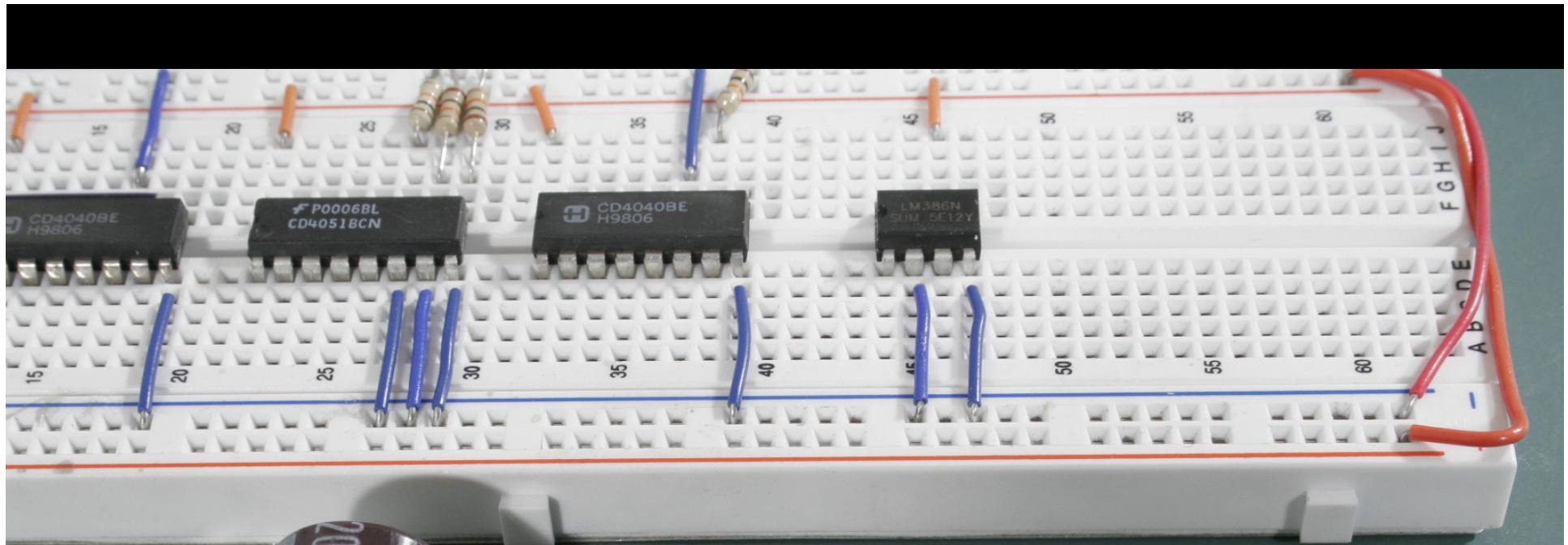


100k ohm resistor

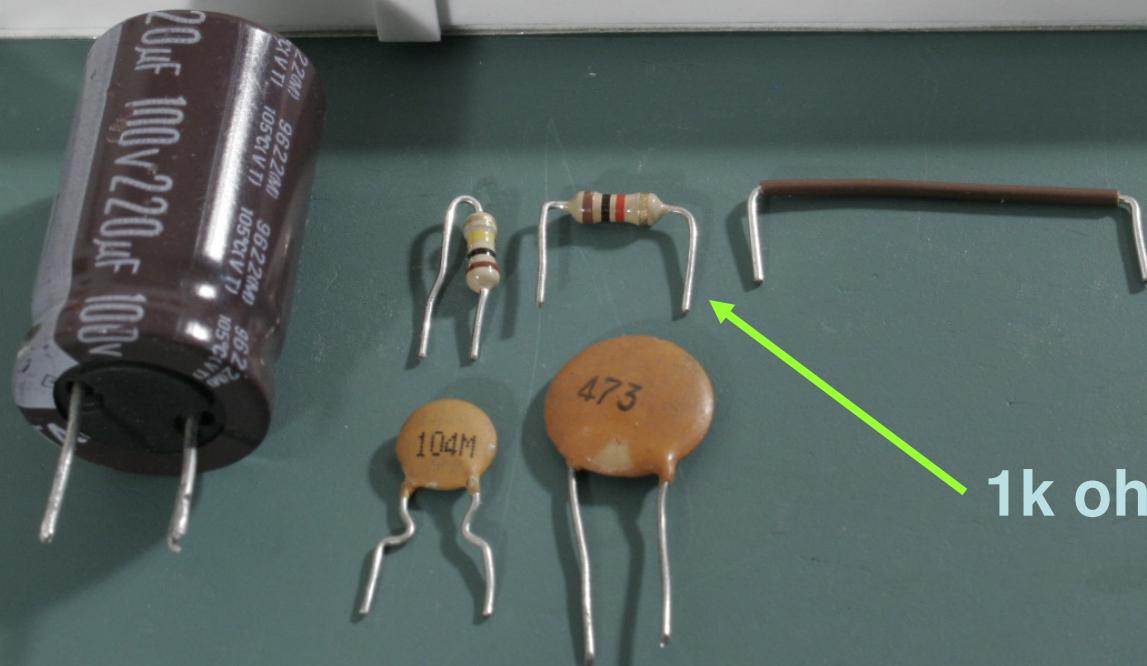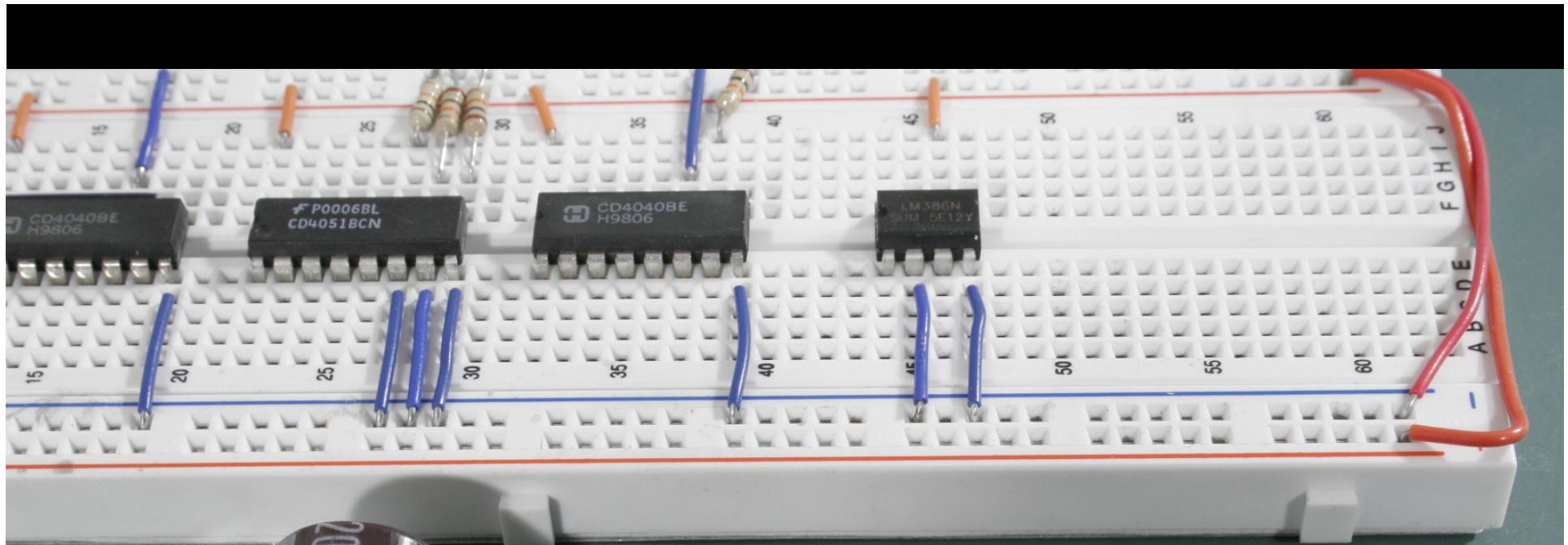


1k ohm resistor

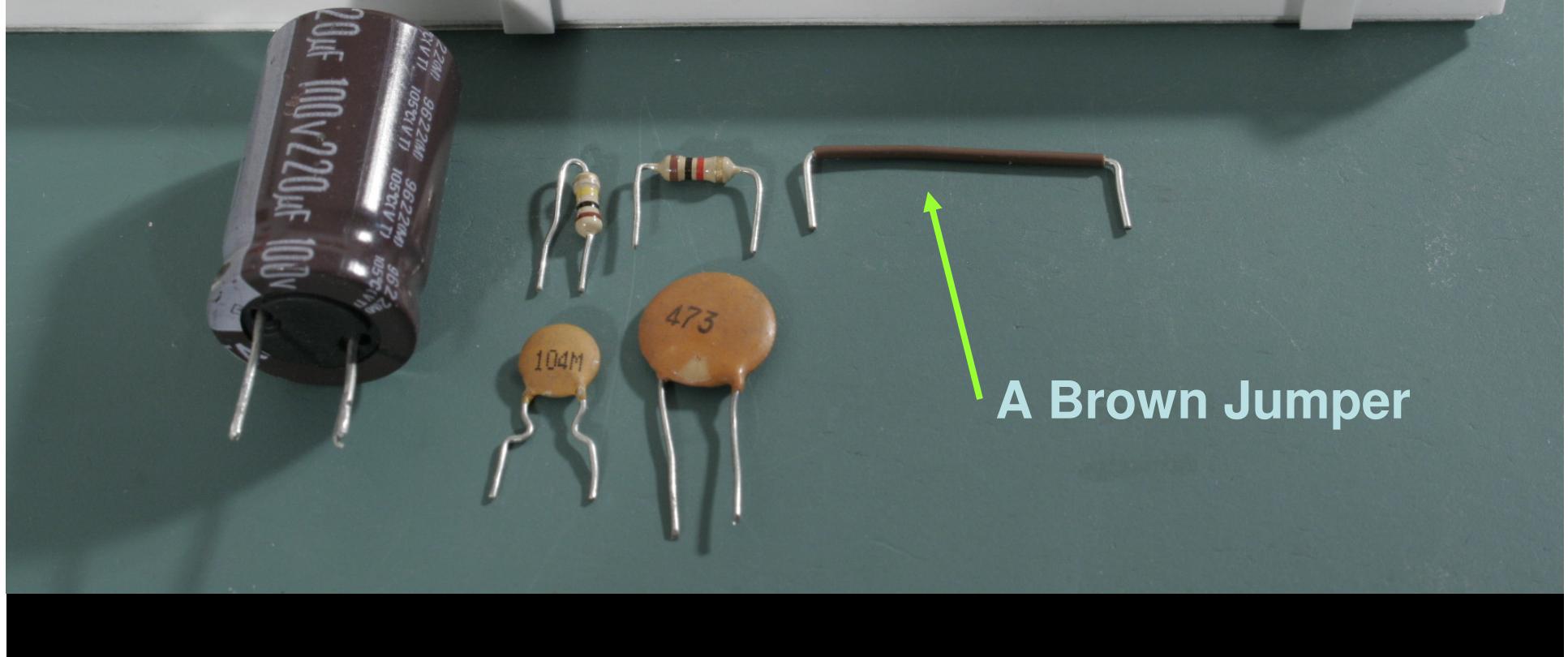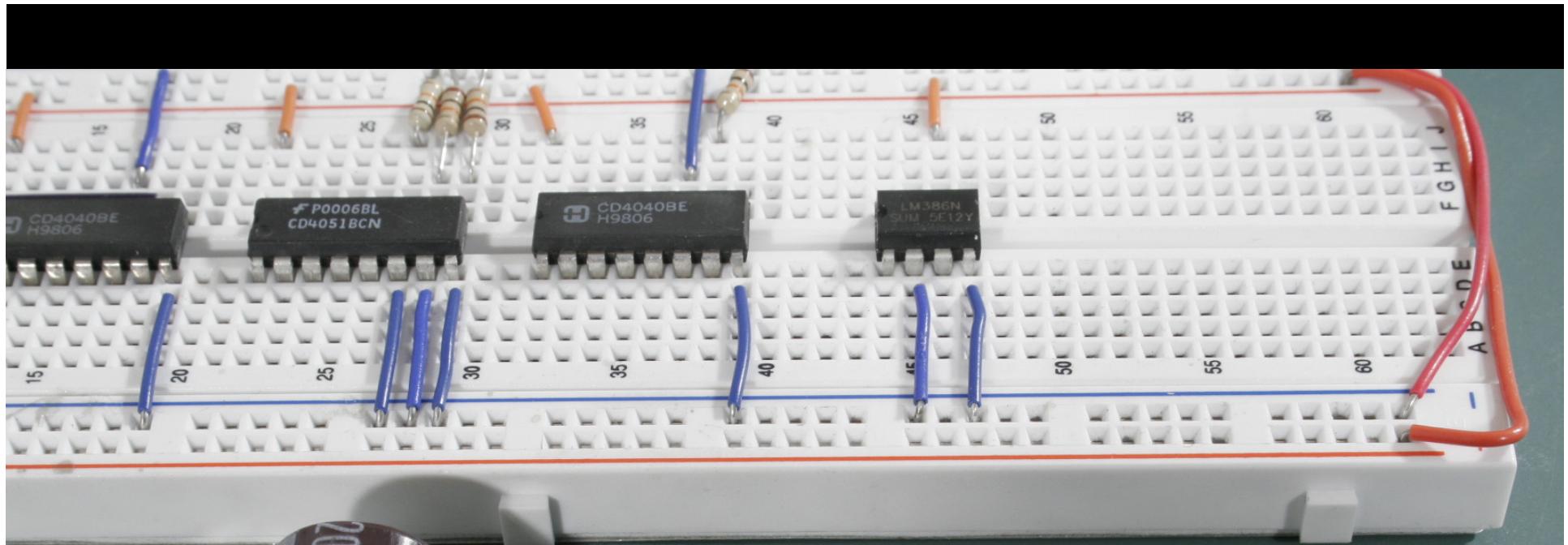

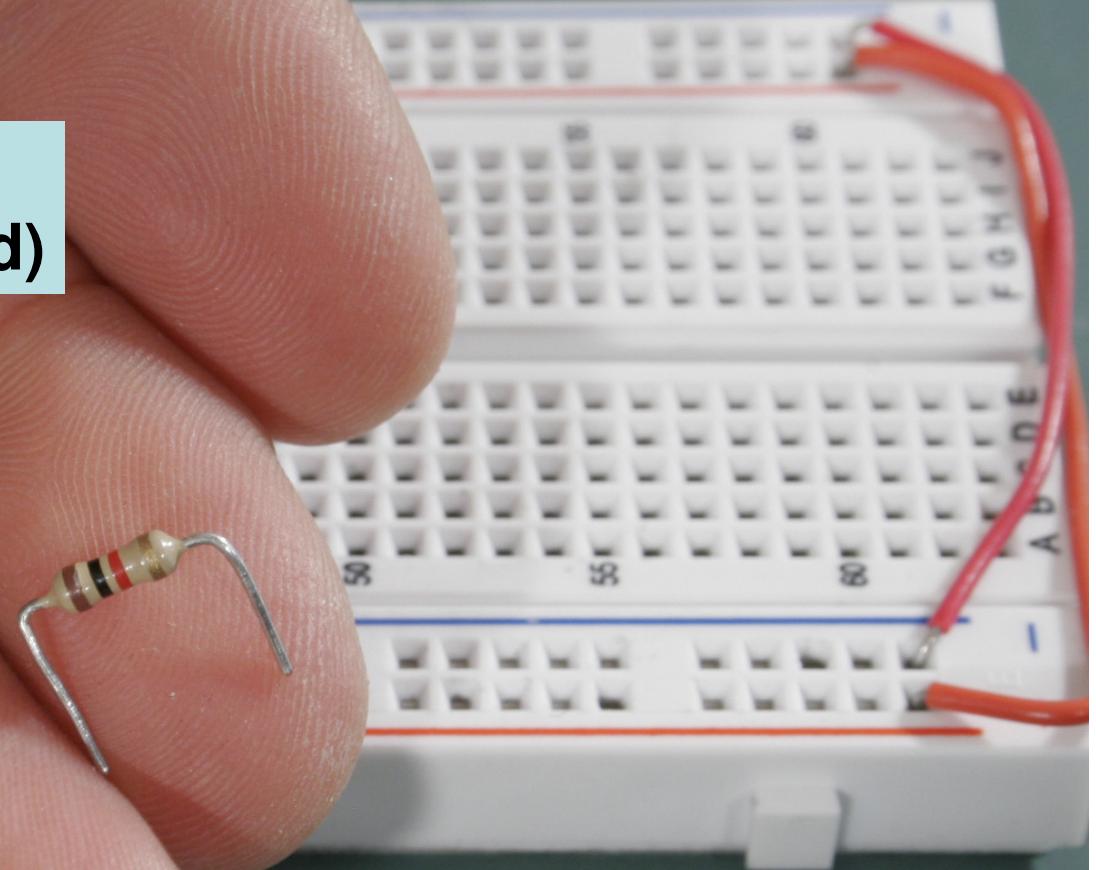
**The 1k Ohm resistor
(Brown Black Red Gold)**



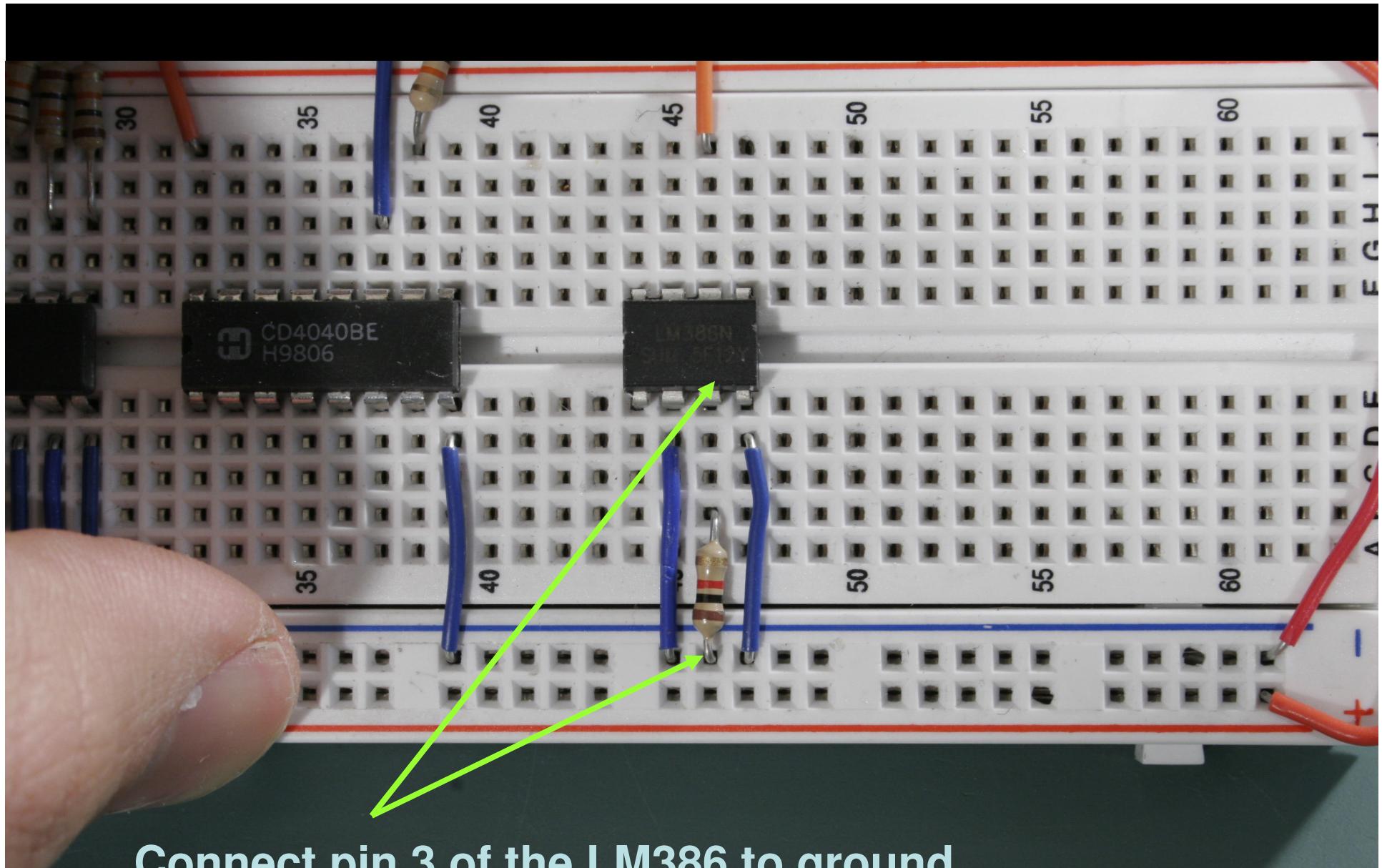


Connect pin 3 of the LM386 to ground through the 1k ohm resistor.


**The .1 uF capacitor
(code: 104)**

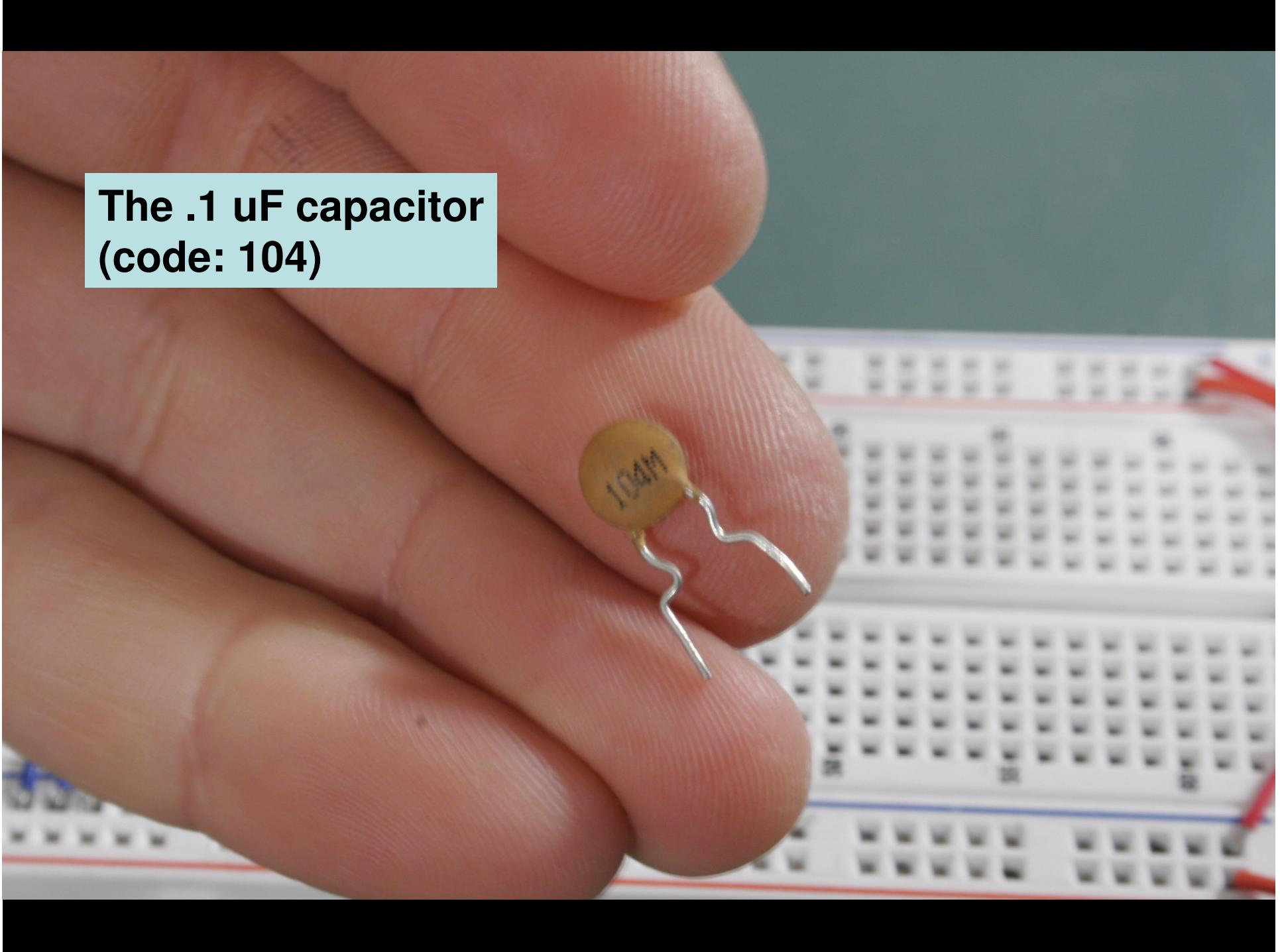

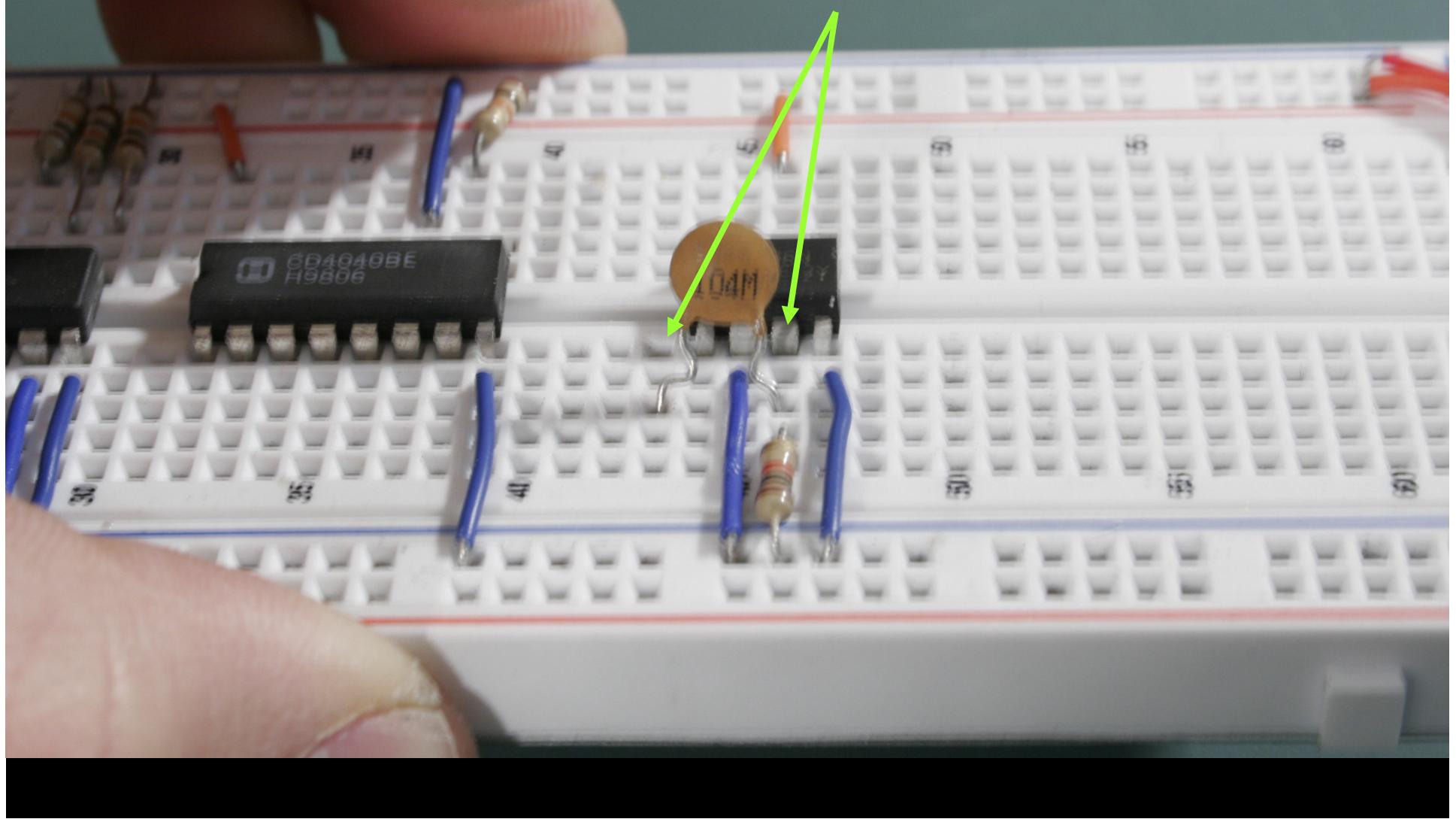
The .1 uF capacitor connects to pin 3 on the LM386 and row 43.



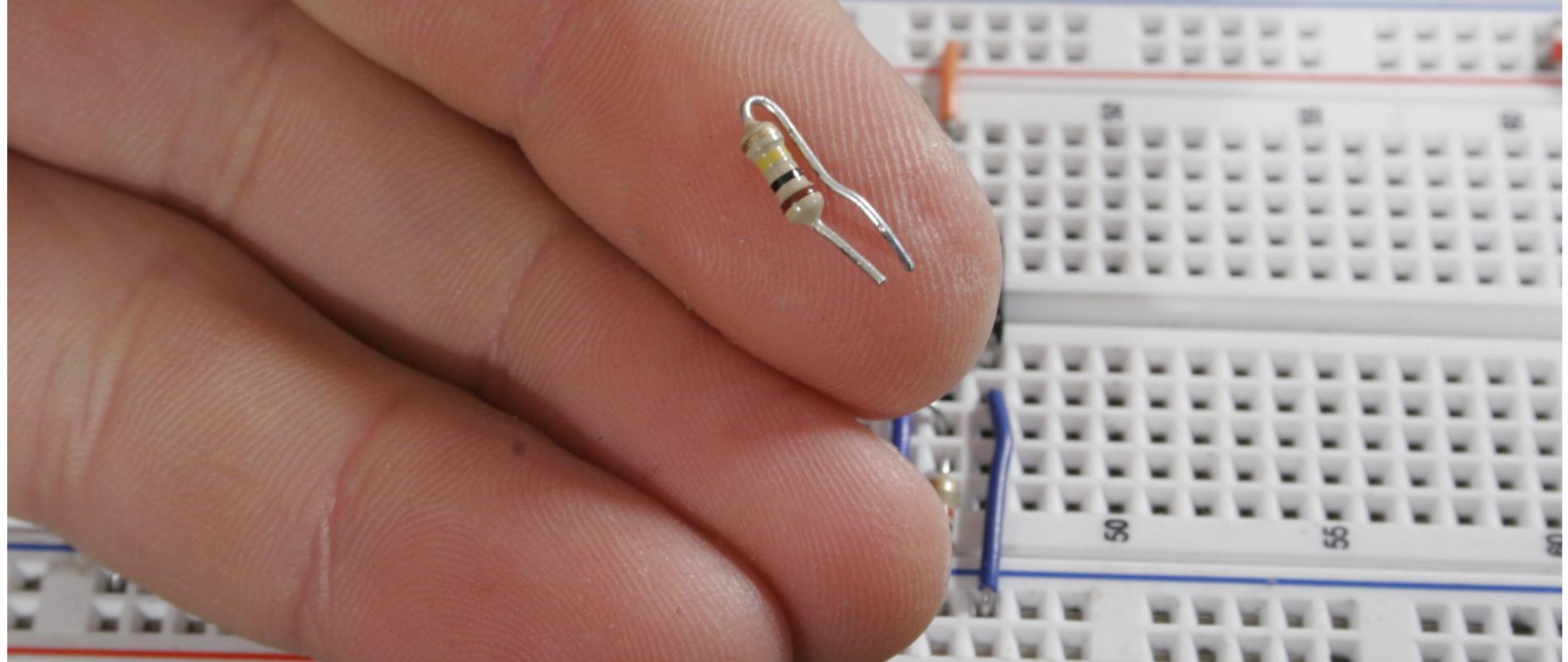
**The 100k Ohm resistor
(Brown Black Yellow Gold)**



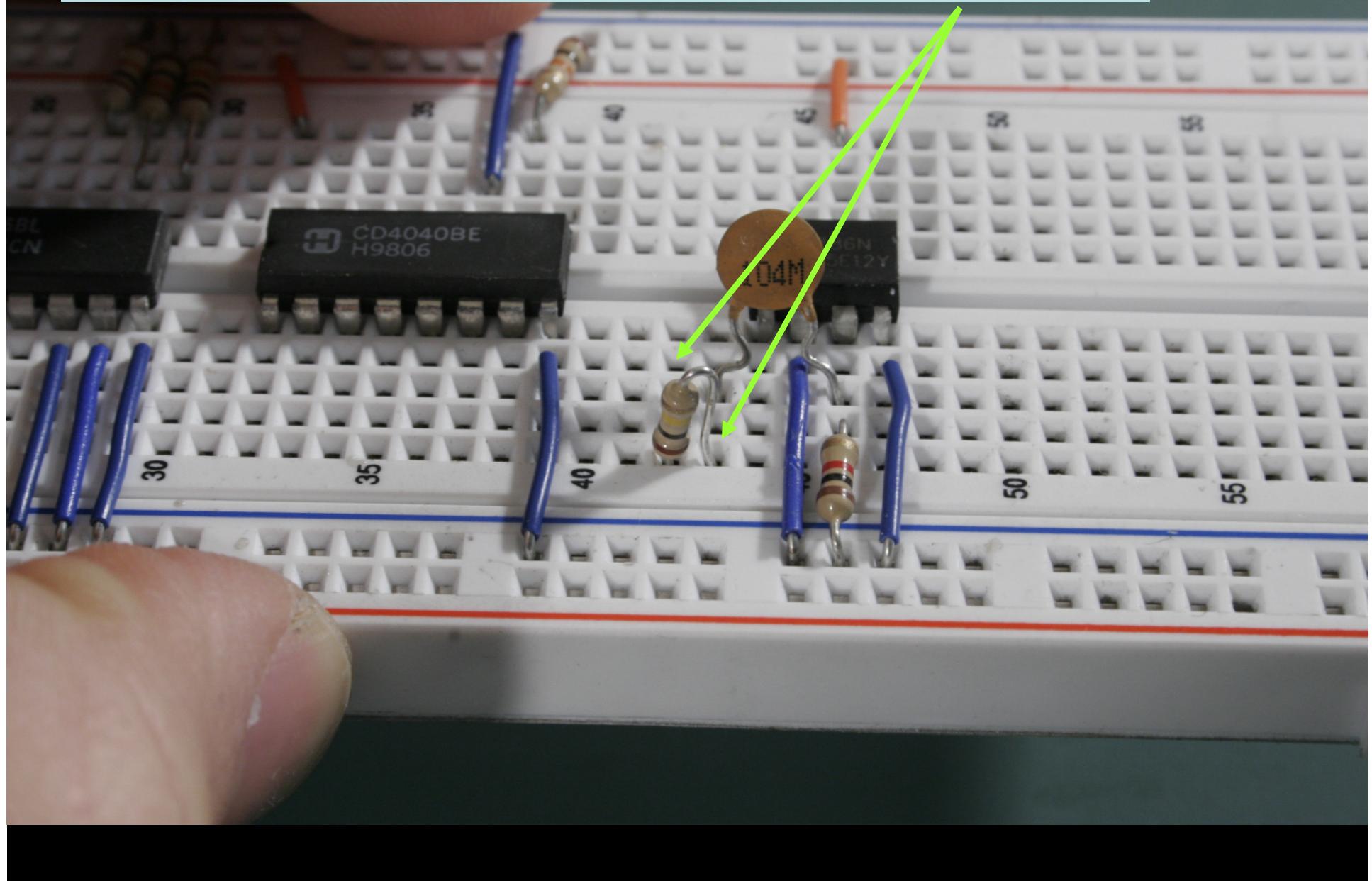
The 100k ohm resistor connects to row 43 and 42



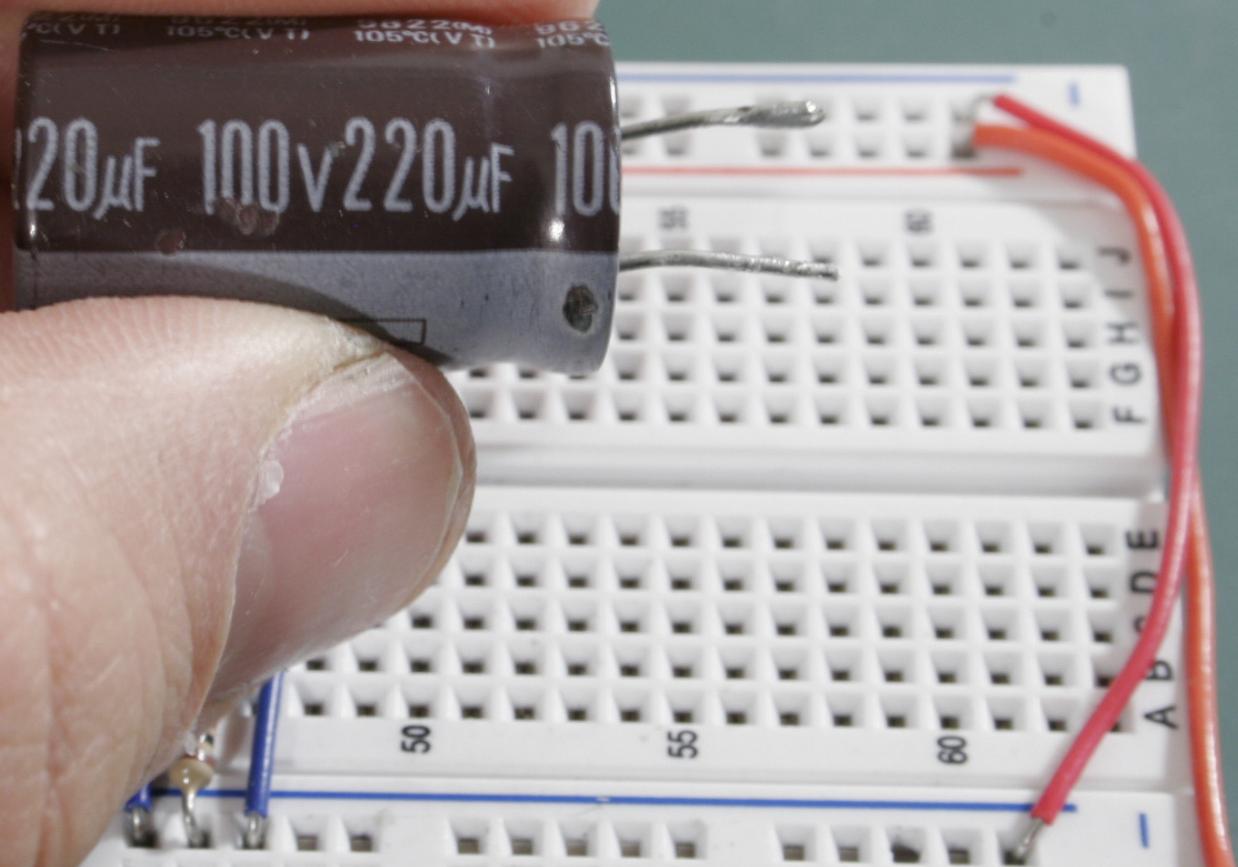**The 220 uF capacitor
(observe polarity!)**




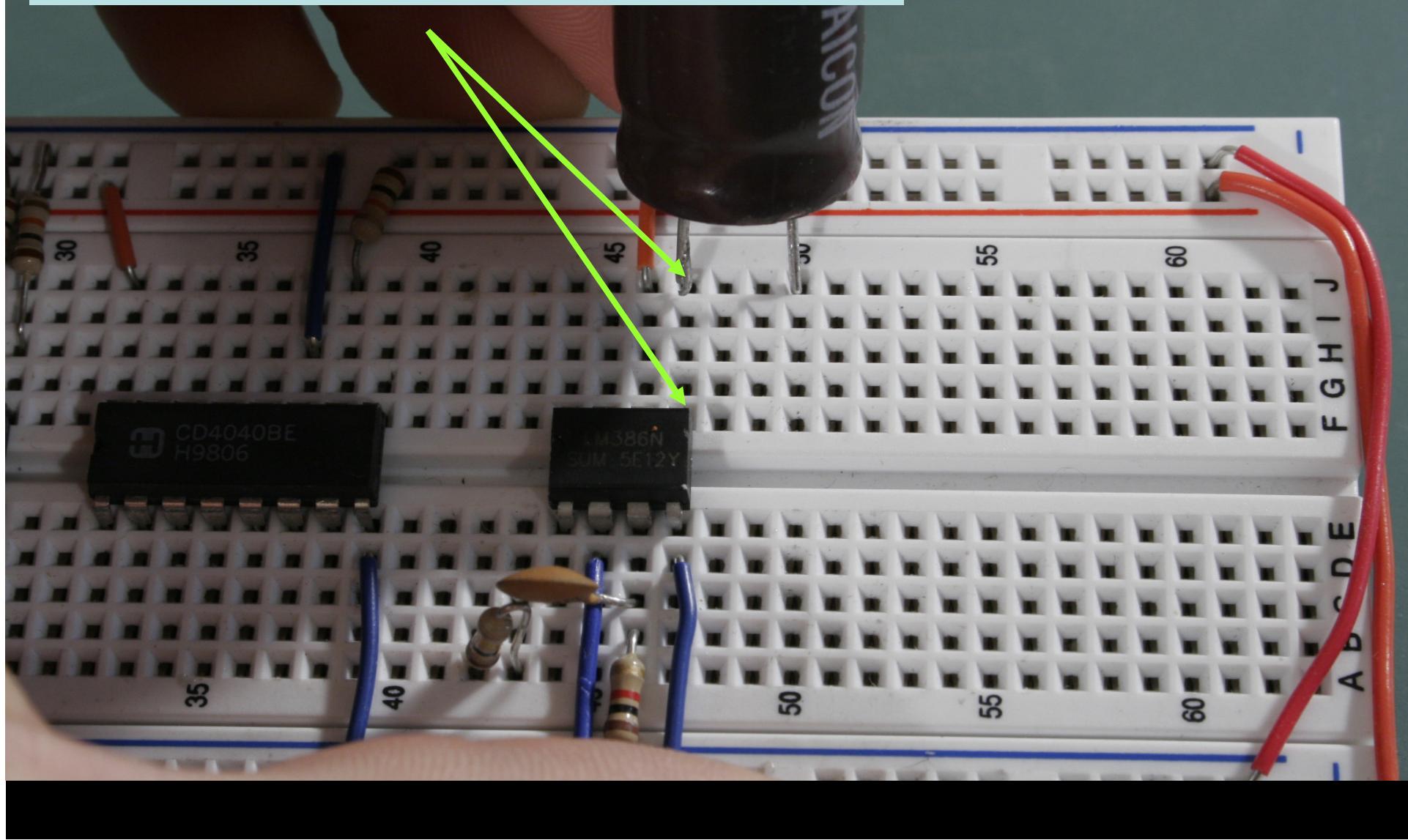Connect positive side of the capacitor to pin 5 on the LM 386.




Connect positive side of the capacitor
to pin 5 on the LM 386.


negative side
to row 50

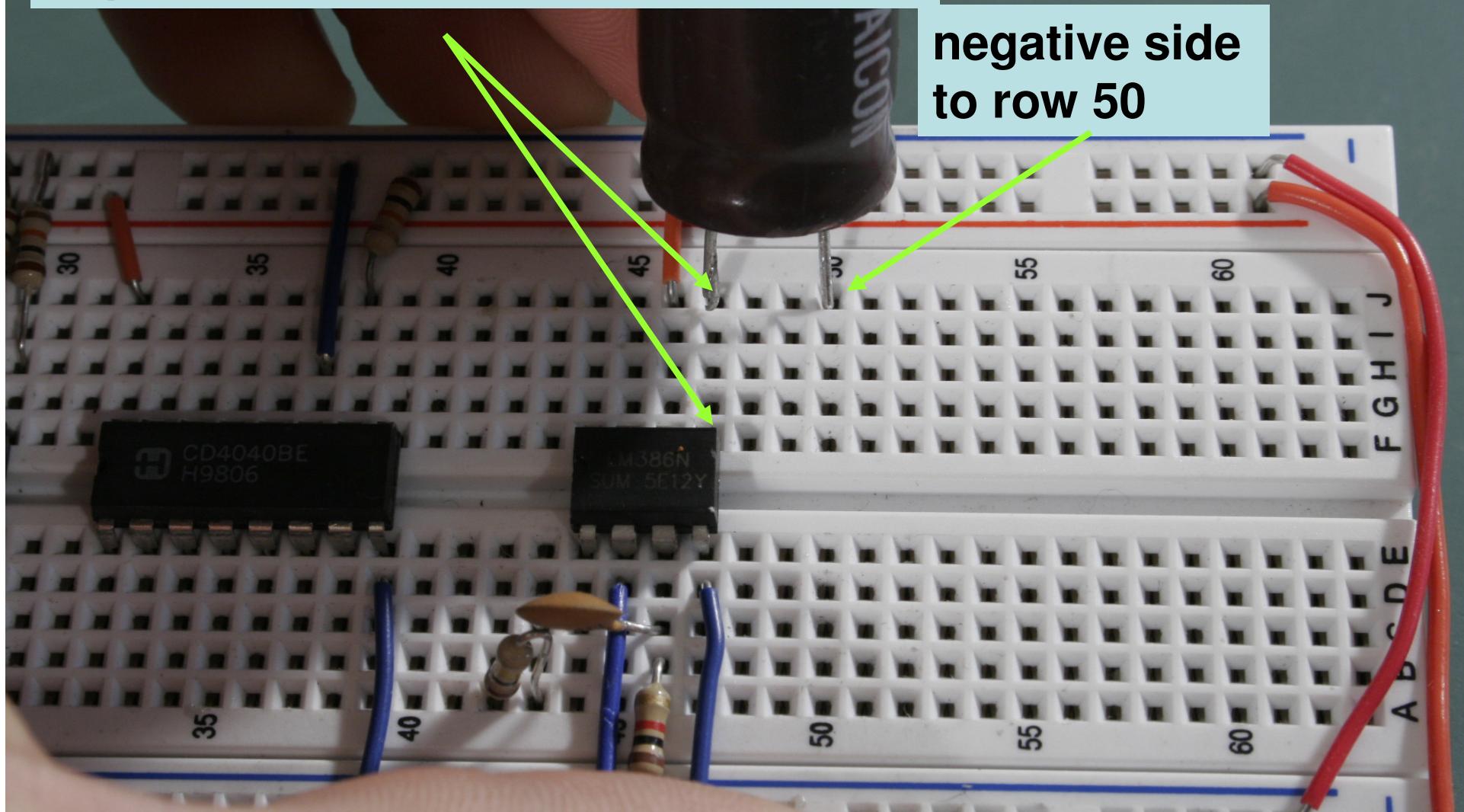


**The .047uF capacitor
(code: 473)**

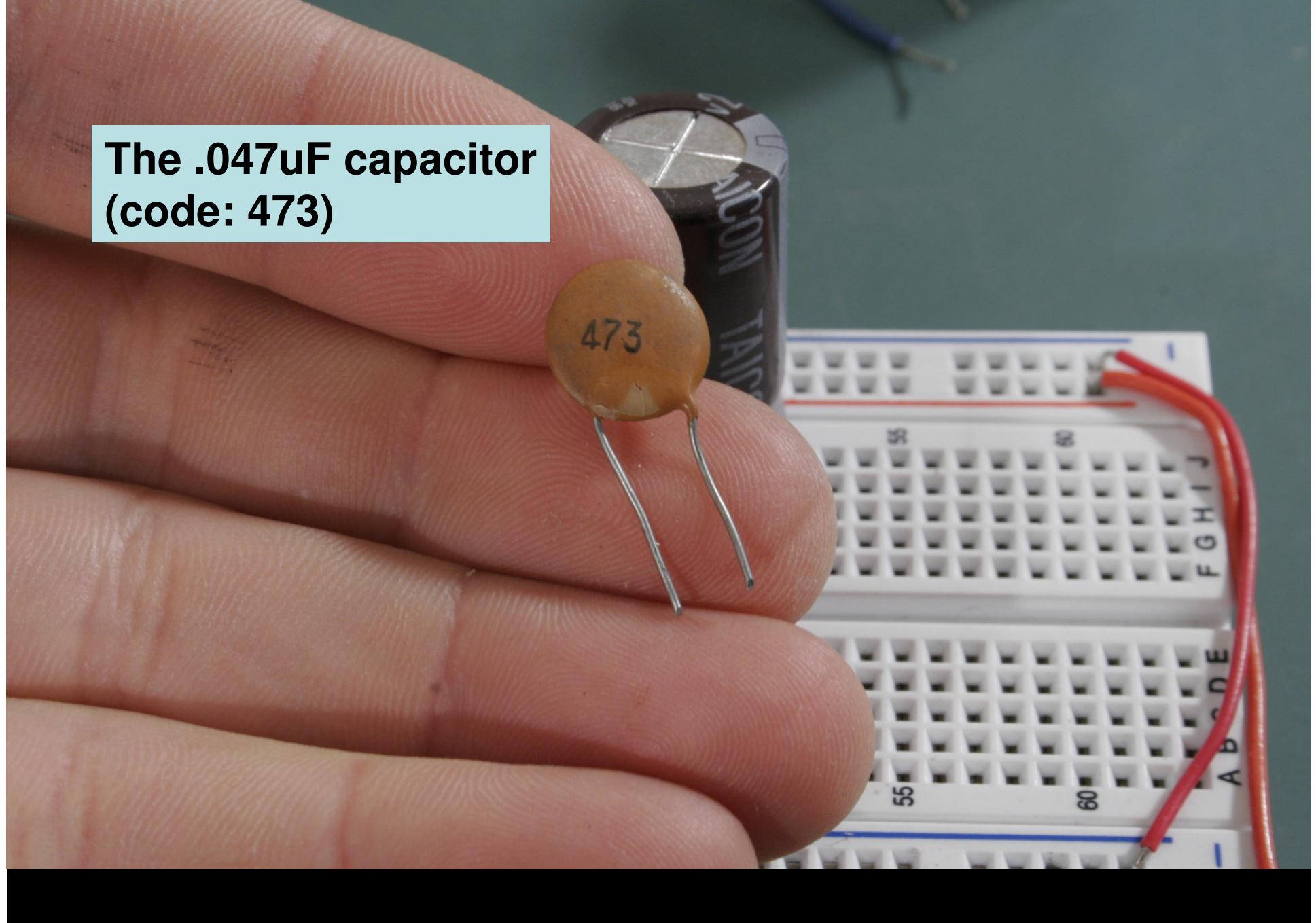


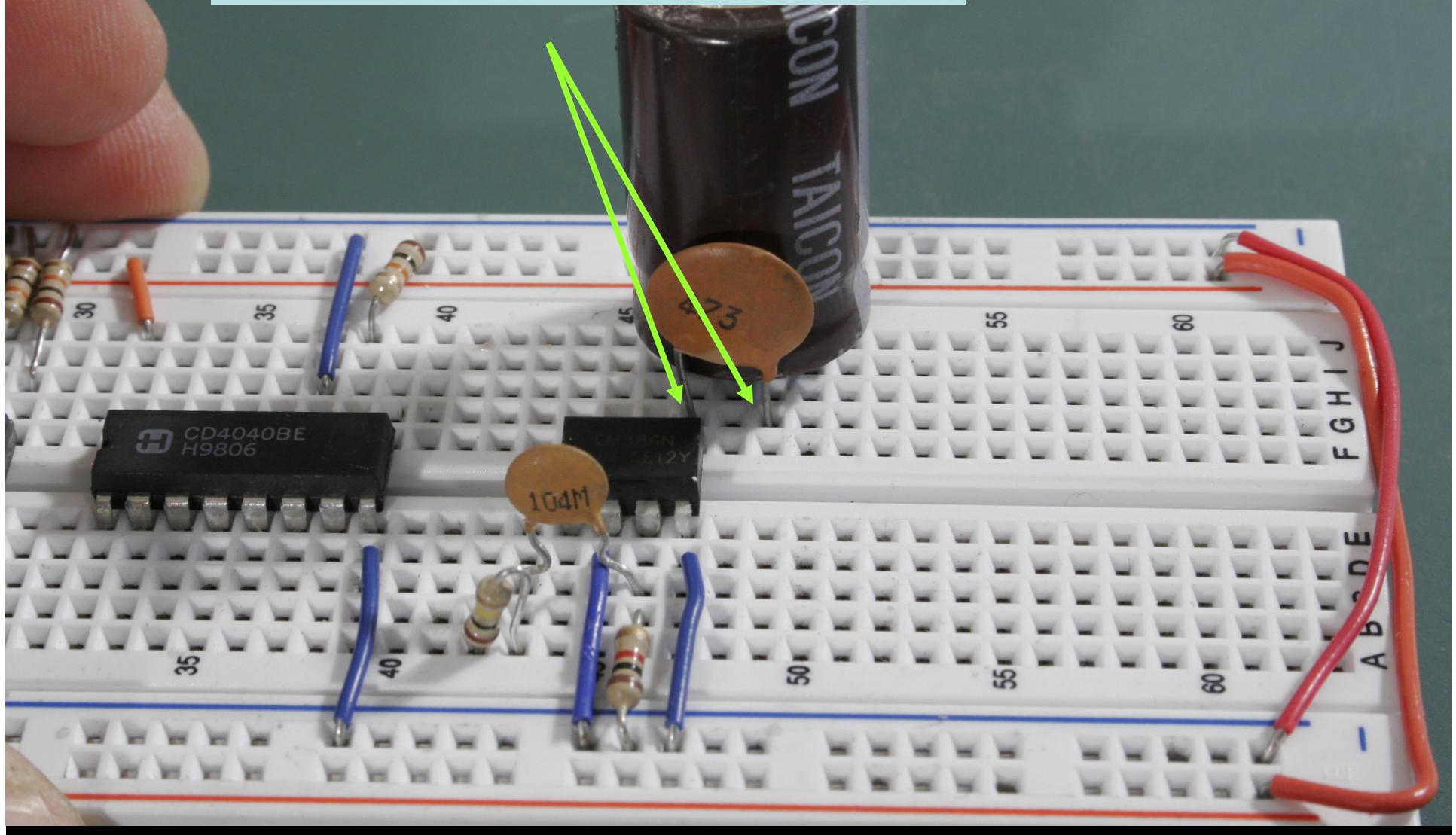
Connects to pin 5 on the LM386
and to row 49.



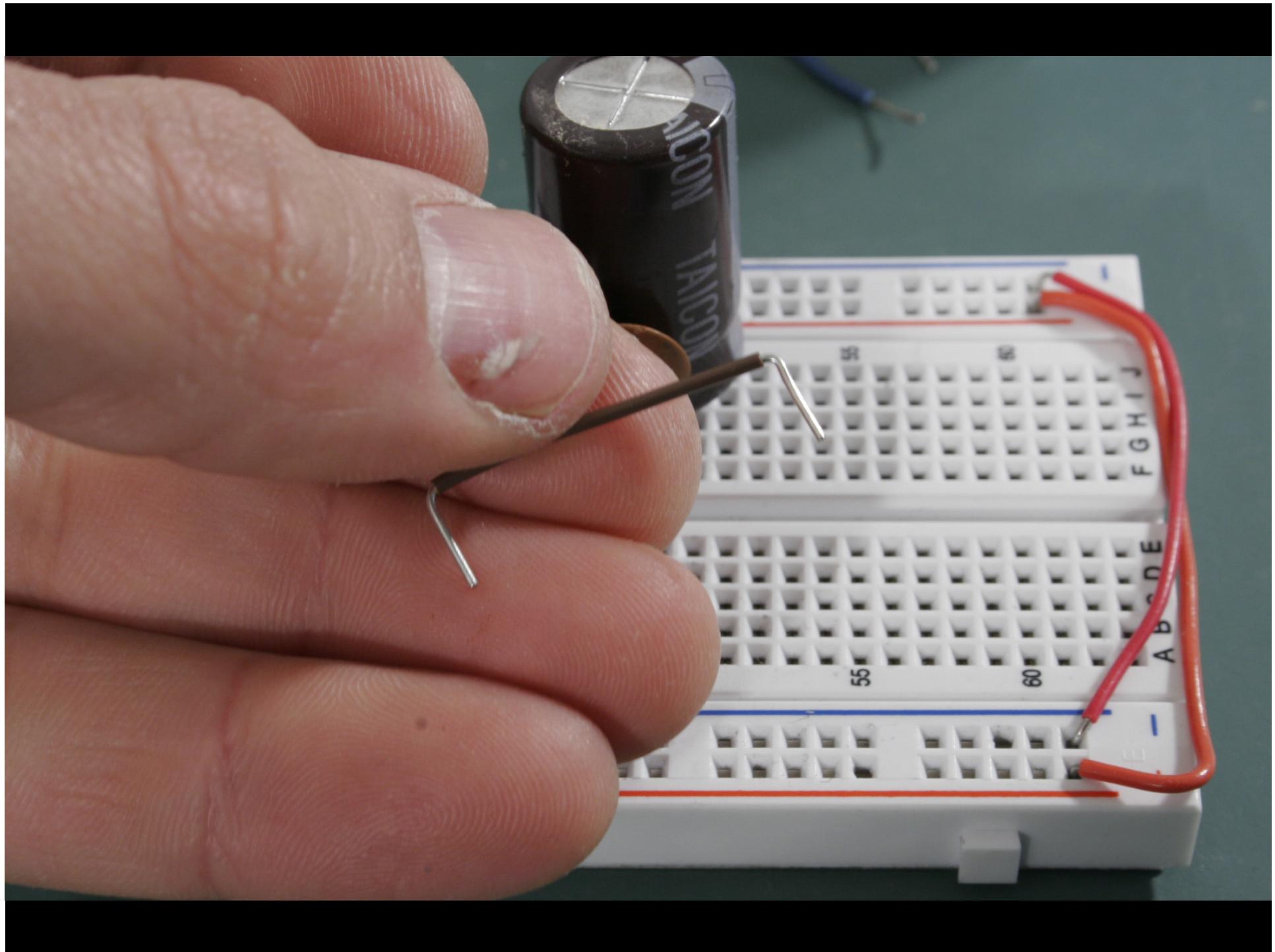


Connects row 49 to ground.

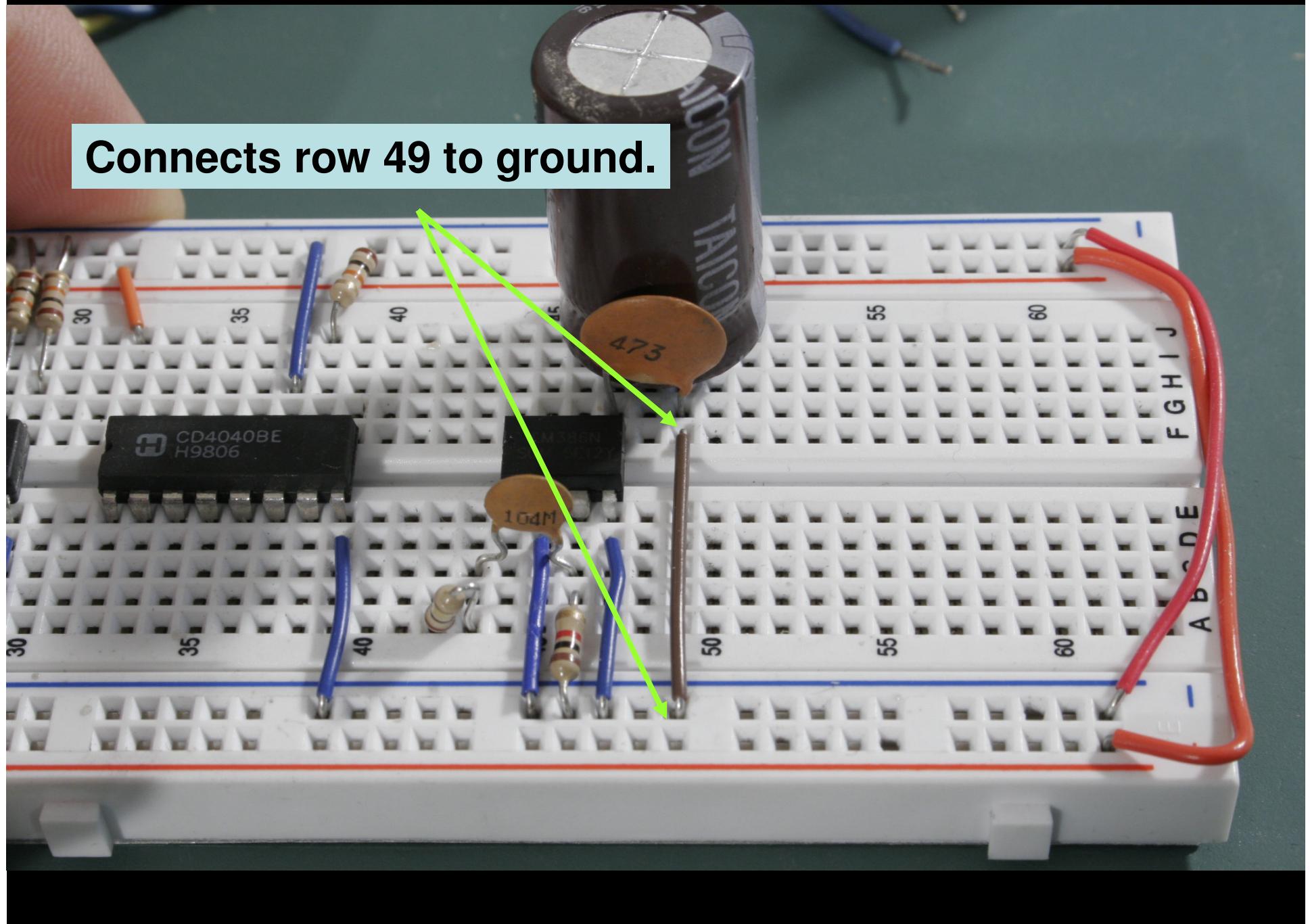


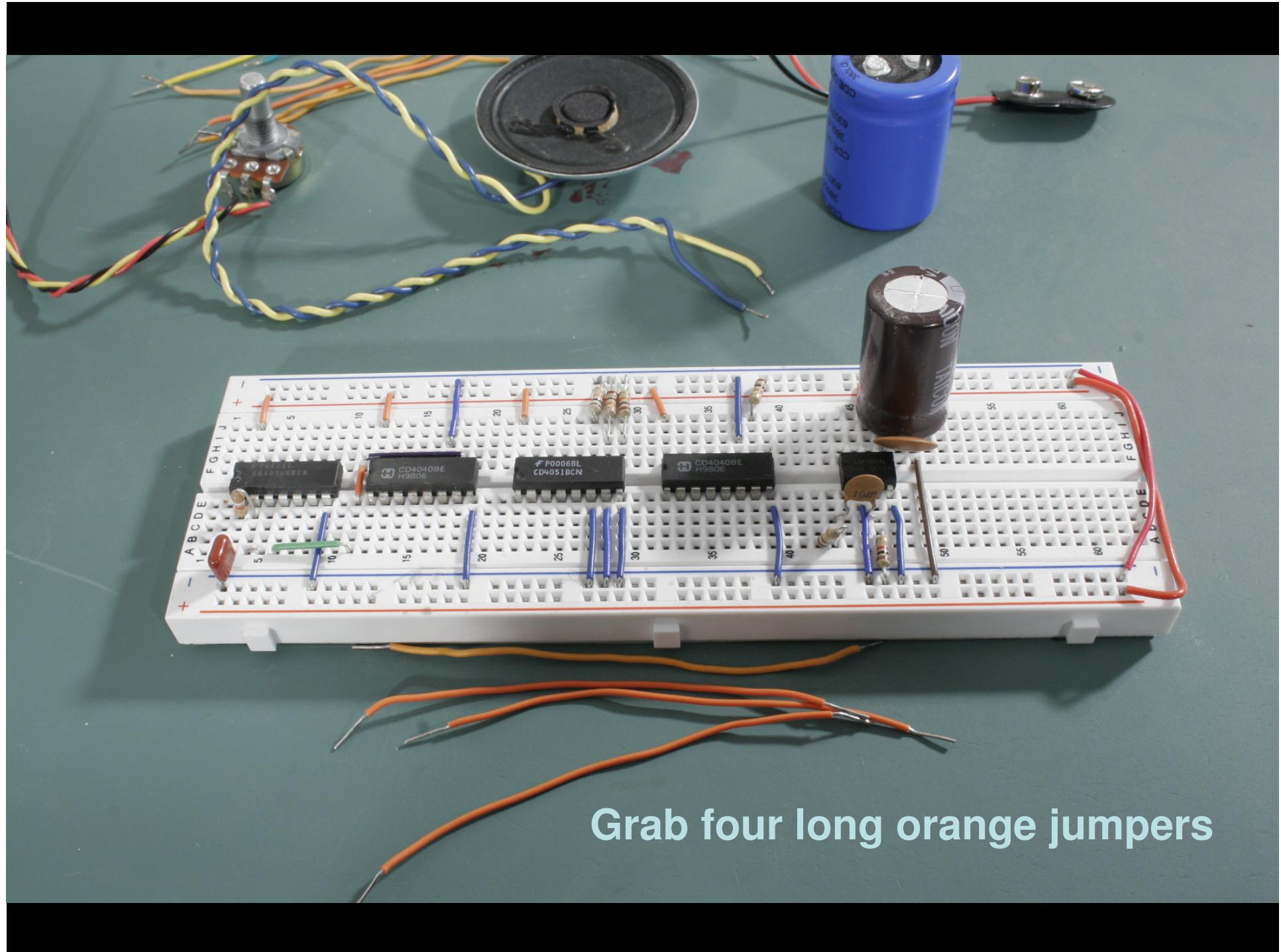


Grab four long orange jumpers

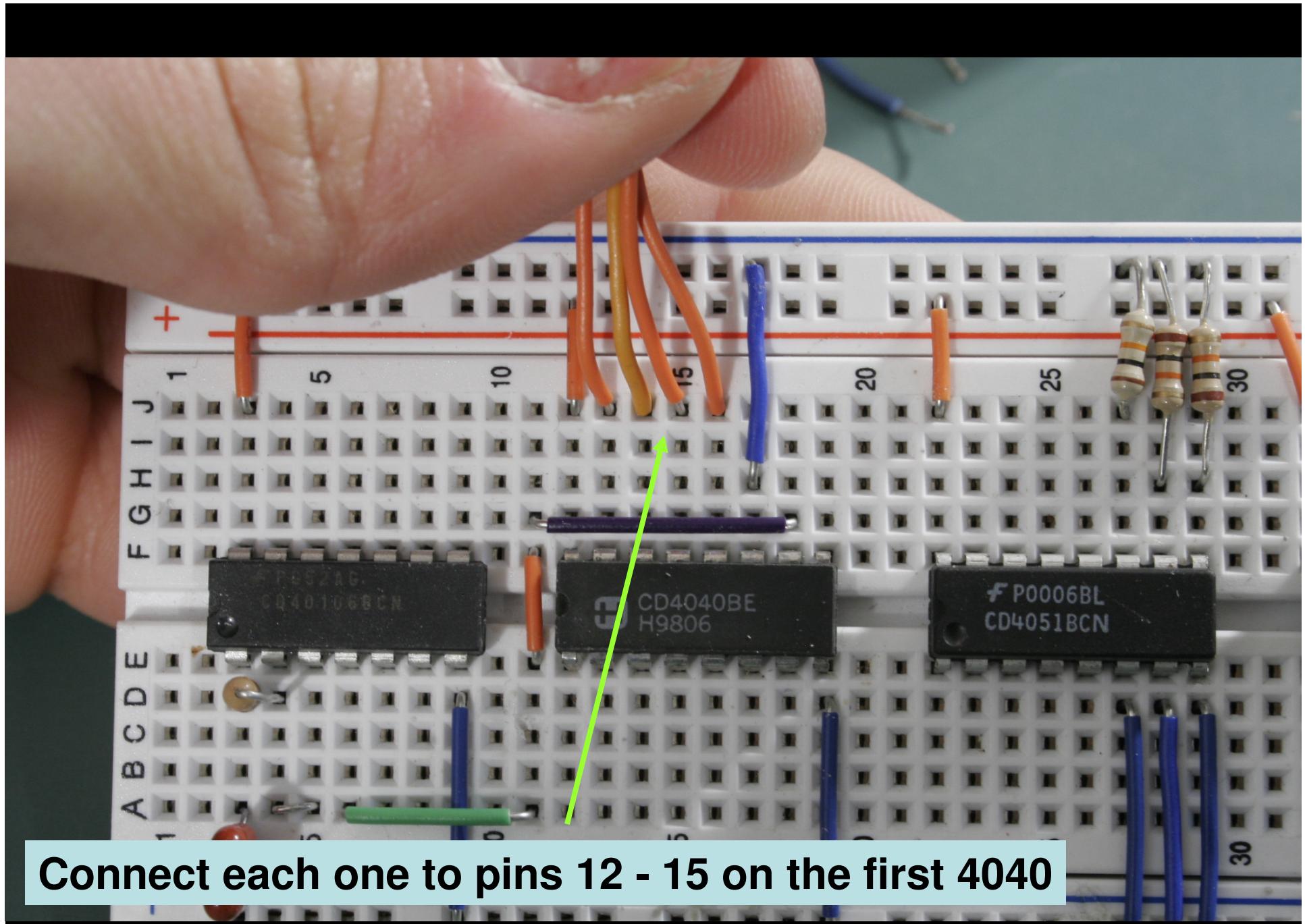

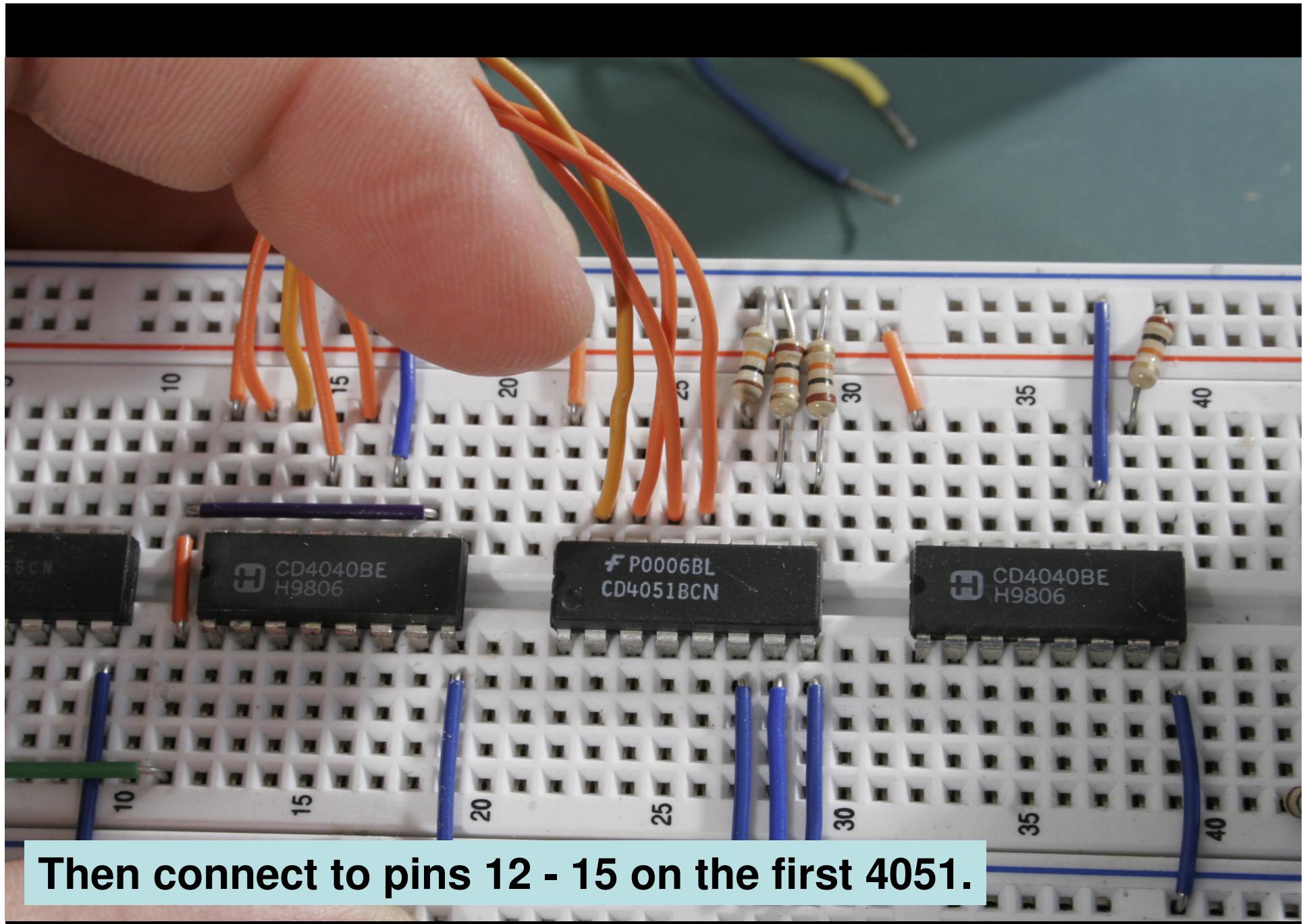
Connect each one to pins 12 - 15 on the first 4040



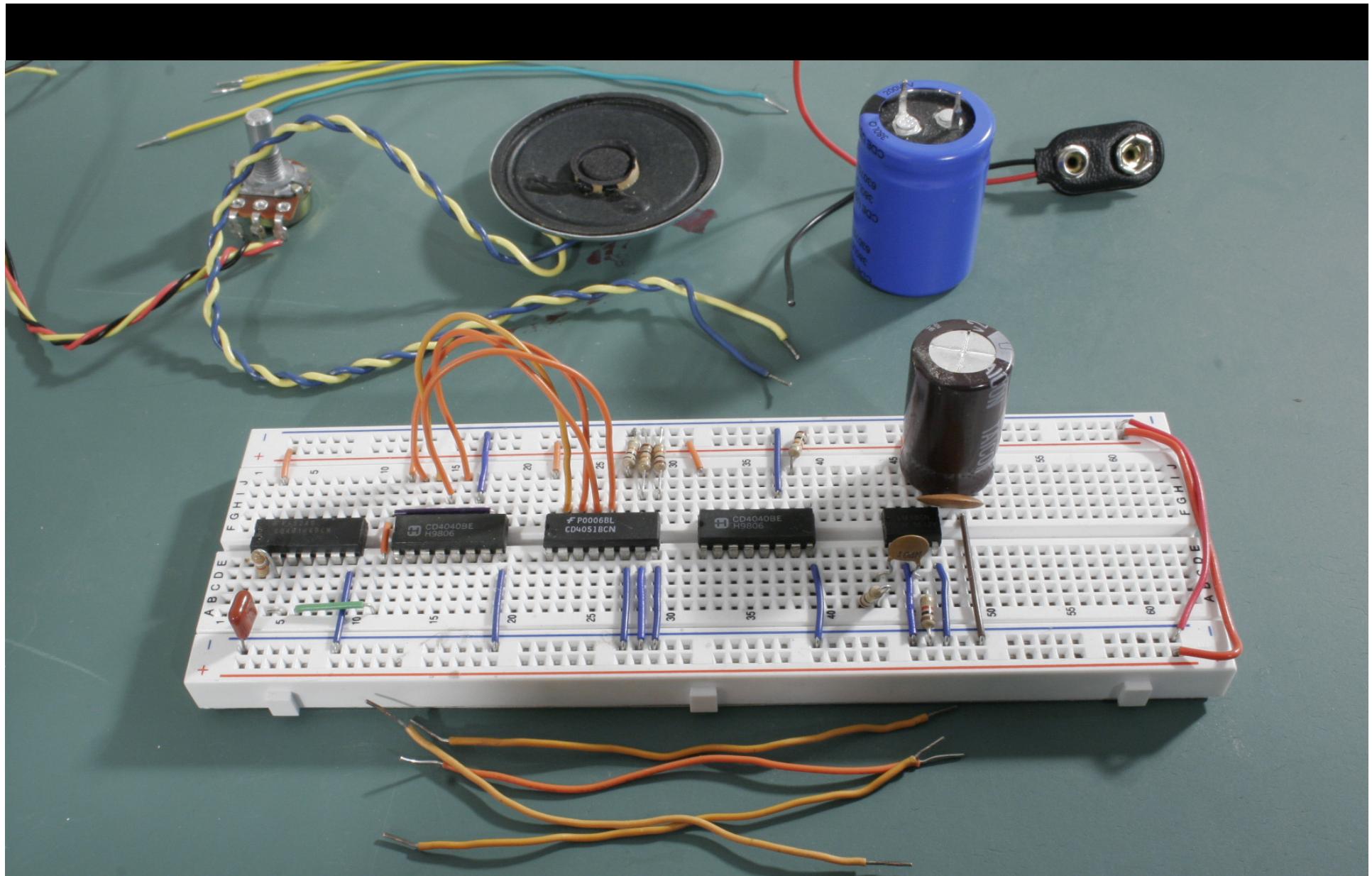
Then connect to pins 12 - 15 on the first 4051.




Grab four more long orange jumpers

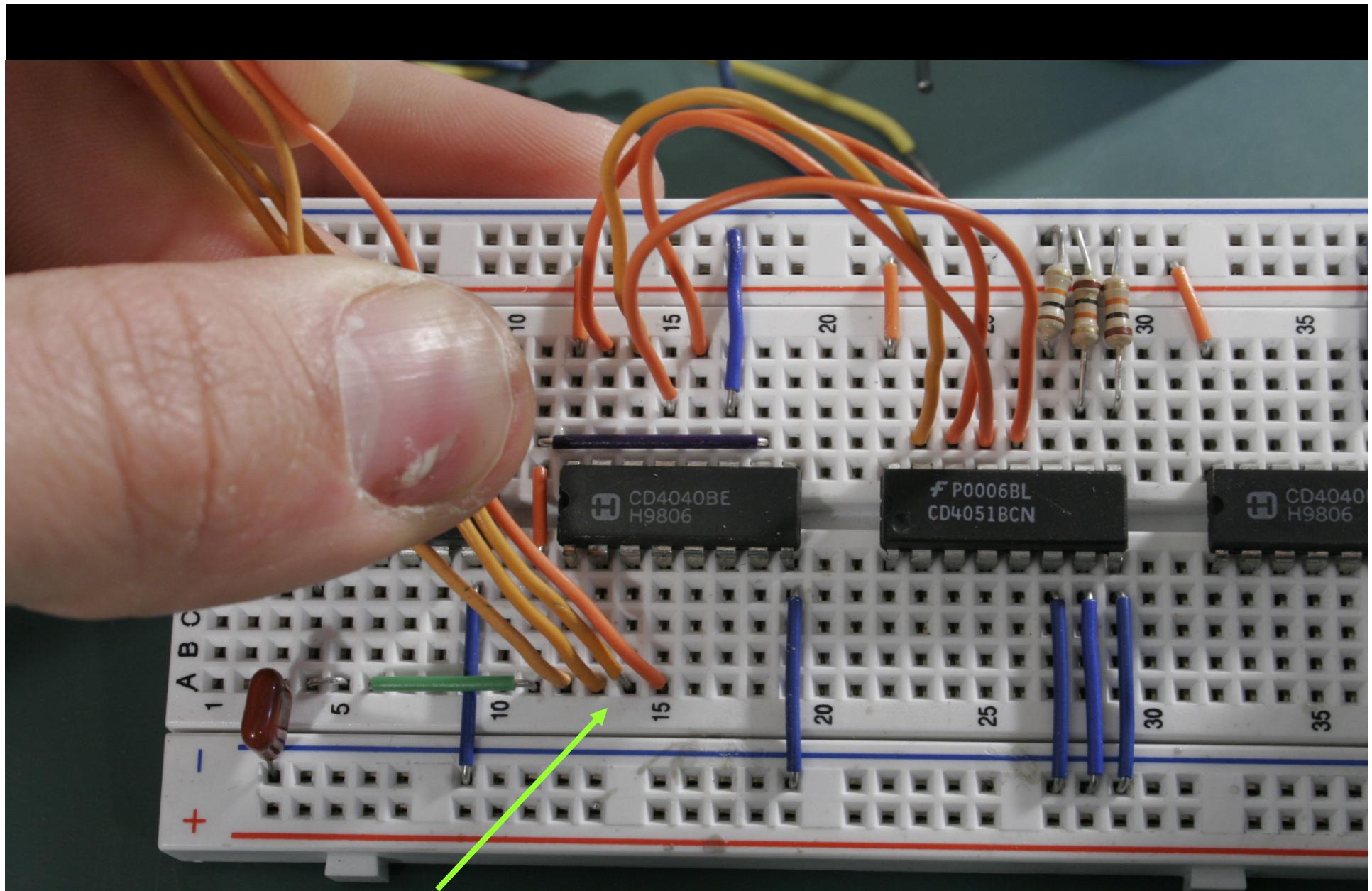

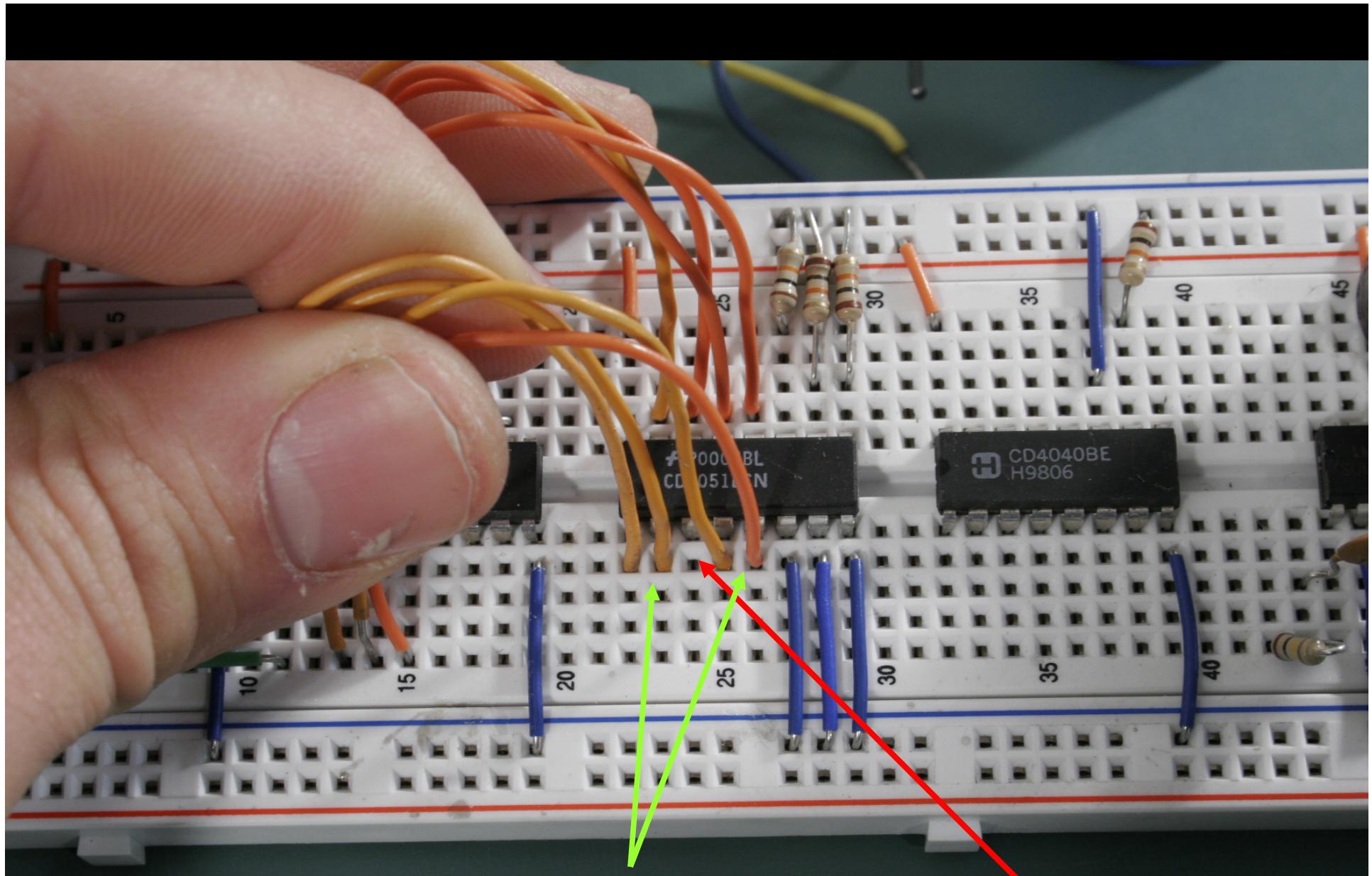
Connect each one to pins 1- 4 on the first 4040



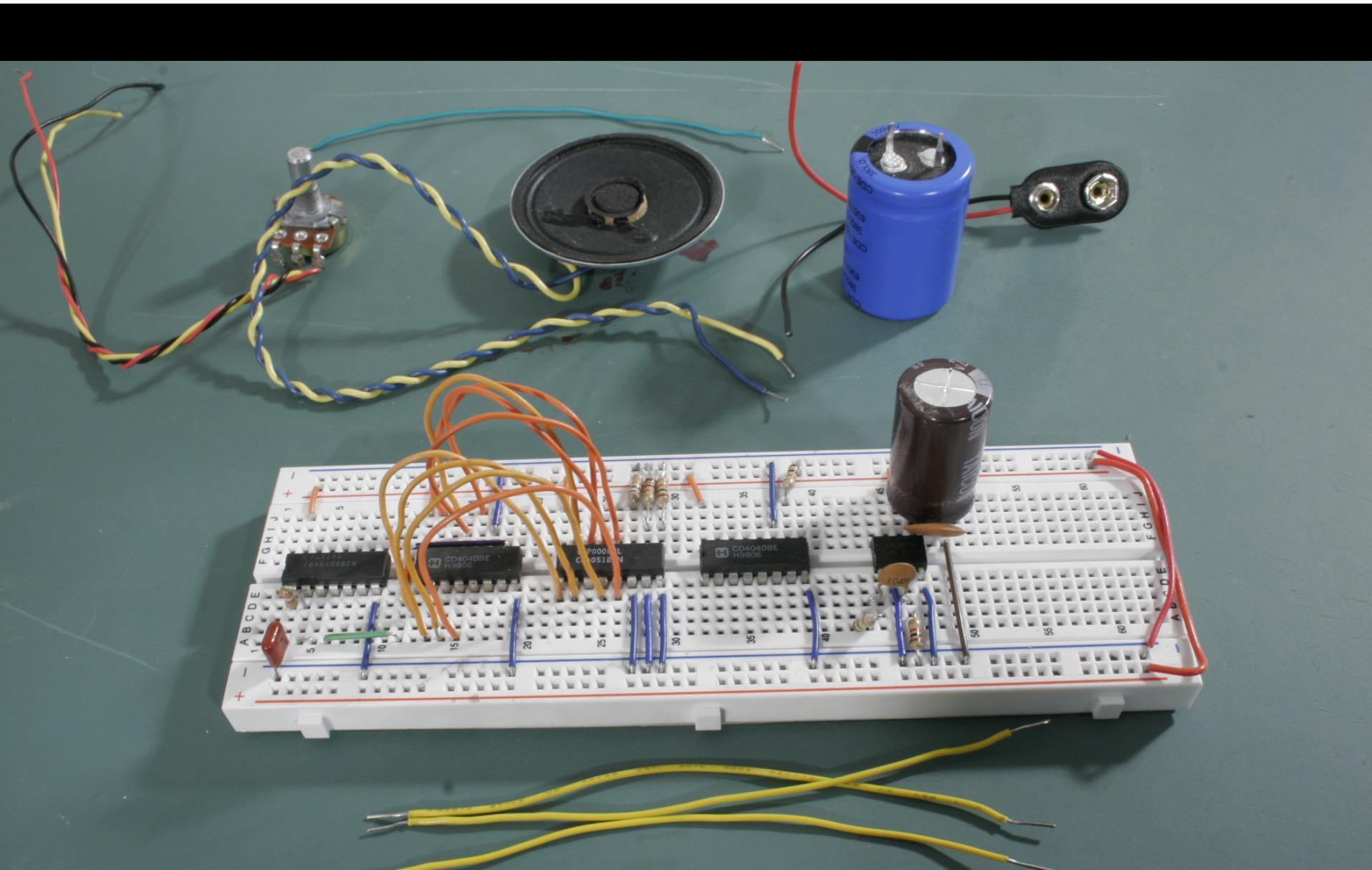
Connect each to pins 1,2, 4, and 5. SKIP PIN 3!




Grab three long yellow jumpers

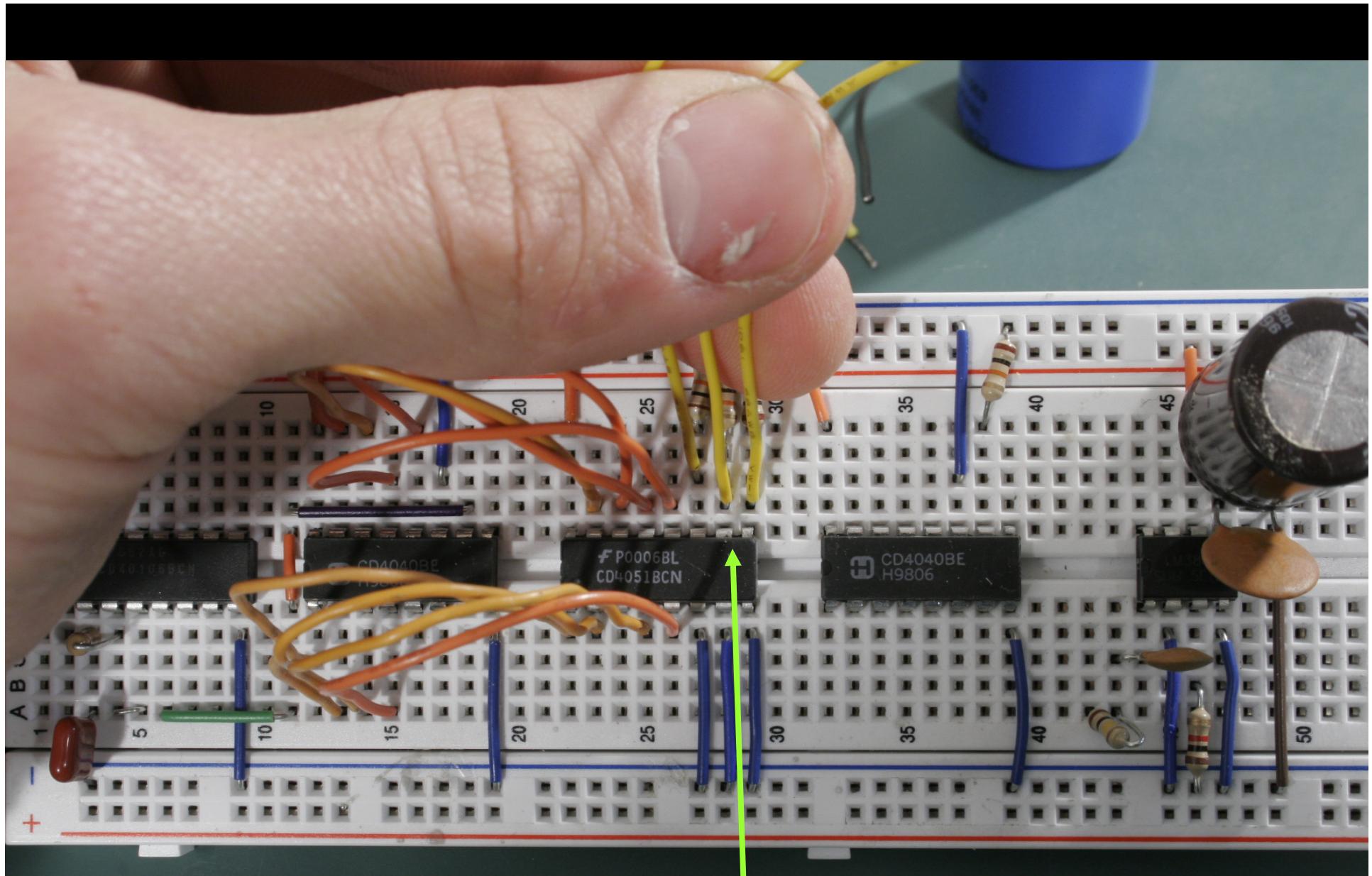

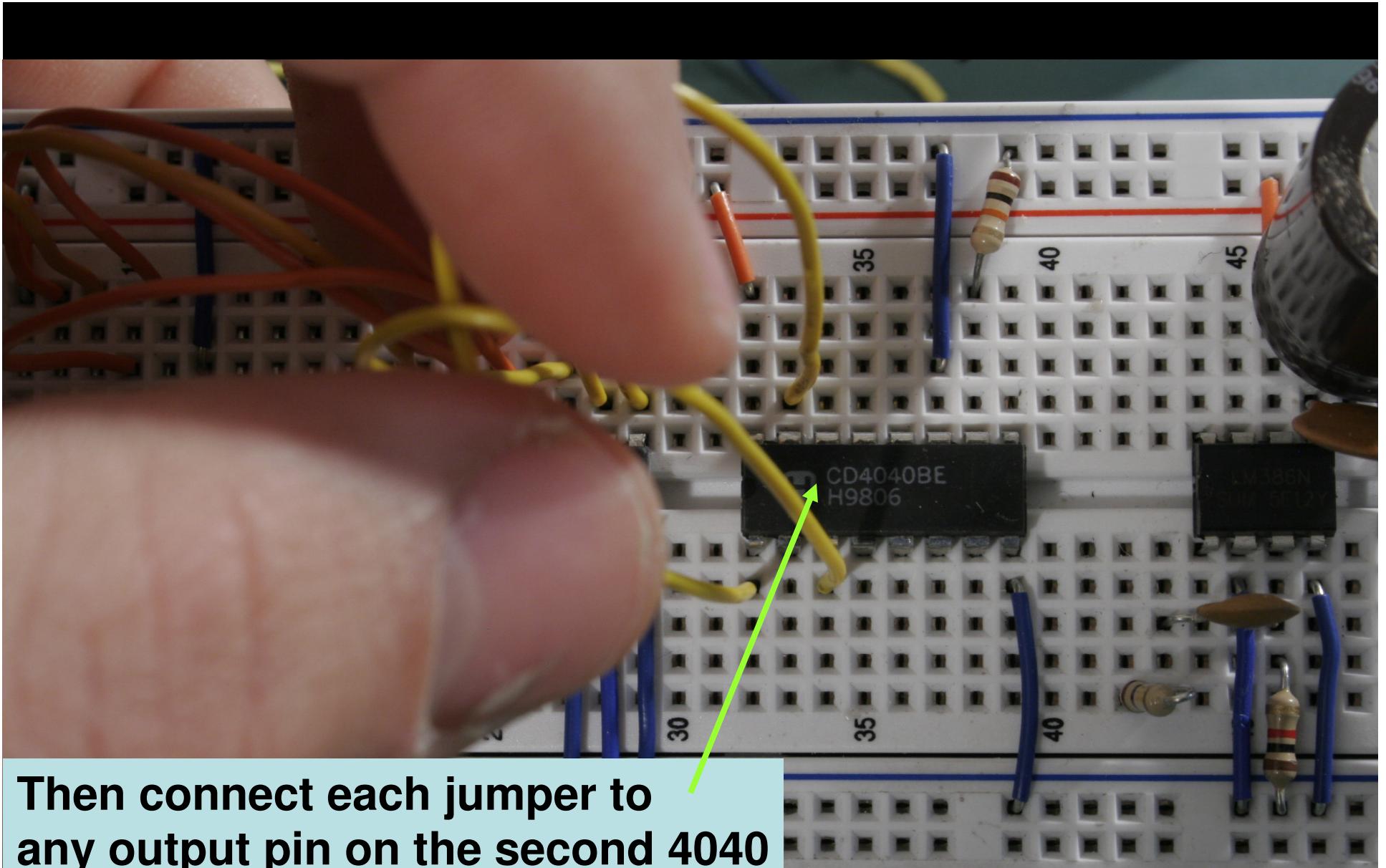
Connect one each to pins 9, 10 and 11 on the 4051



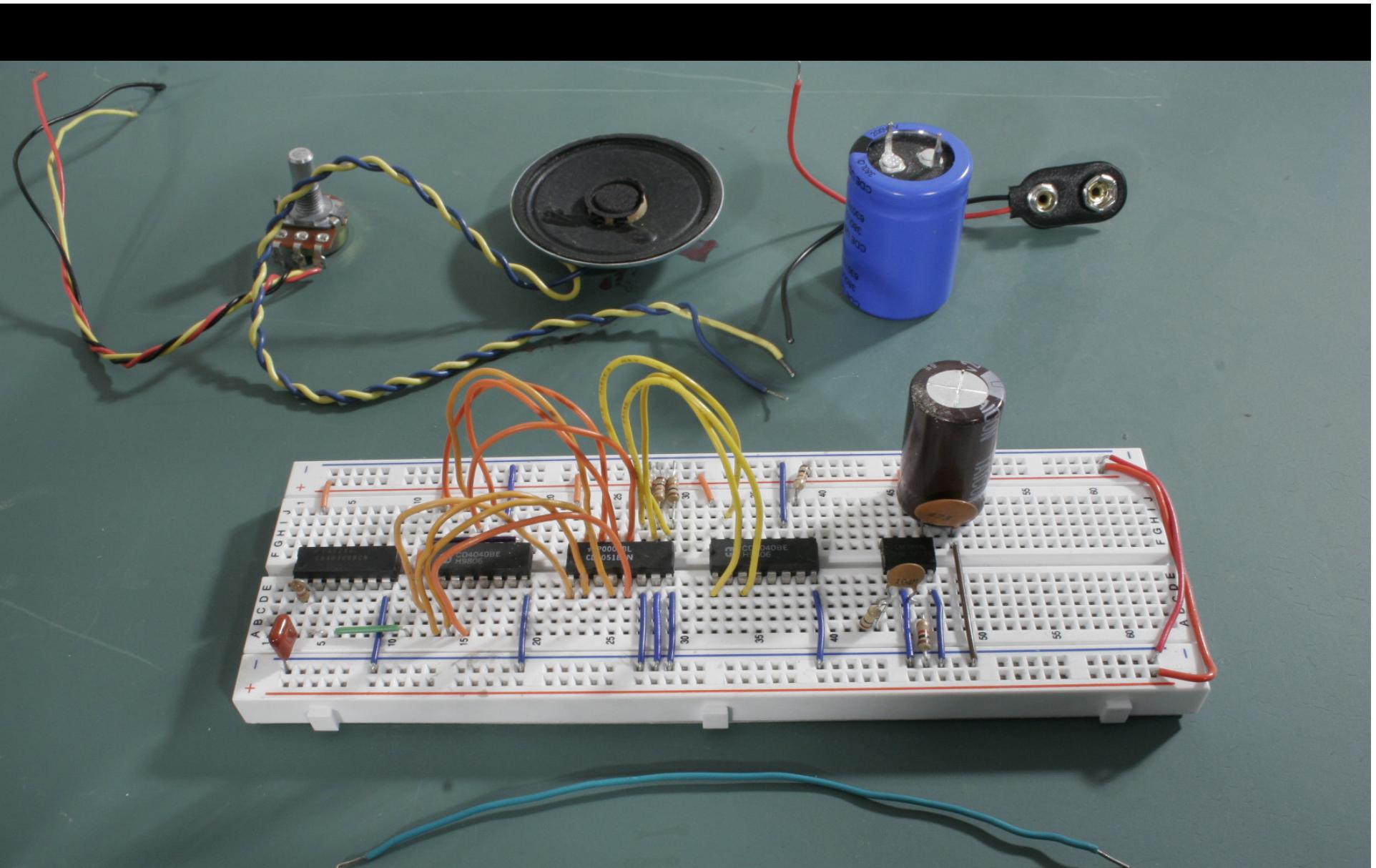
Then connect each jumper to
any output pin on the second 4040




Grab one long green jumper

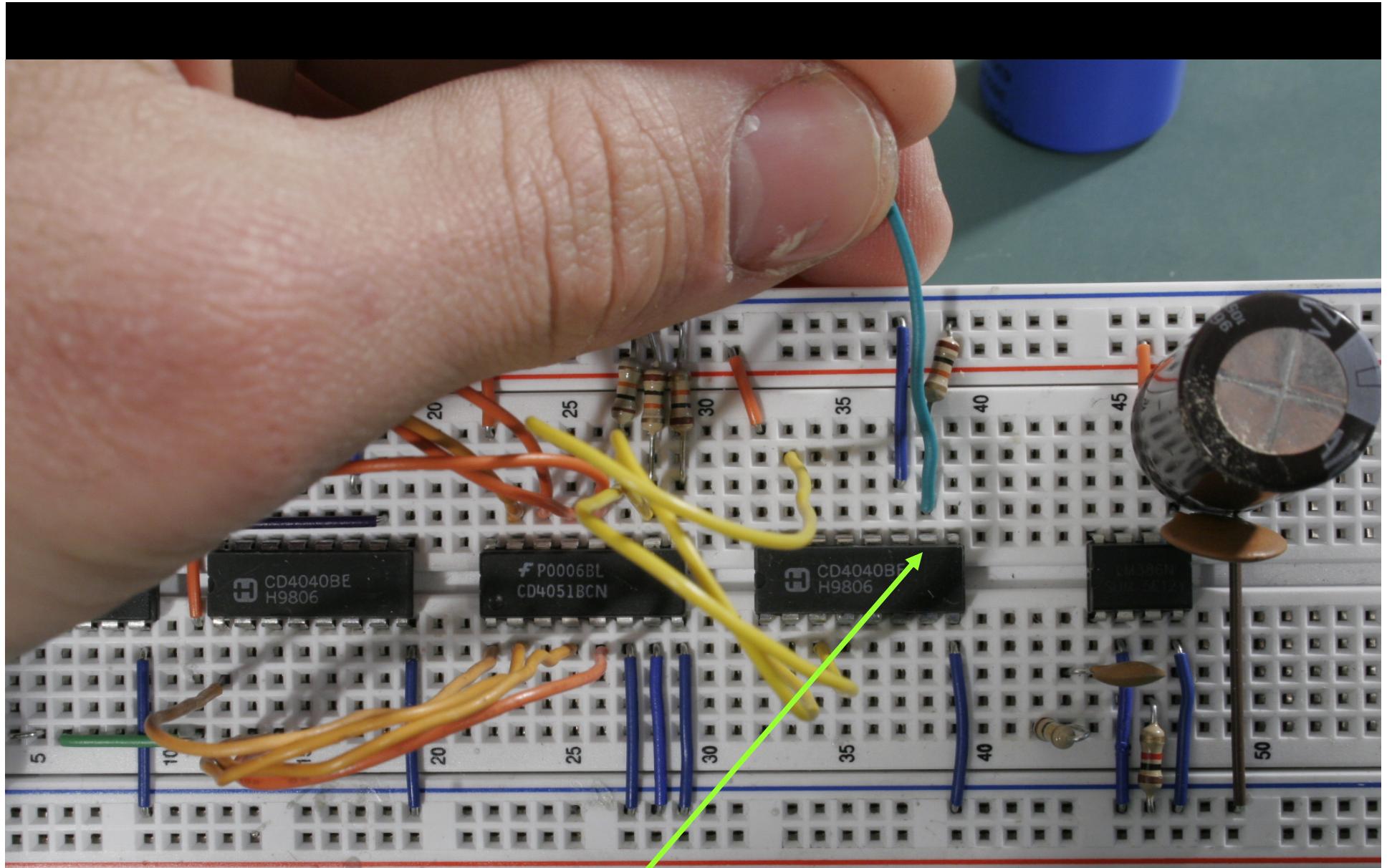

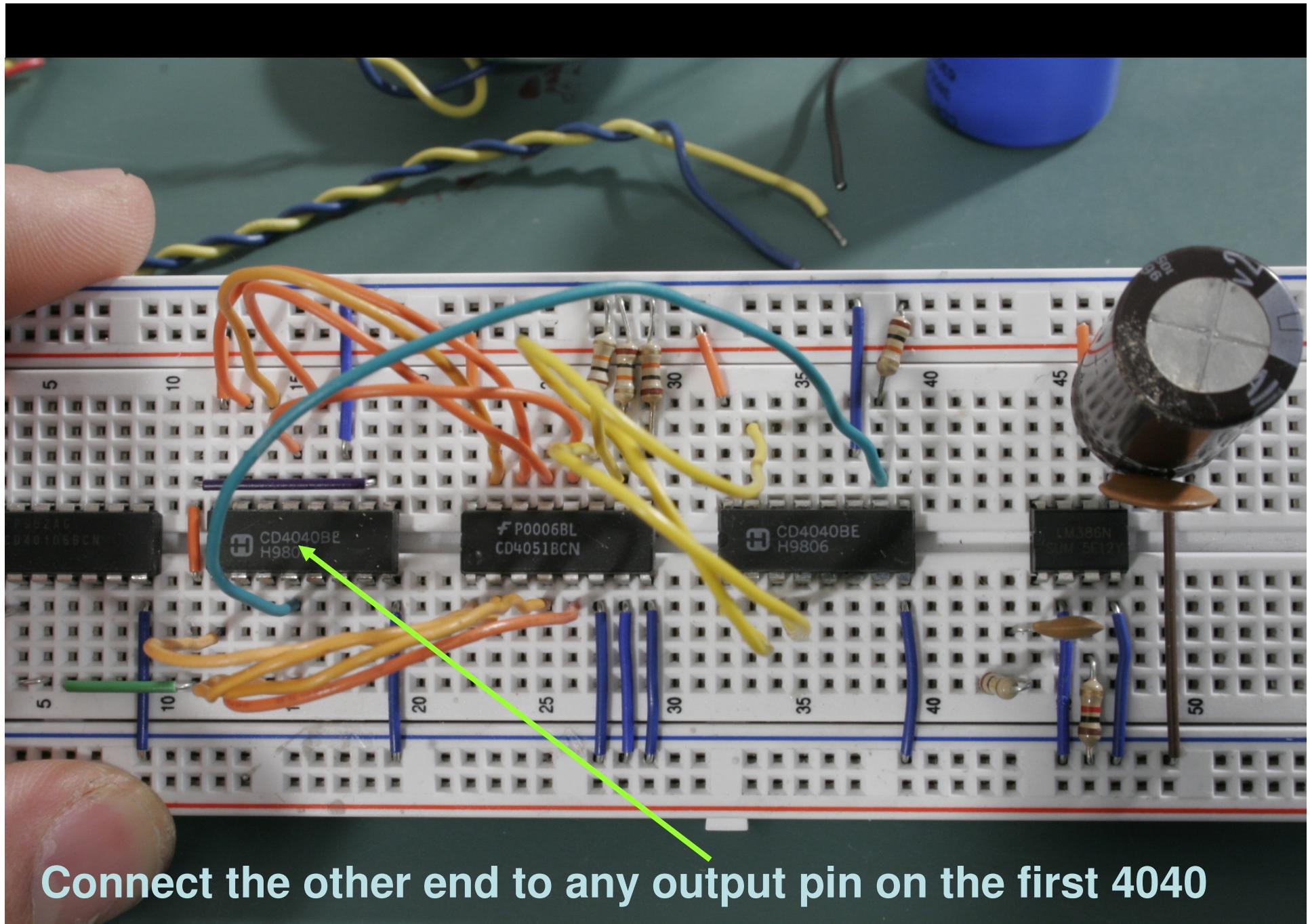Connect one end to pin 10 on the second 4040




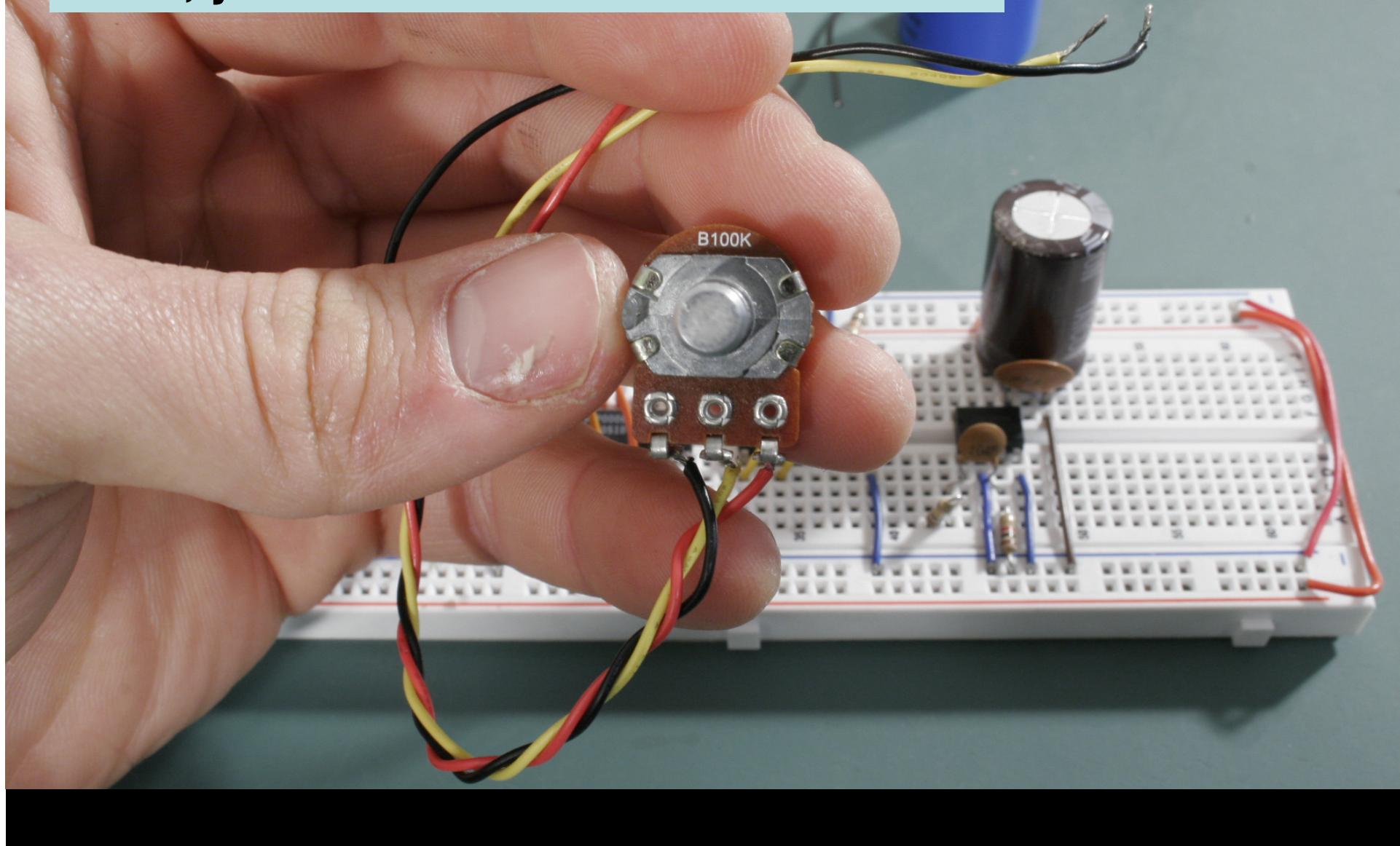**Solder up a potentiometer with
black, yellow and red wire as shown here:**



Solder up a potentiometer with black, yellow and red wire as shown here:


Lug 1 = black

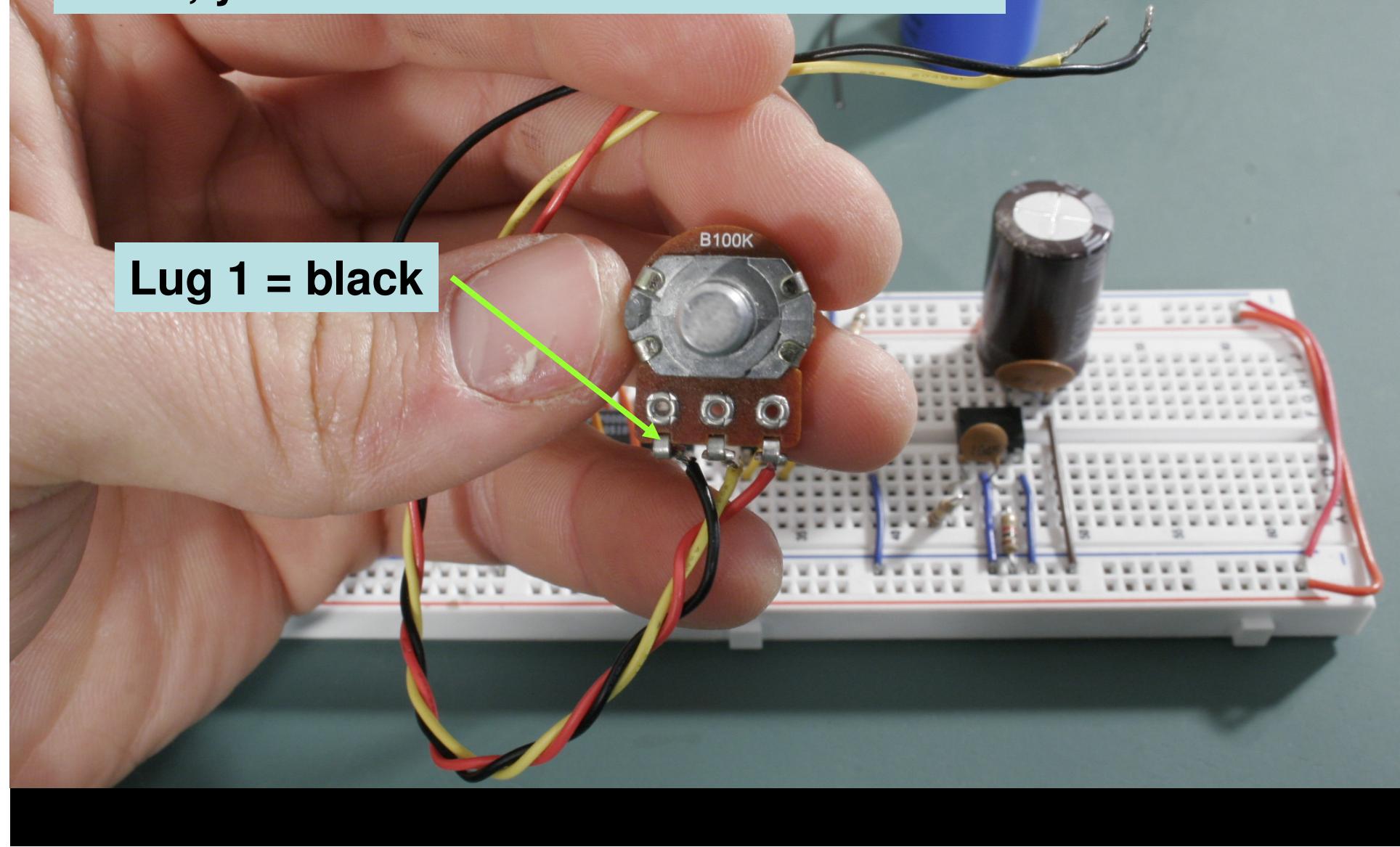

Solder up a potentiometer with black, yellow and red wire as shown here:

Lug 1 = black

Lug 2 = yellow

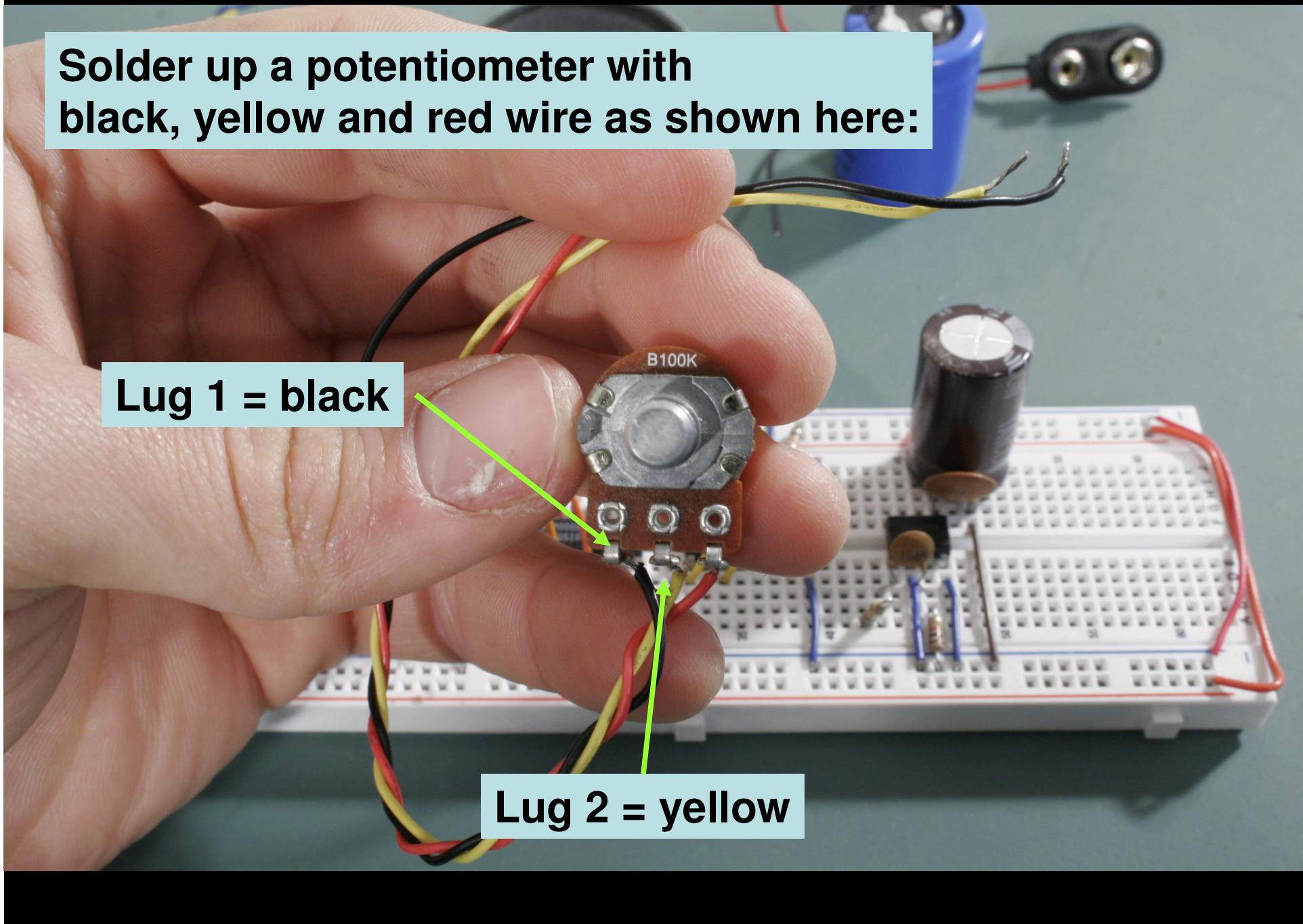



Solder up a potentiometer with black, yellow and red wire as shown here:

Lug 1 = black


Lug 3 = red

Lug 2 = yellow

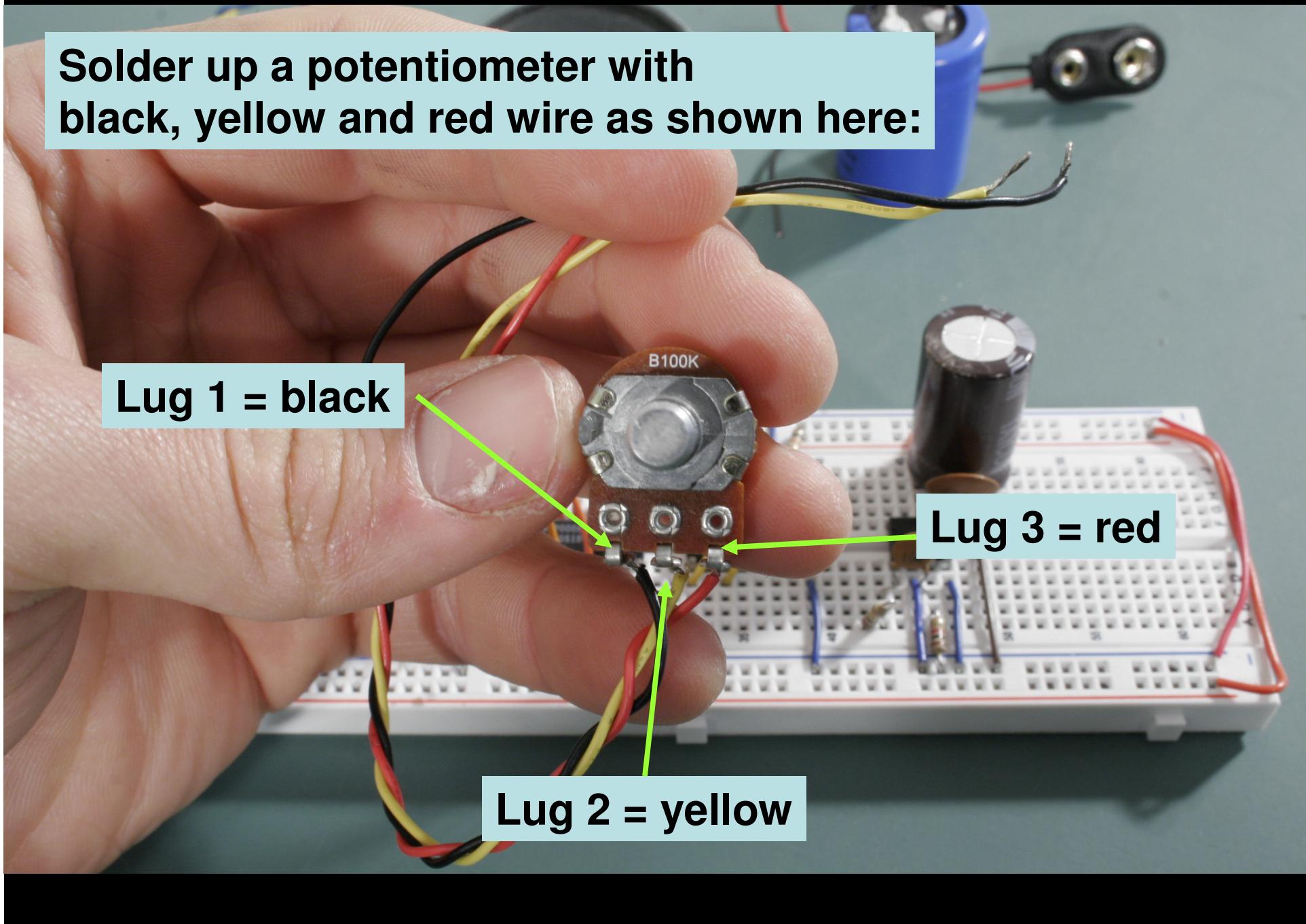

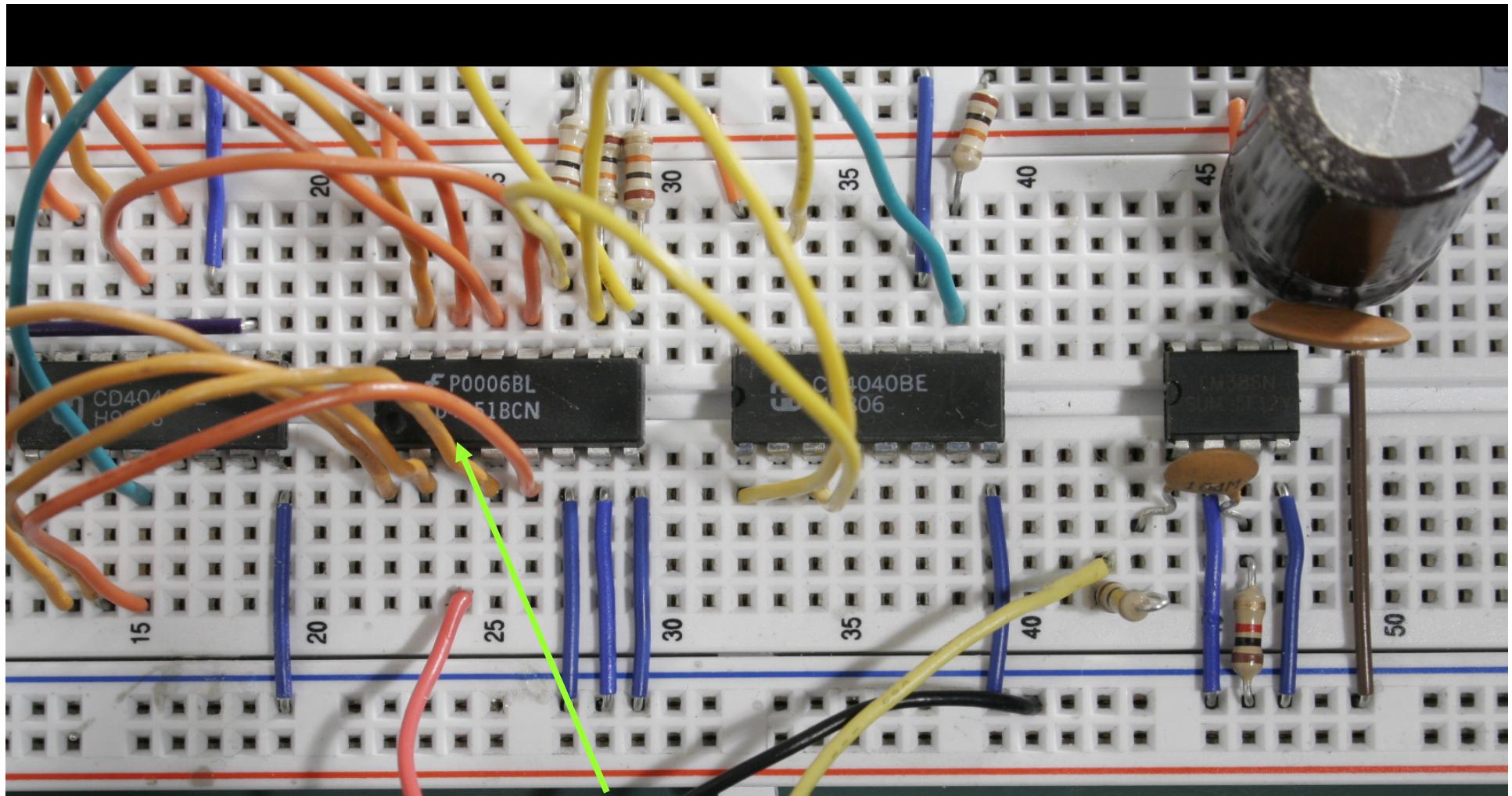


The red wire goes to pin3 on the 4051

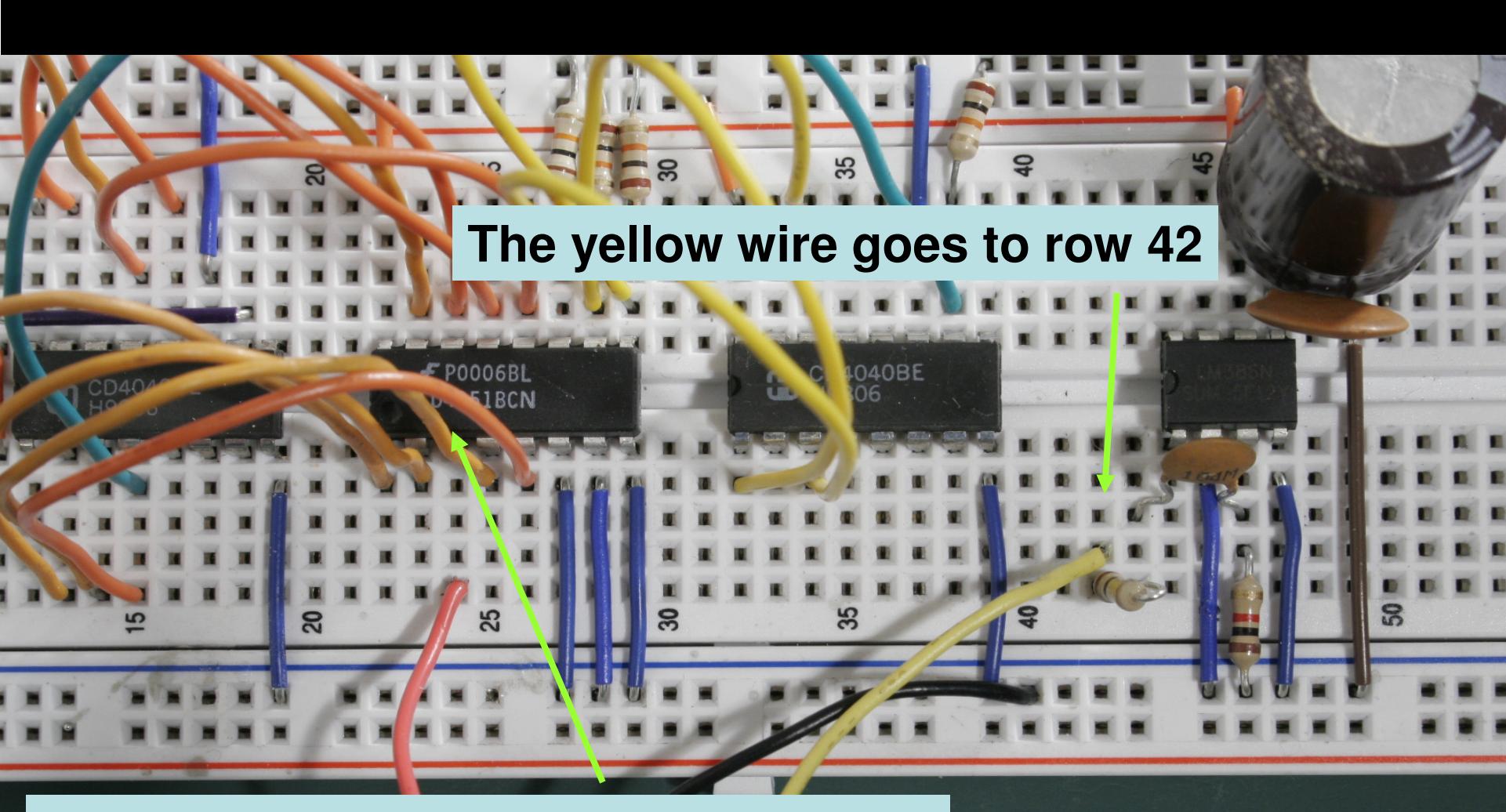

The yellow wire goes to row 42

The red wire goes to pin3 on the 4051

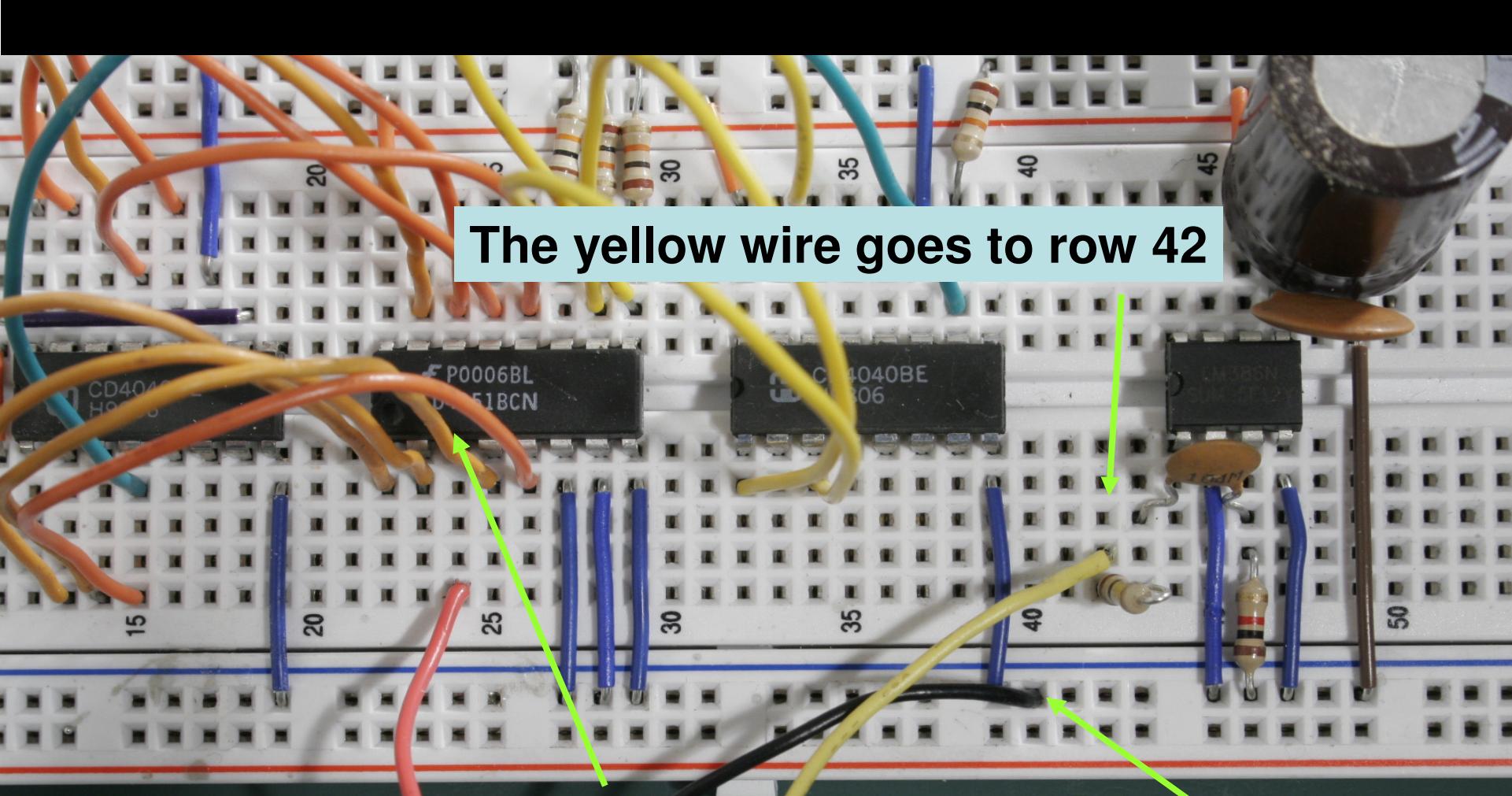


The yellow wire goes to row 42


The red wire goes to pin3 on the 4051

The black wire connects to ground

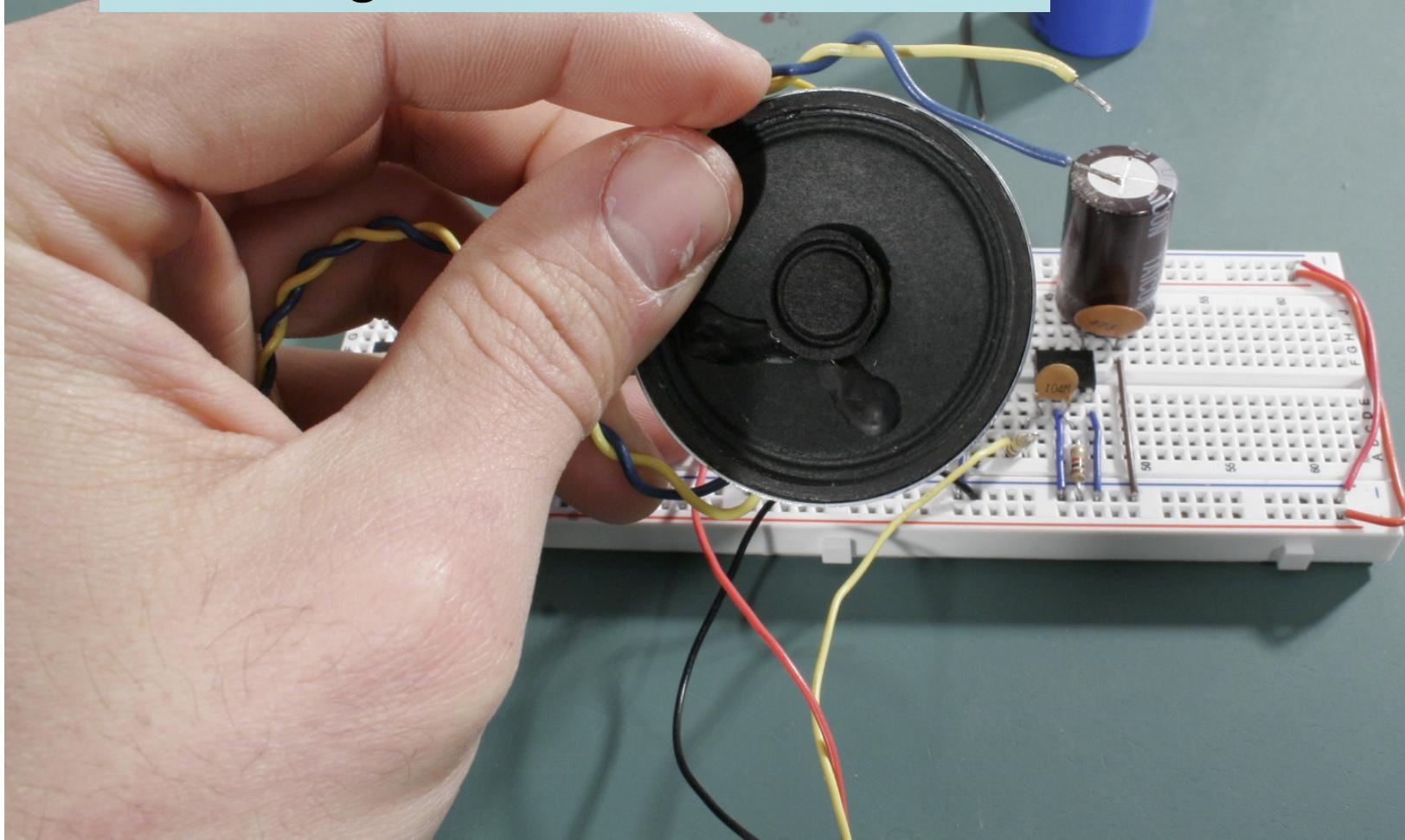
**Solder wires to your speaker.
Use a dark color for the “-” lug
and a brighter color to the “+” one.**



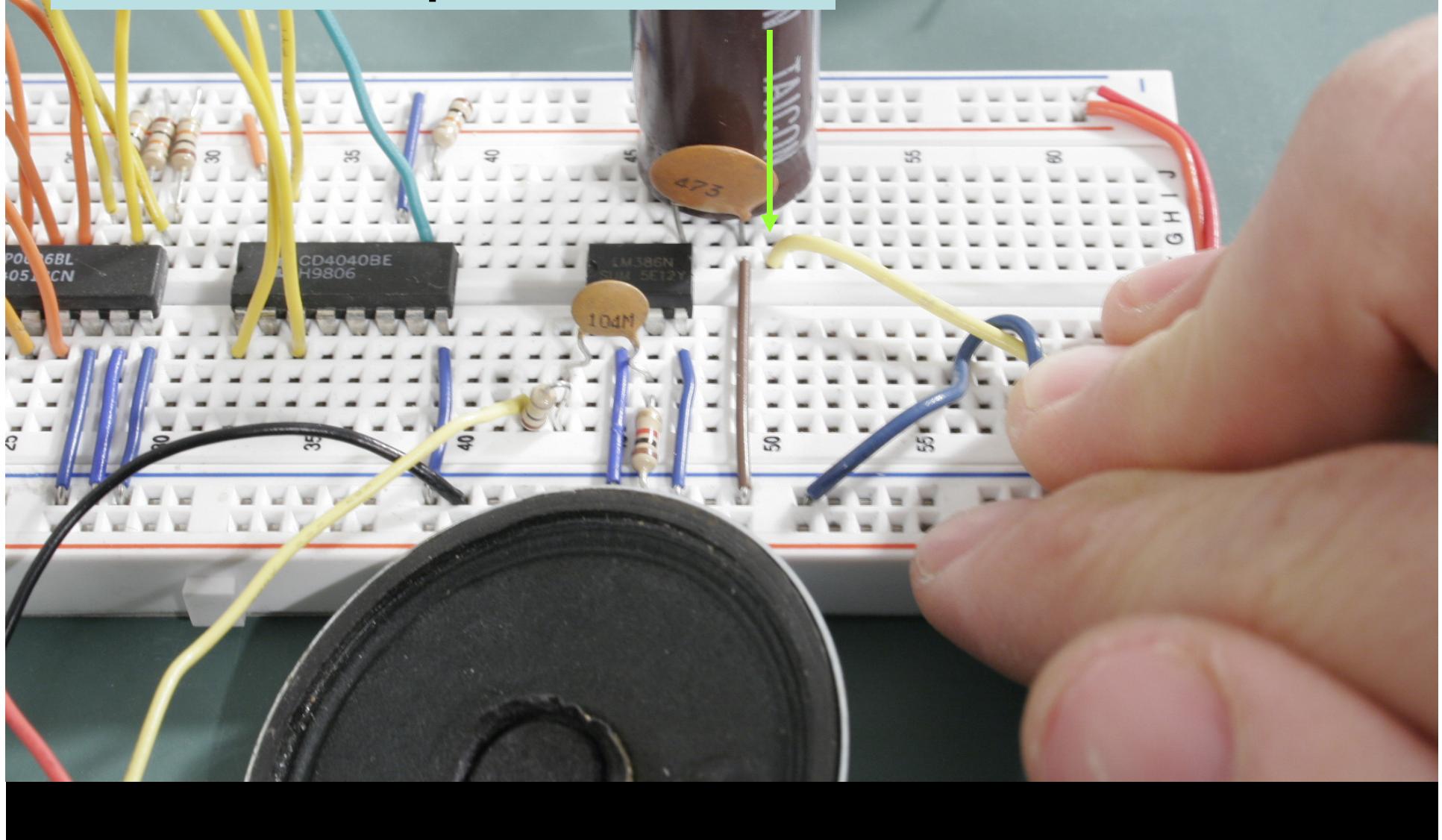
The “+” speaker wire connects to the 220 uF capacitor on row 50



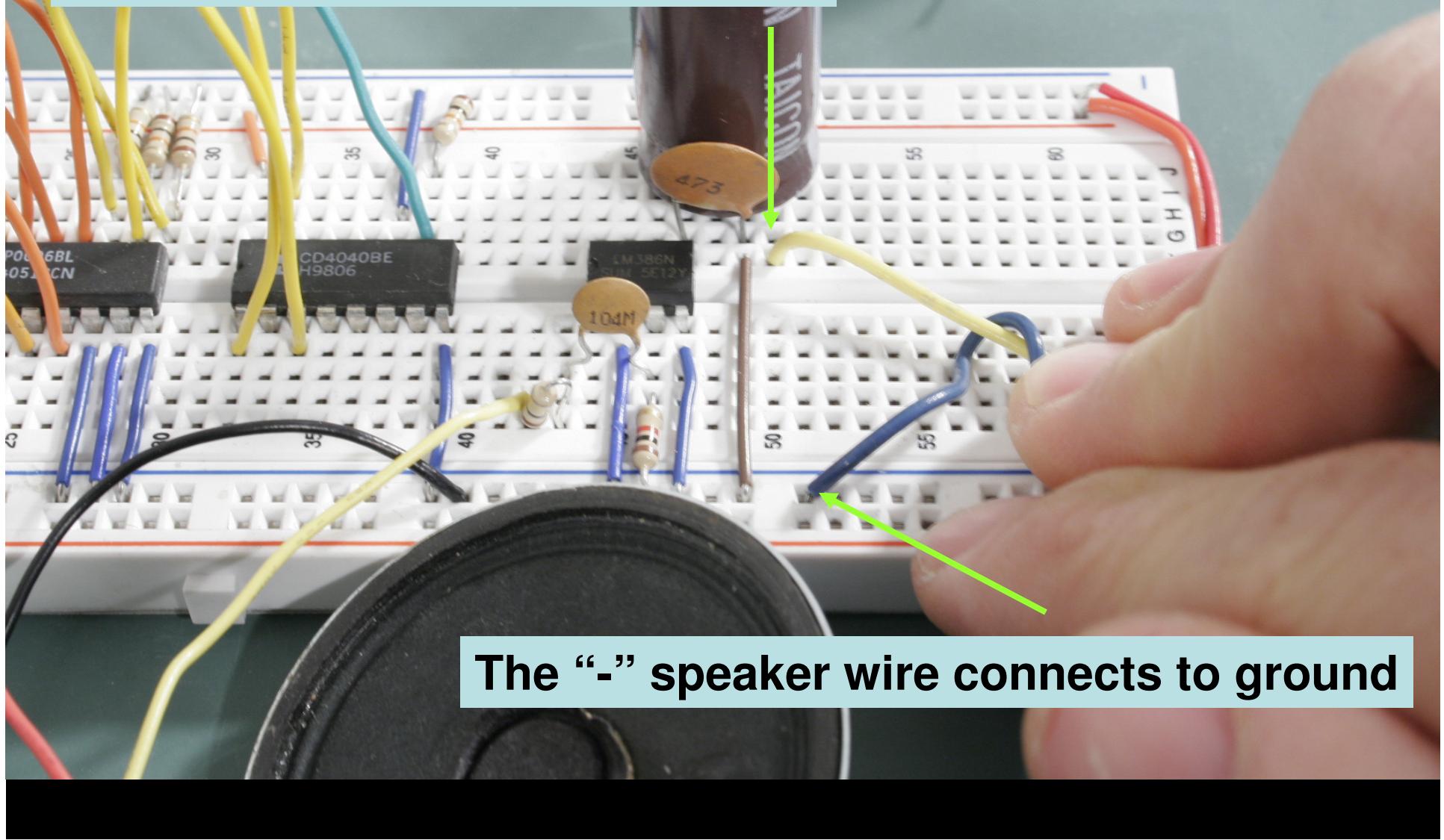
The “+” speaker wire connects to the 220 uF capacitor on row 50




Grab the battery connector.

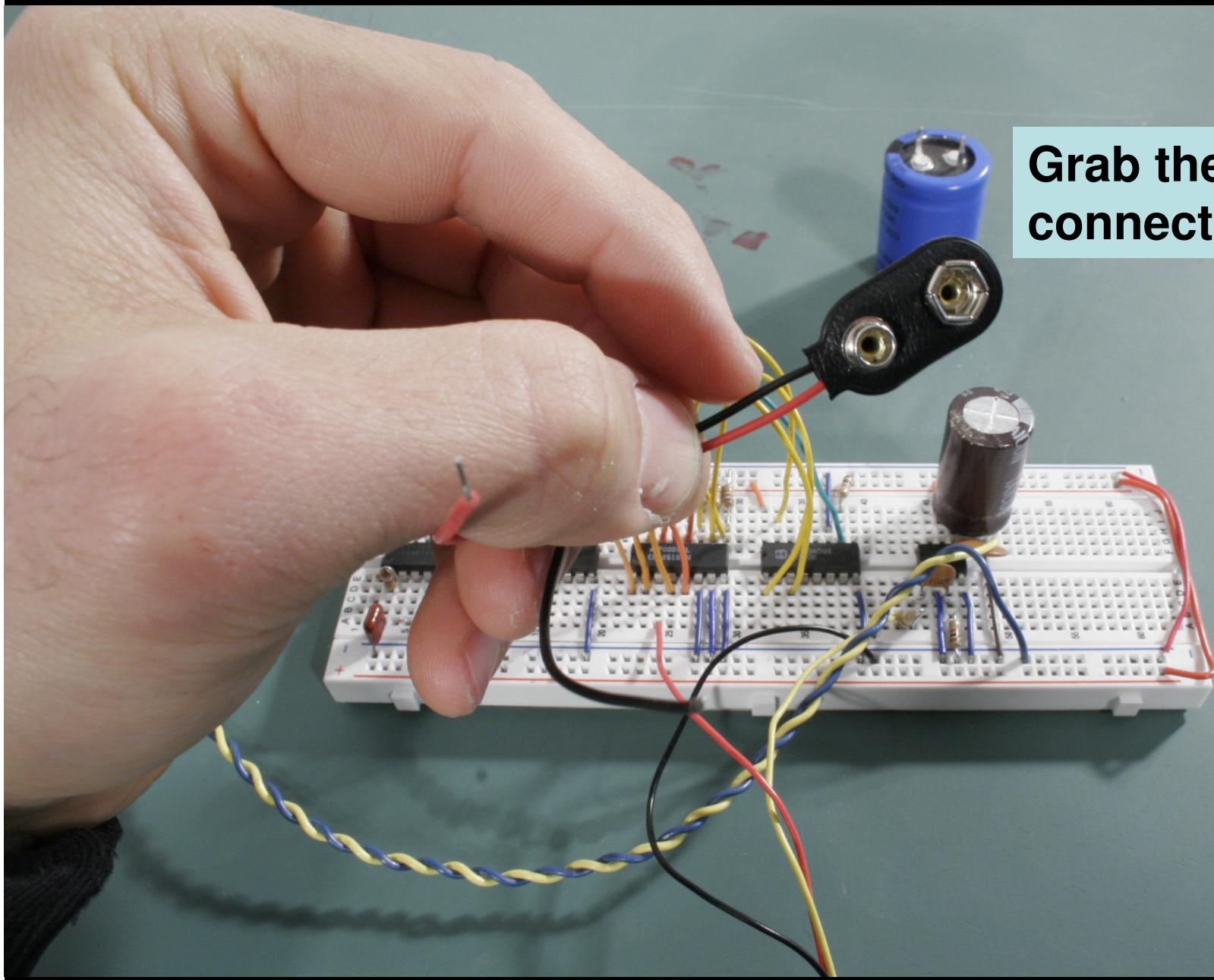


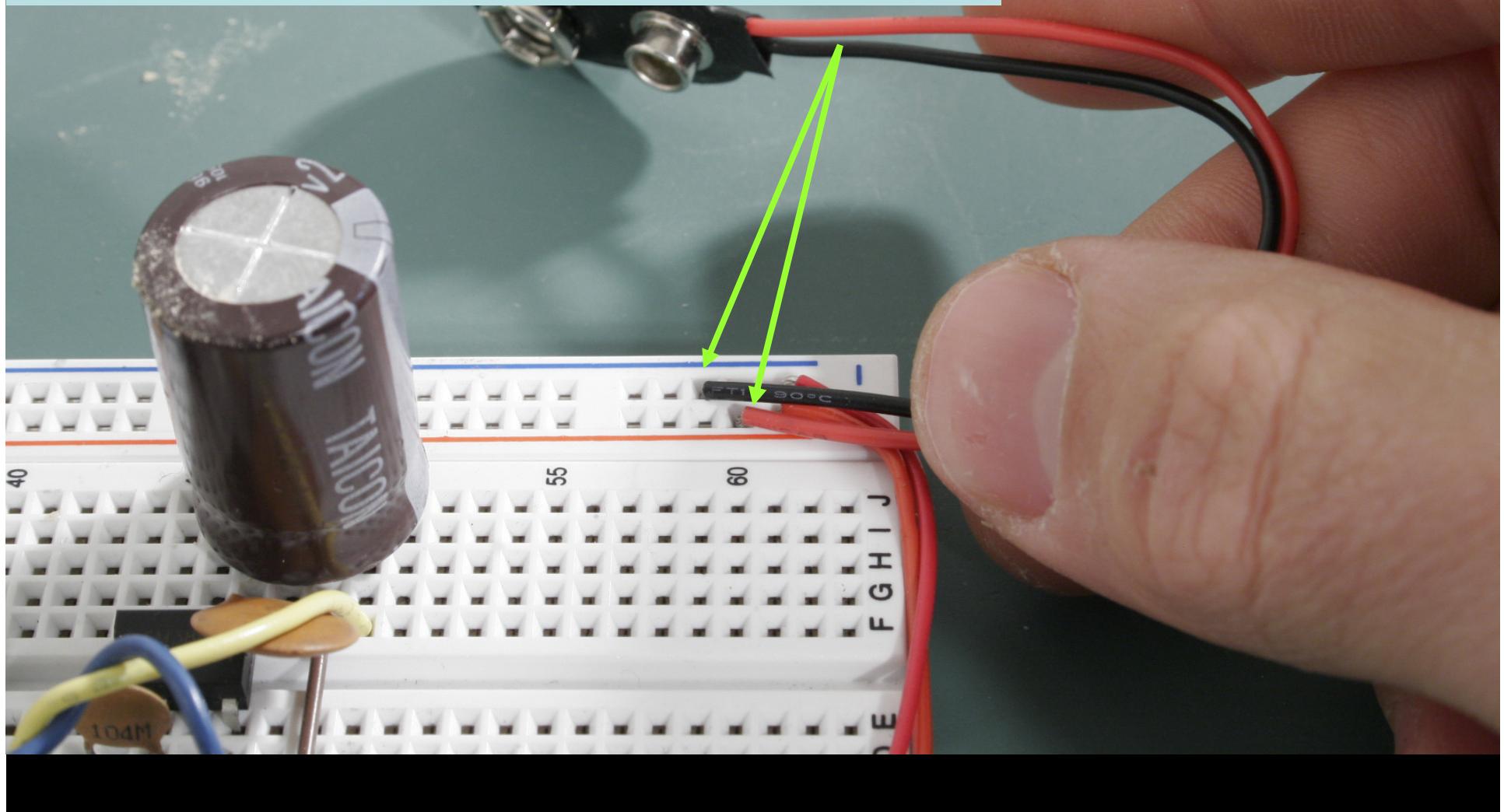**Connect the black lead to the ground rail
and the red lead to the positive supply.**



Find the 2200uf capacitor.

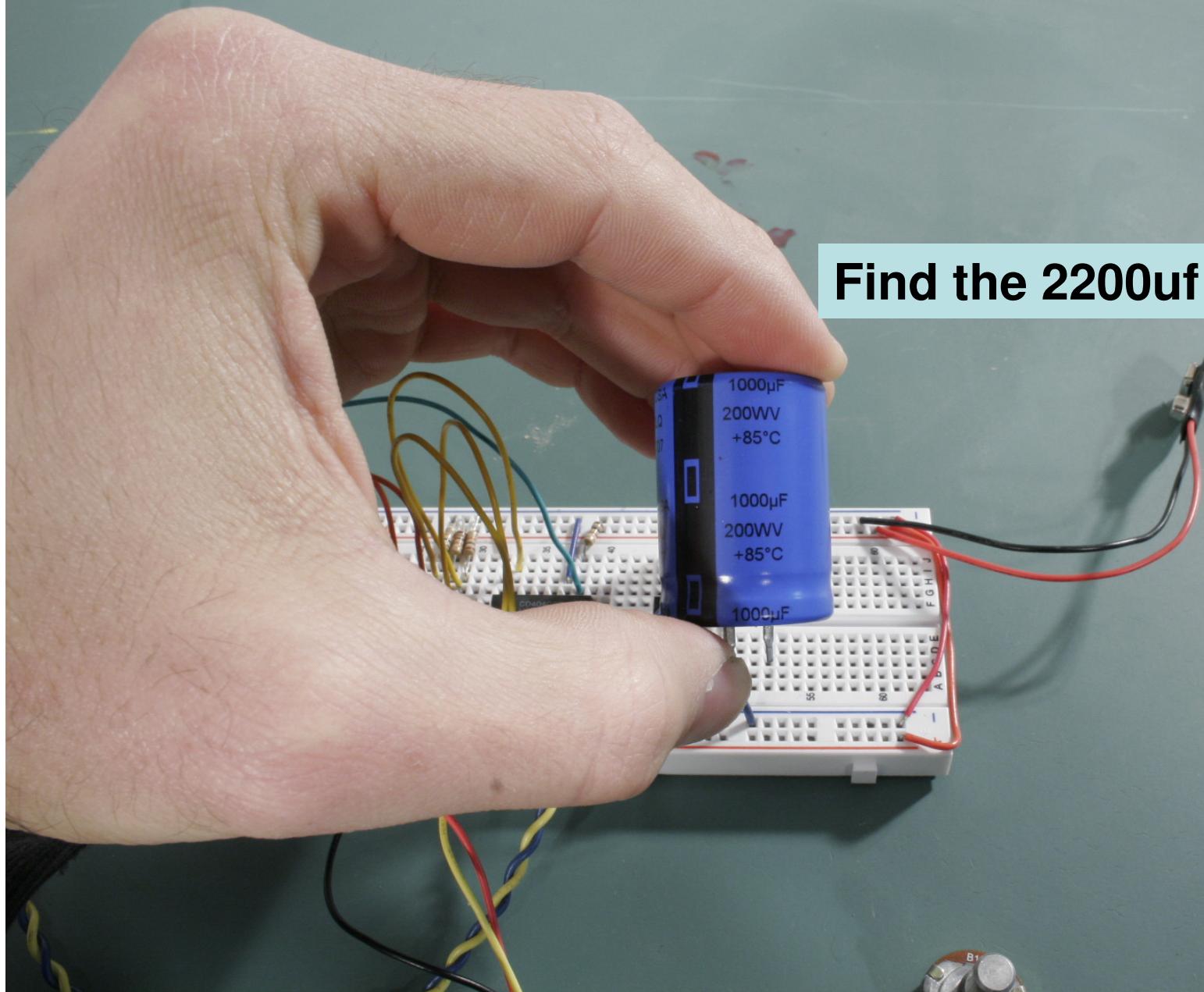


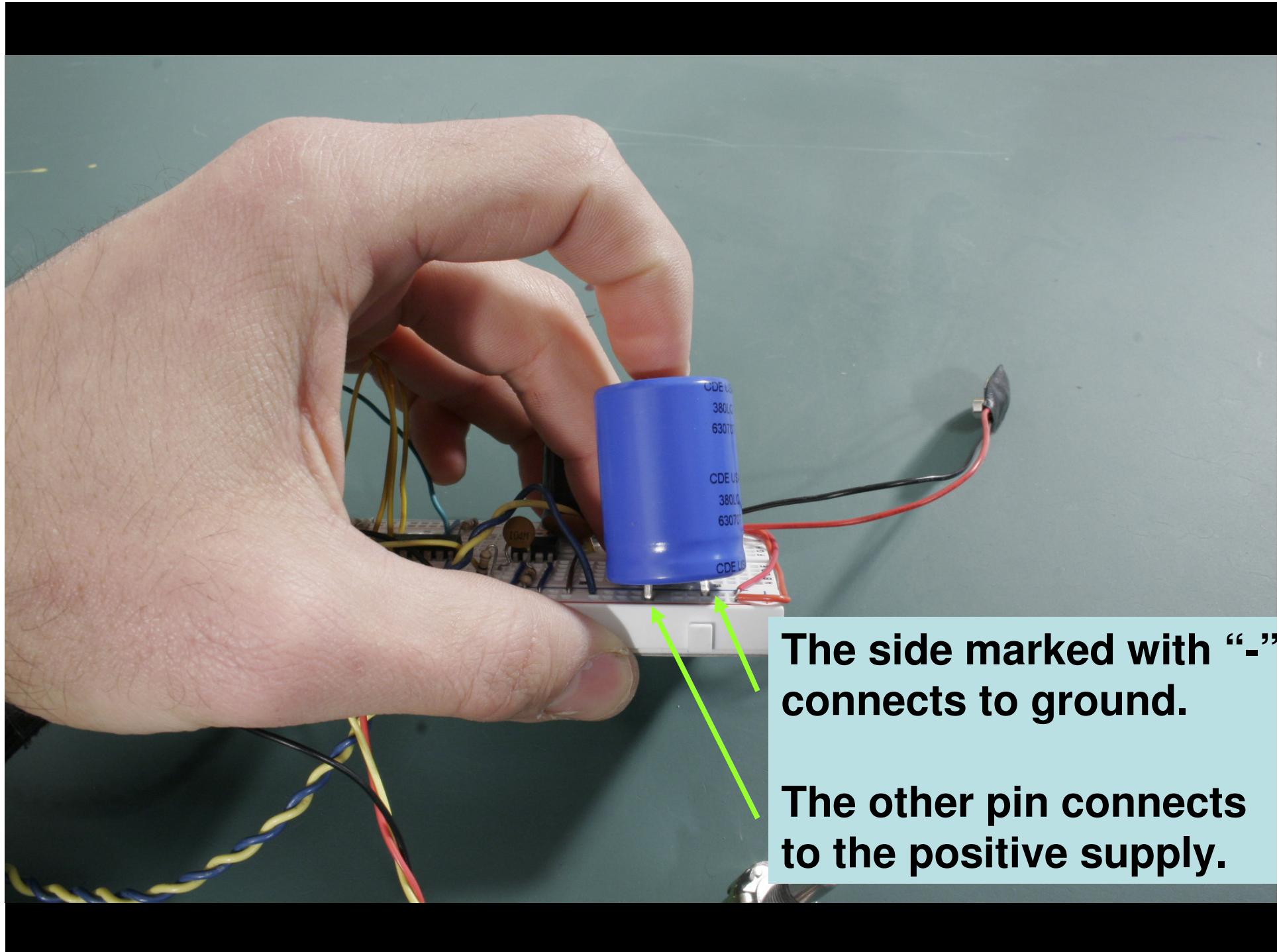


The side marked with “-” connects to ground.

The other pin connects to the positive supply.


Connect the battery!

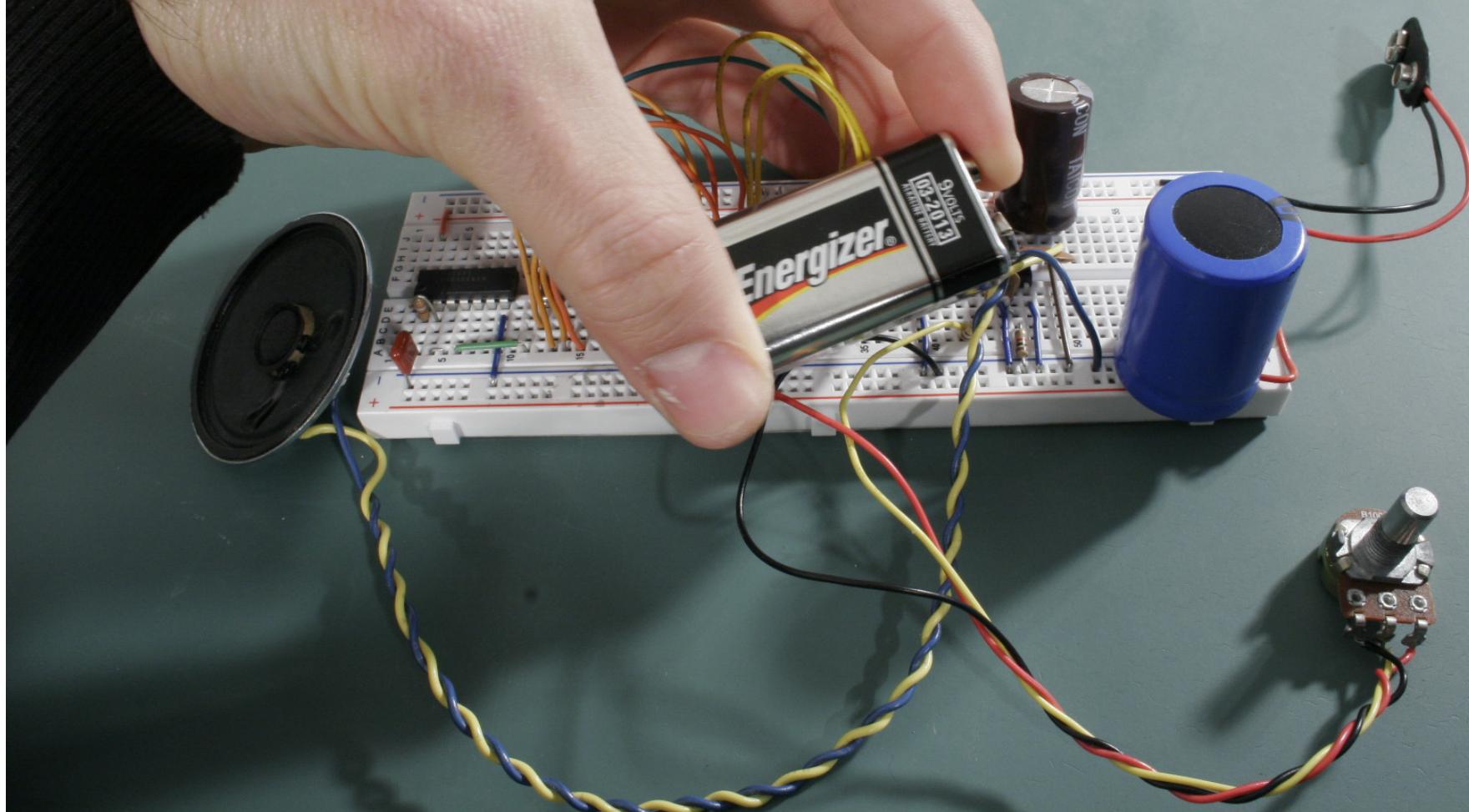

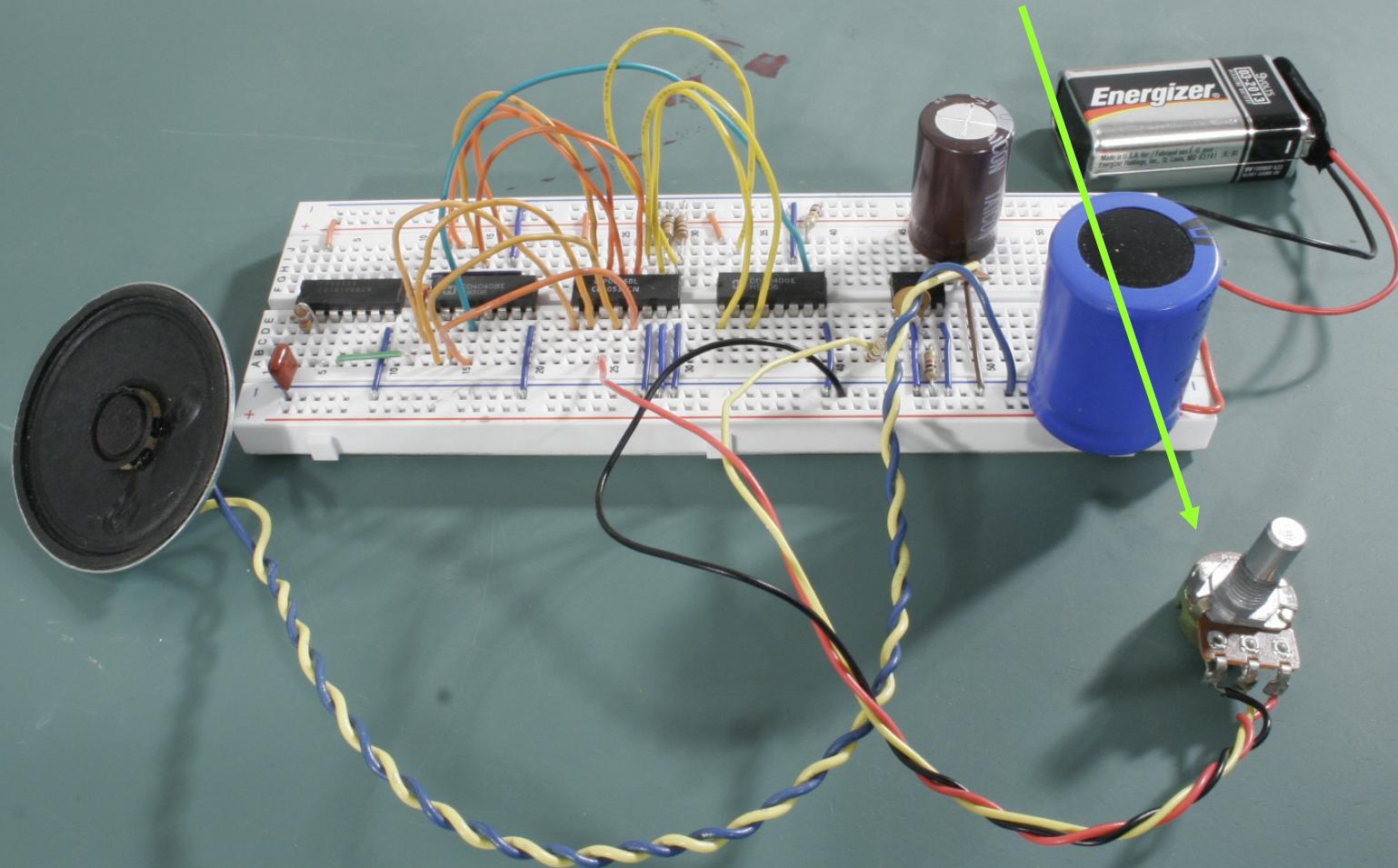
Turn up the volume with the potentiometer
and rock some 1 bit glitch!




Full Schematic

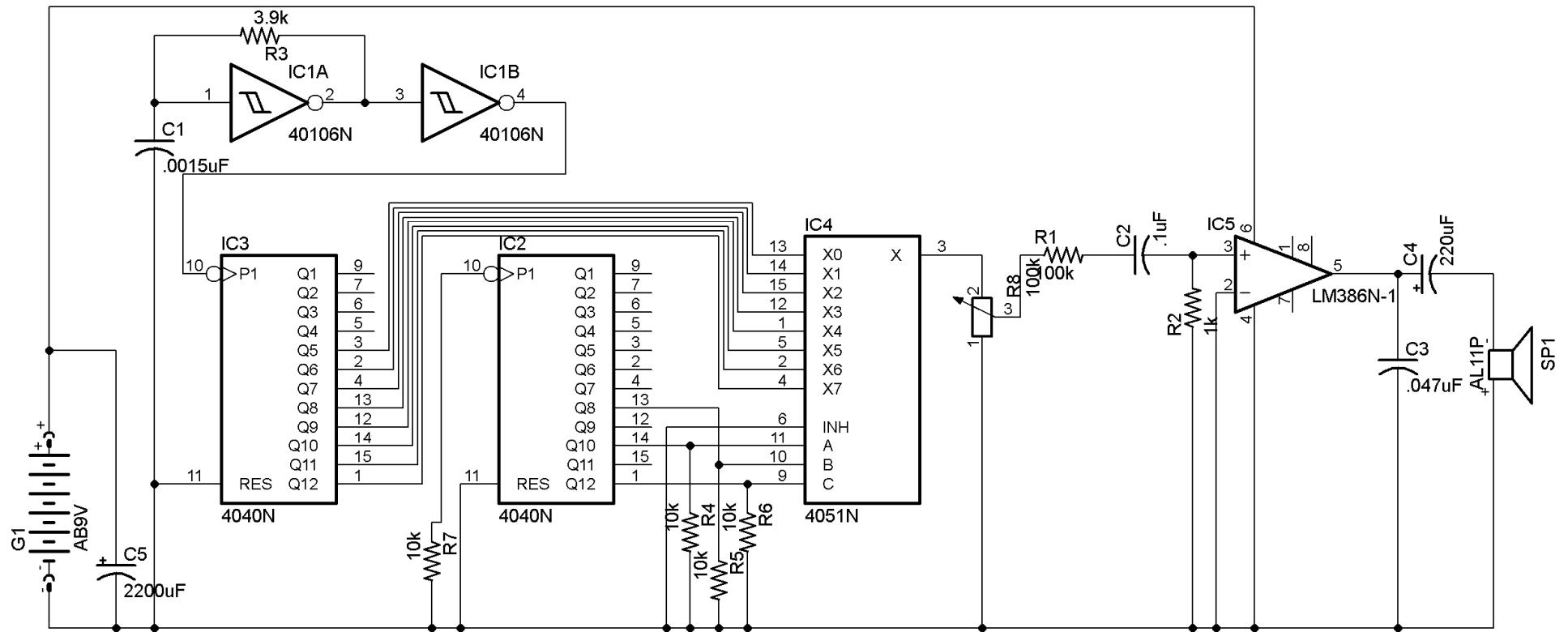

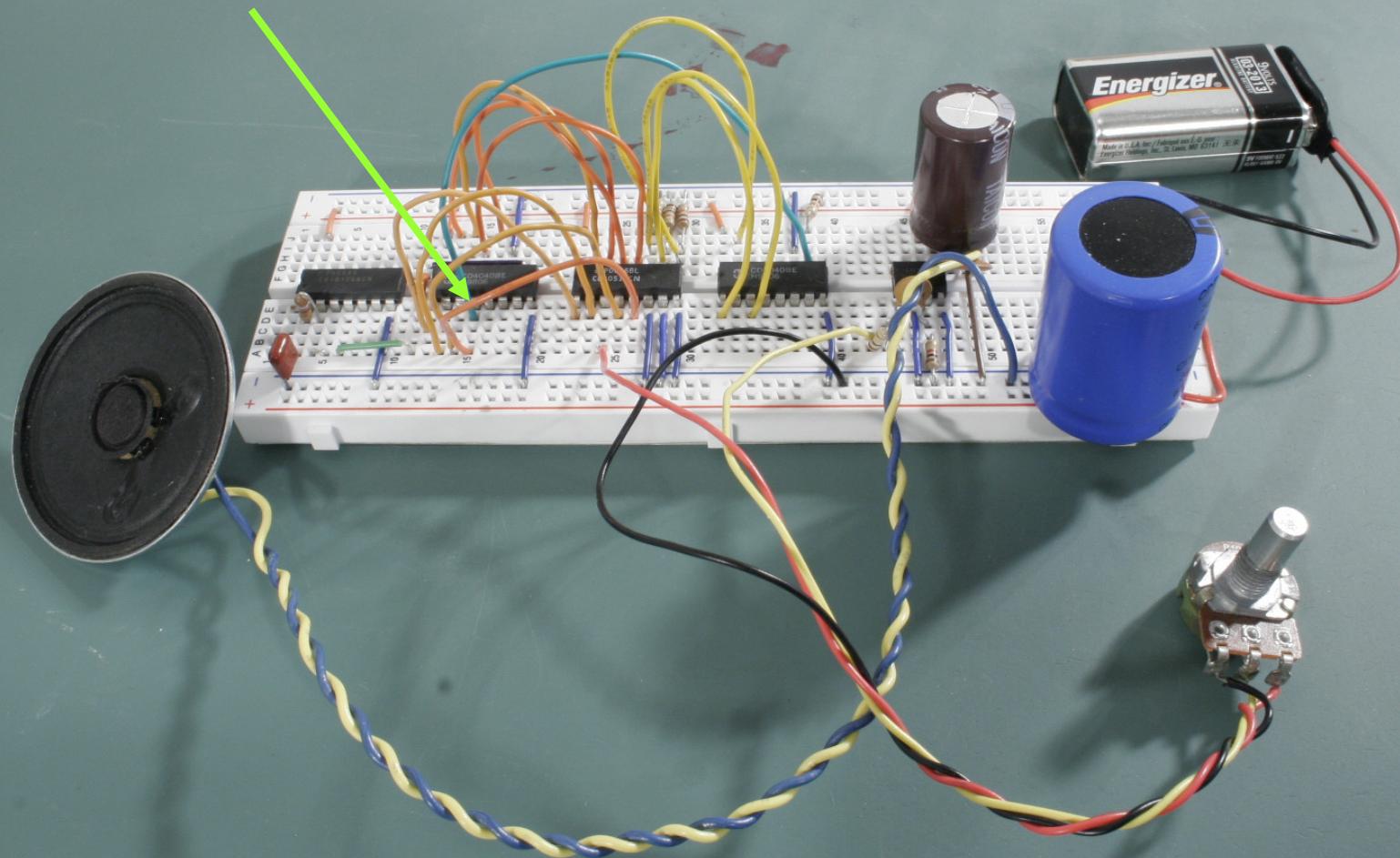Try changing the position of
this end of the green jumper



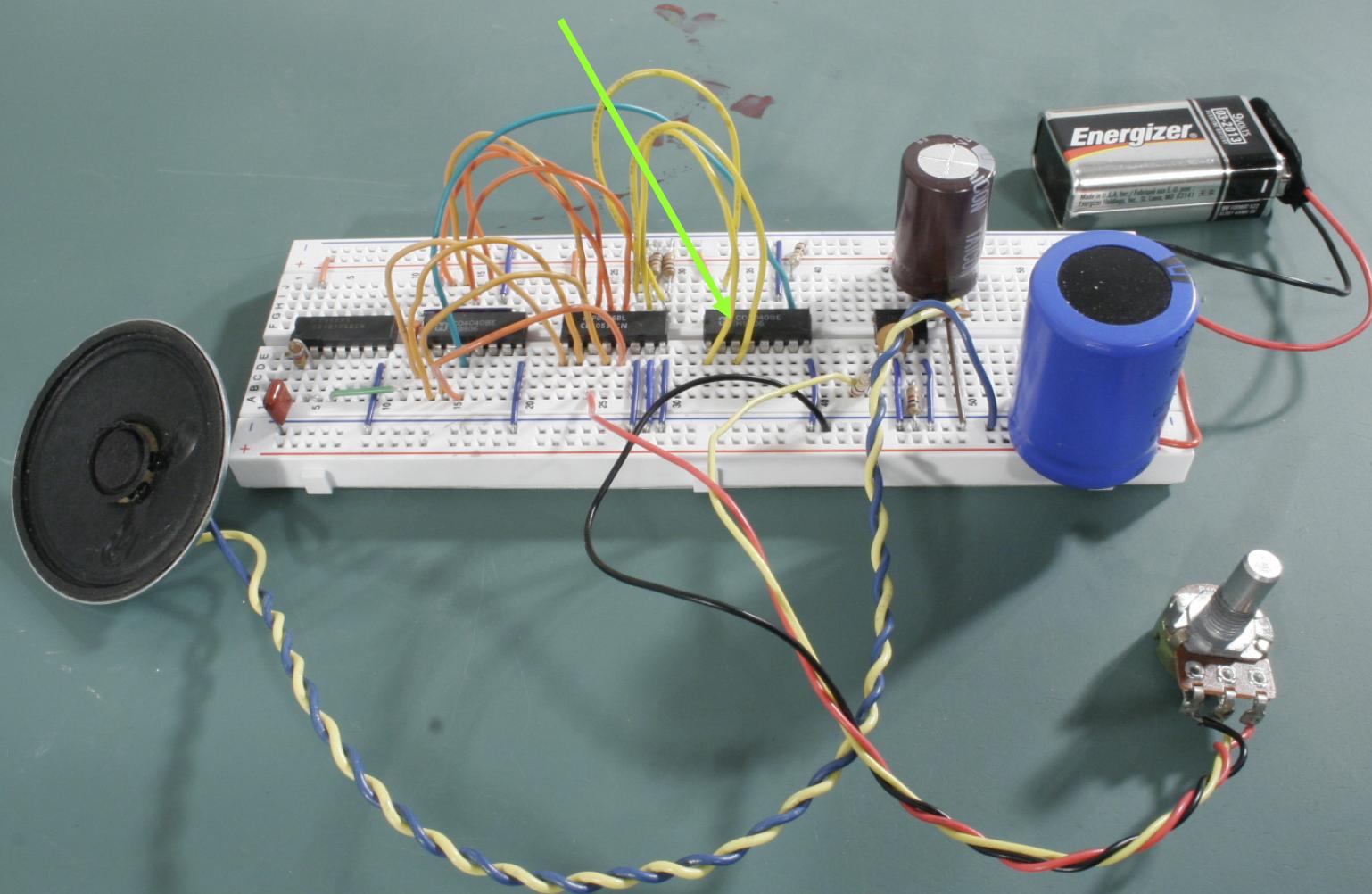Try changing the position of these yellow jumpers on this chip



You can also change the position of these orange jumpers on this chip

